

U.S.N.								
--------	--	--	--	--	--	--	--	--

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

May 2023 Semester End Main Examinations

Programme: B.E.

Semester: III

Branch: Computer Science and Engineering

Duration: 3 hrs.

Course Code: 22CS3PCLOD

Max Marks: 100

Course: Logic Design

Date: 19.05.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1 a) Analyze the given Truth Table. Reduce it to SOP and draw the logic diagram. **6**

X	Y	Z	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

b) Given the Boolean function, determine a minimal sum and minimal product using K-maps where w, x, y, z are variables. **6**
 $f(w, x, y, z) = \sum m(2,3,4,10,13,14,15) + \text{dc}(7,9,11)$

c) Using Quine McClusky method obtain the essential prime implicants for the expression given below. **8**
 $f(A, B, C, D) = \sum m(0,2,3,6,7,8,10,12,13)$

OR

2 a) Design a SOP circuit which accepts 3 inputs a, b and c and outputs a 1(HIGH) when input has exactly two 1's. **6**

b) Given the Boolean function, determine a minimal sum and minimal product using K-maps where w, x, y, z are variables. **6**
 $f(w, x, y, z) = \pi M(0,1,2,4,10,11,15) + \text{dc}(3,8,9)$

c) Simplify $f(w,x,y,z) = \sum m(0,5,6,7,9,10,13,14,15)$ using Quine McCluskey method. **8**

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

UNIT - II

3 a) Assume an adder/subtractor which is capable of handling two 4-bit operands. For each of the following set of unsigned operands, X & Y, and control input Add/Sub, determine the output. Check your answers by converting the binary numbers into decimal.

6

i) $X=0101, Y=0011, \text{Add/Sub}=0$

ii) $X=0101, Y=0011, \text{Add/Sub}=1$

Draw the logic diagram using parallel binary adder /subtractor using X-OR gate.

b) Using 3-to-8 decoder realize the following pairs of expressions. In each case gates should be selected as to minimize their total number of input terminals.

6

i) $f_1(x_2, x_1, x_0) = \sum m(1, 2, 4, 5)$

$f_2(x_2, x_1, x_0) = \sum m(0, 1, 3, 4, 5, 6)$

ii) $f_1(x_2, x_1, x_0) = \pi m(0, 3, 5)$

$f_2(x_2, x_1, x_0) = \pi m(1, 2, 3, 4, 5, 6)$

c) Realize each of the following Boolean expressions

8

i) using an 8-to-1 line multiplexer where w,x, and y appear on select lines S_2, S_1 and S_0 respectively

$f(w, x, y, z) = \sum m(0, 4, 6, 8, 9, 11, 13, 14)$

ii) using 4-to-1 line multiplexer and external gates implement

$f(w, x, y, z) = \sum m(4, 5, 7, 8, 10, 12, 15)$

Let w and x appear on the select lines S_1 and S_0 respectively.

UNIT - III

4 a) Explain Programmable Array Logic with a neat diagram.

6

b) Design the PROM for the following function.

6

$f_1(x, y, z) = \sum m(0, 1, 2, 5, 7)$

$f_2(x, y, z) = \sum m(1, 2, 4, 6)$

c) Design a PLA 4x5x2 i.e 4 inputs, 5 AND gates and 2 OR gates for the following functions.

8

$f_1(w, x, y, z) = \sum m(2, 4, 5, 10, 12, 13, 14)$

$f_2(w, x, y, z) = \sum m(2, 9, 10, 11, 13, 14, 15)$

UNIT - IV

5 a) List the different types of Registers. Explain Serial In Parallel Out with neat diagram.

6

b) Explain the working of Master-Slave JK flip flop with timing diagram.


6

c) Derive the characteristic equation for SR flip flop, JK flip flop and D flip flop.

8

UNIT - V

 6 a) Design a MOD-6 synchronous up counter using JK flip flop 10
b) Given the state transition diagram using Moore Model design the sequence detector that receives the binary data with the pattern '011'.
Note: Consider data coming from Left to Right



OR

7 a) Design a synchronous up counter using JK flip flop for the given sequence 10
2,3,7,5,6,4
b) Design a sequence detector that receives binary data stream at its input X and signals when a combination '011' arrives at the input by making its output , Y high which otherwise remains low. Consider data coming from Left to Right i.e first bit to be identified is 1, second 1 and third 0 from the input sequence. Design the above sequence detector using Mealy Model.
