

U.S.N.								
--------	--	--	--	--	--	--	--	--

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## April 2024 Semester End Main Examinations

**Programme: B.E.**

**Branch: Computer Science and Engineering**

**Course Code: 23CS3PCLOD**

**Course: Logic Design**

**Semester: III**

**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

			<b>UNIT - I</b>		<b>CO</b>	<b>PO</b>	<b>Marks</b>
<b>Important Note:</b> Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.	1	a)	Suppose a 3-variable truth table has high output for these input values:000, 010, 100, 110. Draw the SOP circuit		CO1	PO1	<b>6</b>
		b)	Implement the K-Map for the given Boolean expression. Obtain the minimal sum (SOP) and minimal product(POS). Using Quine McClusky method obtain the essential prime implicants for the expression given below. $f(w,x,y,z) = \sum m (0,1,2,4,5,7,9,12)$		CO2	PO2	<b>6</b>
		c)	Using Quine McClusky method obtain the essential prime implicants for the expression given below. $f(w,x,y,z) = \sum m (2,7,9,12,14,15) + dc(0,8,13)$		CO2	PO2	<b>8</b>
			<b>OR</b>				
	2	a)	Design a SOP circuit which accepts 3 inputs a, b and c and outputs a 1(HIGH) when input has exactly two 1's.		CO1	PO1	<b>6</b>
		b)	Given the Boolean function, determine a minimal sum and minimal product using K-maps where w, x, y, z are variables. $f(w, x, y, z) = \sum m (2,3,4,10,13,14,15) + dc (7,9,11)$		CO2	PO2	<b>6</b>
		c)	Using Quine McClusky method obtain the essential prime implicants for the expression given below. $f(A, B, C, D) = \sum m (0,2,3,6,7,8,10,12,13)$		CO2	PO2	<b>8</b>
			<b>UNIT - II</b>				
	3	a)	Realize each of the following Boolean expressions using an 8-to-1 line multiplexer choosing a, b and c as select lines $f(a,b,c,d) = \sum m(0,1,5,6,7,9,10,15)$		CO2	PO2	<b>6</b>
		b)	i. Using 3-to-8 decoder realize the following pairs of expressions. $f1(a,b,c) = \sum m (0,2,3,5,6,7)$ $f2(a,b,c) = \sum m (1,3,4,6,7)$		CO2	PO2	<b>6</b>

		ii. Using 3-to-8 decoder realize the following pairs of expressions with active low outputs and AND gates. $f1(a,b,c) = \pi M(0,1,3,5,6)$ $f2(a,b,c) = \pi M(2,3,4,5,7)$			
	c)	Design a 2-bit comparator that compares the magnitude of two binary numbers (i.e greater than, less than and equal to the other) with truth table and neat logic diagram.	CO3	PO3	8
		<b>UNIT - III</b>			
4	a)	Design the PROM for the following function. $f1(x,y,z) = \sum m(0,1,2,5,7)$ $f2(x,y,z) = \sum m(1,2,4,6)$	CO3	PO3	4
	b)	Design a $3 \times 4 \times 2$ PLA i.e 3 inputs, 4 AND gates and 2 OR gates for the following functions. $f1(w,x,y,z) = \sum m(1,2,3,7)$ $f2(w,x,y,z) = \sum m(0,1,2,6)$ Use XOR gate to show the true and complemented form of the function.	CO3	PO3	8
	c)	Design the PAL with 4-inputs and 3-outputs to implement the following function. $f1(A,B,C) = \sum m(0,3,4,5,6)$ $f2(A,B,C) = \sum m(1,3,5,6,7)$ $f3(A,B,C) = \sum m(0,4,5)$	CO3	PO3	8
		<b>UNIT - IV</b>			
5	a)	Illustrate the working of basic bi-stable element with neat diagram.	CO1	PO1	6
	b)	Explain the working of Master-Slave JK flip flop with neat timing diagram.	CO1	PO1	6
	c)	Derive the characteristic equation for SR flip-flop, JK flip flop and D flip flop.	CO2	PO2	8
		<b>UNIT - V</b>			
6	a)	Explain Combinational circuit and Sequential circuit with example.	CO1	PO1	6
	b)	Differentiate between Mealy model and Moore model	CO2	PO2	6
	c)	Design a MOD-6 synchronous up-counter using JK flip flop.	CO3	PO3	8
		<b>OR</b>			
7	a)	Design a synchronous up-counter using JK flip flop for the given counting sequence. 000, 101, 001, 111, 011, 100	CO3	PO3	10
	b)	Design a sequence detector that receives binary data stream at its input X and signals when a combination '011' arrives at the input by making its output, Y high which otherwise remains low. : Consider data coming from Left to Right i.e first bit to be identified is 1, second 1 and third 0 from the input sequence. Design the above sequence detector using Mealy Model.	CO3	PO3	10