

U.S.N.


B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

June 2025 Semester End Main Examinations**Programme: B.E.****Semester: III****Branch: Computer Science and Engineering****Duration: 3 hrs.****Course Code: 23CS3PCLOD / 22CS3PCLOD****Max Marks: 100****Course: Logic Design**

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.			UNIT - I	CO	PO	Marks
	1	a)	Simplify using K map $Y(a,b,c,d)=\sum m(7,9,10,11,12,13,14,15)$	CO2	PO2	10
		b)	Simplify the equation $Y=(A+B)((A'(B'+C'))'+A'(B+C))$	CO2	PO2	5
		c)	With neat diagram and truth table explain basic gates.	CO1	PO1	5
			OR			
	2	a)	Minimize using Quine McClusky method. $Y(A,B,C,D)=\sum(0,1,2,3, 10,11,12,13,14, 15)$	CO1	PO1	10
		b)	Prove that $A(A'+C)(A'B+C)(A'BC+C')=0$	CO1	PO1	5
		c)	Write $Y(A,B,C)=A'B'C'+A'BC+AB'C+ABC$ as Sum of product and Product of Sum.	CO2	PO2	5
			UNIT - II			
	3	a)	Realize function $Y(A,B,C,D)=\sum(0,2,3,4,5,8,9,10,11,12,13,15)$ using 8:1 multiplexer.	CO2	PO2	6
		b)	Realize 16:1 multiplexer using 4:1 multiplexer with suitable examples.	CO2	PO2	6
		c)	Design 4:1 multiplexer using basic gates.	CO2	PO2	8
			OR			
	4	a)	Design 2:4 decoder.	CO2	PO2	6
		b)	Realize $f1=\sum m(0,4,6)$ and $f2=\sum m(0,5)$ using 3:8 decoder.	CO2	PO2	6
		c)	Design BCD to decimal decoder.	CO2	PO2	8

 			UNIT - III				
5	a)	Realize $F1(a,b,c)=\sum m(0,1,3,5,7)$ and $F2(a,b,c)=\sum m(1,2,5,6)$ using PROMs.	CO2	PO2	6		
	b)	Compare different programmable devices.	CO1	PO1	6		
	c)	Explain structure of PAL?	CO2	PO2	8		
		OR					
6	a)	Realize $A=XY+XZ'$ and $B= XY'+ YZ + XZ'$ using PLA.	CO2	PO2	6		
	b)	Realize $A=XY+XZ'$ and $B= XY' +YZ'$ using PAL.	CO2	PO2	6		
	c)	With a neat diagram explain structure of PROM.	CO1	PO1	8		
		UNIT - IV					
7	a)	Design SR latch using NOR gates.	CO3	PO3	6		
	b)	Derive characteristic equation for JK FF.	CO3	PO3	6		
	c)	Design positive edge triggered JK flip flop. Also write truth table and timing diagram.	CO3	PO3	8		
		OR					
8	a)	Derive characteristic equation for SR Flip flop.	CO3	PO3	6		
	b)	Design SR flip flop with enable input.	CO3	PO3	6		
	c)	How Master slave JK flip flop overcomes the toggling of JK flip flop.	CO3	PO3	8		
		UNIT - V					
9	a)	Design 3-bit ripple counter.	CO3	PO3	6		
	b)	Compare mealy and Moore machines	CO3	PO3	6		
	c)	Design mod6 synchronous counter using JK flip flops.	CO3	PO3	8		
		OR					
10	a)	Design 3bit up/down counter using JK flip flops.	CO3	PO3	6		
	b)	Convert the given mealy machine to Moore machine. 	CO3	PO3	6		
	c)	Design Mealy machine to check for 011 in the bit stream.	CO3	PO3	8		