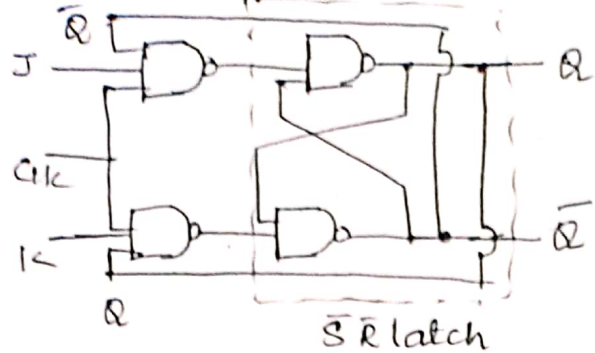


JK flip flop





State Table of $\overline{S}\overline{R}$ Latch.

$\overline{S}$	$\overline{R}$	Q	$\overline{Q}$	
0	0	1*	1*	invalid / not used.
0	1	1	0	
1	0	0	1	
1	1	Q	$\overline{Q}$	memory / NC.



Case 1:- When $J=0, K=0$ Clk=0 ;
When Clk=0, the flip flop retains its previous output irrespective of the i/p values at J and K.

Case 2:- When Clk=1, $J=0, K=1$ let $Q=0$

a) let $Q=0$.

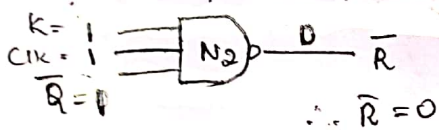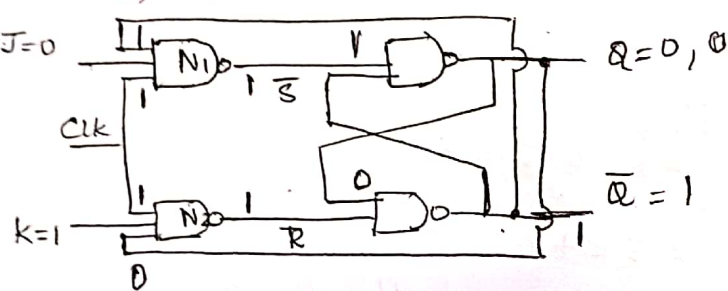

b) let $Q=1$

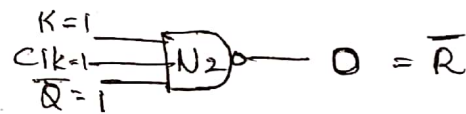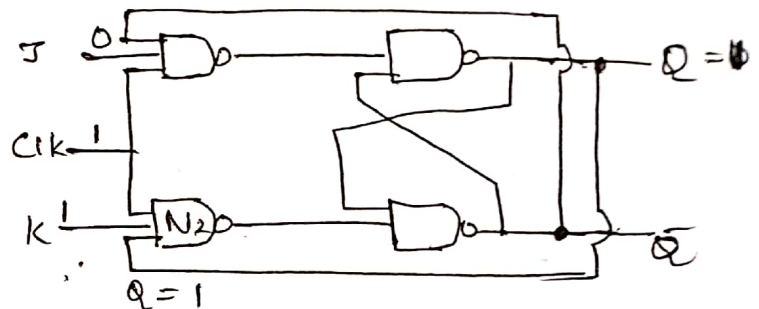




$J=0, Clk=1, Q=1$
 $N1$ output $\overline{S} = 1$
 $N2$ output $\overline{R} = 0$
 $\therefore \overline{S}, \overline{R} = 1, 0$

hence from state table of $\overline{S}\overline{R}$ latch
 $Q_{t+1} = 0, \overline{Q}_{t+1} = 1$

$J=0, Clk=1, Q=0$
 $N1$ output $\overline{S} = 1$
 $N2$ output $\overline{R} = 0$
 $\therefore \overline{S}, \overline{R} = 1, 0$
 $\therefore$ from $\overline{S}\overline{R}$ latch state table $Q_{t+1} = 0, \overline{Q}_{t+1} = 1$

Case 2:- When $J=1$, $K=0$ and $Clk=1$

a) $Q = 0$.

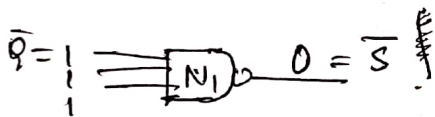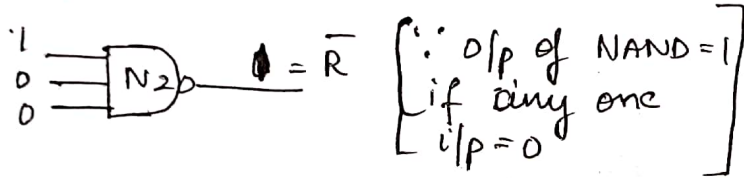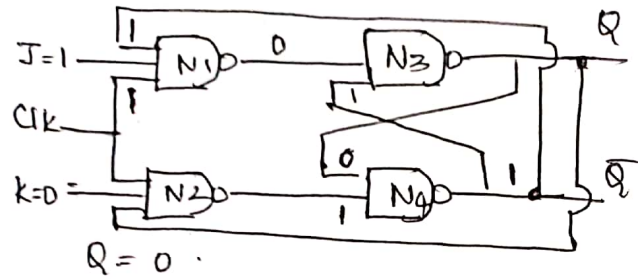





∴ $\bar{S} = 0$ and $\bar{R} = 1$
from $\bar{S} \bar{R}$ latch o/p

$$Q = 1$$

$$\bar{Q} = 0$$

∴ when $J=1, K=0 \Rightarrow Q_{t+1} = 1, \bar{Q}_{t+1} = 0$.

b) $Q = 1$

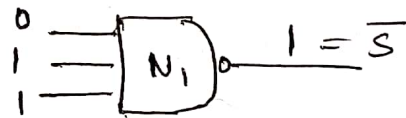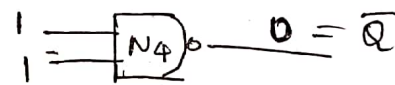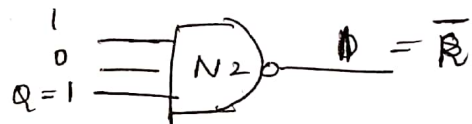
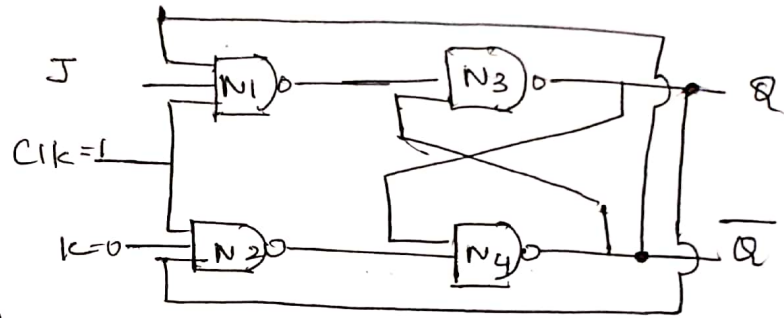


∴ $\bar{S} = 1, \bar{R} = 0$ from $\bar{S} \bar{R}$ latch o/p $Q = 1$ and $\bar{Q} = 0$.


Case 3

$$J=1, K=1, \text{Clk}=\phi$$

assume $Q=0$ and $\bar{Q}=1$

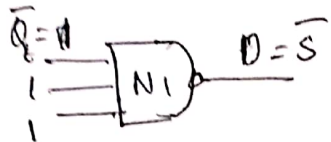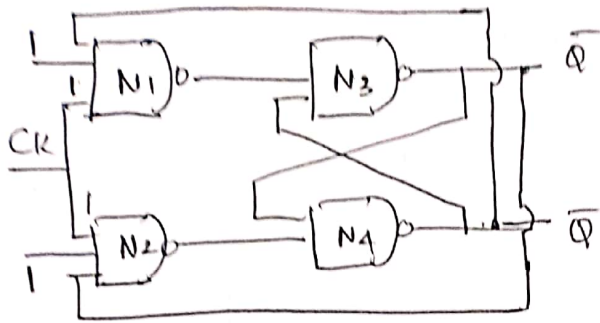


$$\therefore \bar{S}=0, \bar{R}=1$$

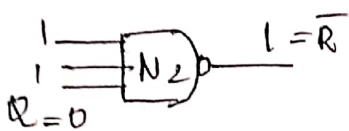

$$\therefore Q_{t+1}=1$$

$$\bar{Q}_{t+1}=0$$

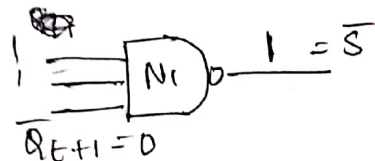

$$Q_{t+1}=0$$



$$Q_{t+1}=1$$

$$\therefore \bar{S}=0, \bar{R}=0$$

$$\therefore Q_{t+2}=0, \bar{Q}_{t+2}=1$$


$\therefore$ the dp switches as follow

$$Q_{t+1} = 0 \ 1 \ 0 \ 1 \ 0 \dots$$


$$\bar{Q}_{t+1} = 1 \ 0 \ 1 \ 0 \ 1 \dots$$

$\therefore$ for the condition $J=1, K=1, \text{Clk}=0$ Q_{t+1} and $\bar{Q}_{t+1}$ switches alternately b/w 0 & 1, This state is known as toggle.


assume $Q=1$ and $\bar{Q}=0$

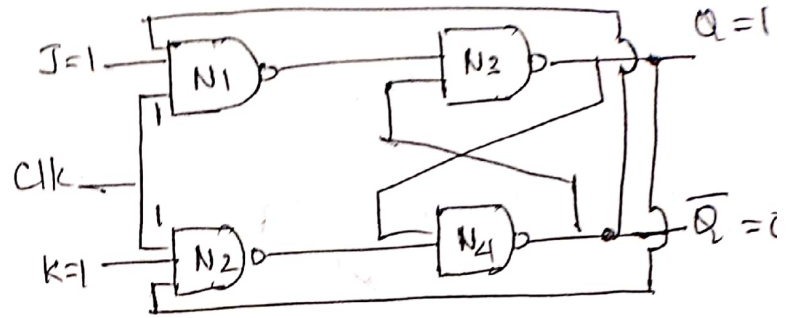

$$Q_t=1 \text{ and } \bar{Q}_t=0.$$

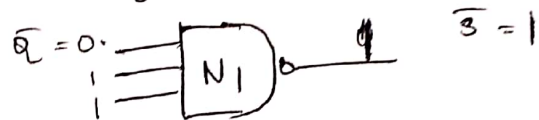


$$\bar{S}=1$$

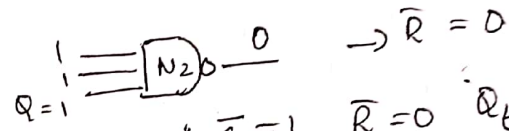


$$\rightarrow \bar{R}=0$$

$$\therefore \bar{S}=1, \bar{R}=0 \quad Q_{t+1}=0$$

$$\bar{Q}_{t+1}=1$$

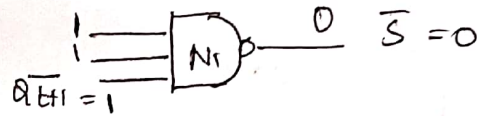

$$Q_{t+1}=1$$

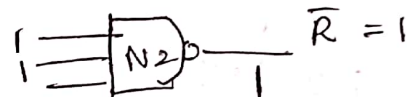

$$Q_{t+1}=0$$

$$\therefore \bar{S} \ \bar{R} = 0 \ 1$$

$$\Rightarrow Q_{t+2}=1, \bar{Q}_{t+2}=0$$







$\therefore$ the ofp switches as follows

$$Q_{t+1} = 0 \ 1 \ 0 \ 1 \dots$$

$$\bar{Q}_{t+1} = 1 \ 0 \ 1 \ 0 \dots$$

let $Q = 1$

let $Q_t = 0$.

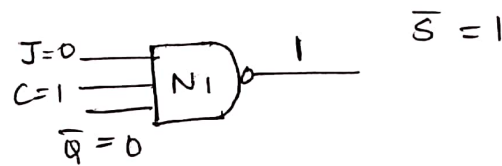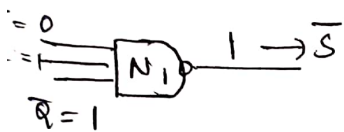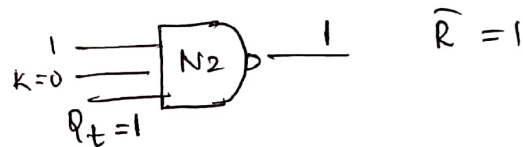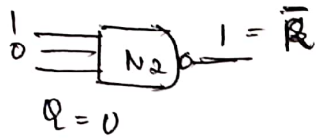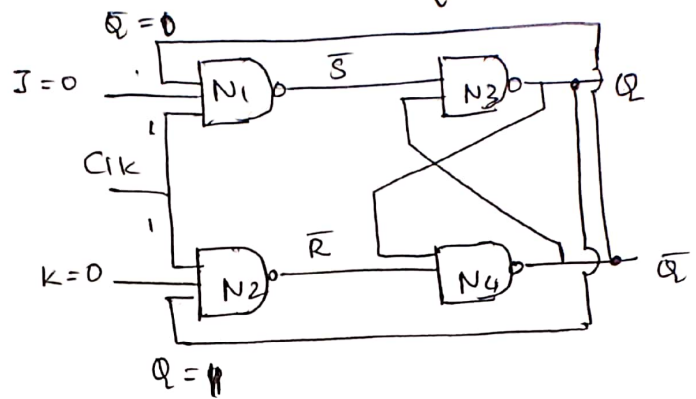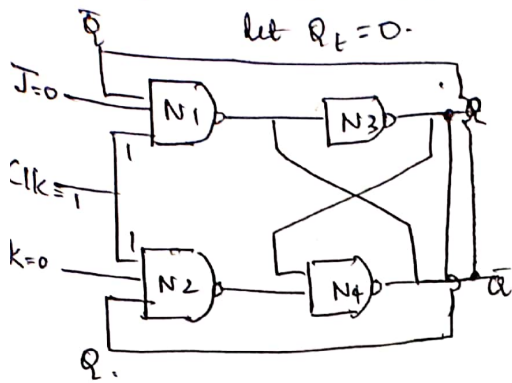

$$\therefore \overline{S} \overline{R} = 11$$

from state table of $\bar{S}\bar{R}$ latch

$$\overline{Q}_{t+1} = \overline{Q}_{t_{\text{th}}} \quad \text{NC}$$

$$Q_{t+1} = Q_t \quad NC$$

$$\therefore \bar{S} \bar{R} = 11$$

$\therefore SR = 11$
from state table of $\overline{S} \overline{R}$ latch

$$Q_{t+1} = Q_t \quad NC$$

$$\overline{Q}_{t+1} = \overline{Q}_t \quad \text{NC.}$$

The above state is known as memory or no charge.

State transition table of JK flip flop

clk	J	K	Q_t	Q_{t+1}	$\overline{Q}_{t+1}$
x	-	-	-	Q_t	$\overline{Q}_t$
↑	0	0	0	NC	NC
			1	NC	NC
↑	0	1	0	0	1
			1	0	1
↑	1	0	0	1	0
			1	0	0
↑	1	1	0	toggle state	
			1		

→ Memory / NC.
memory.