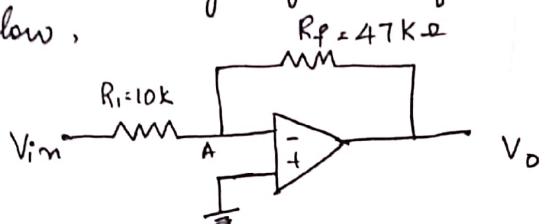


Problems :-

Operational Amplifiers :-

1) Determine the voltage gain of the op-amp circuit shown below.



Soln: The above circuit represents an inverting amplifier.

$$\text{gain } A_f = - \frac{R_f}{R_i} = - \frac{47k}{10k} = -4.7$$

$$A_f = -4.7$$

2) A sine wave of 0.5V peak voltage is applied to an inverting amplifier using $R_i = 10k$ and $R_f = 50k$. It uses the supply voltage of $\pm 12V$. Determine output.

If the amplitude of input sine wave is increased to 5V, what will be the possible output?

Soln: for inverting amplifier

$$\text{gain} = - \frac{R_f}{R_i} = - \frac{50k}{10k} = -5$$

$$\text{if } V_{in} = 0.5V \Rightarrow V_o = V_{in} \times \text{Gain} = 0.5 \times 5 = 12.5V \text{ peak.}$$

\rightarrow o/p is inverted w.r.t. i/p

$$\text{if } V_{in} = 5V$$


$$V_o = V_{in} \times \text{gain} = 5 \times 5 = 25V \text{ peak}$$

But practically o/p saturates at $\pm 12V$

hence portion above $+12$ and below -12 will be clipped.

o/p 180° out of phase w.r.t. i/p

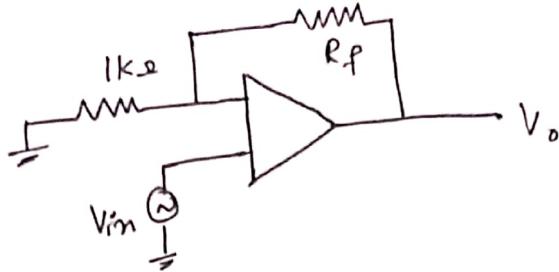3) For the op-amp shown the gain = 61. Determine the appropriate value of feedback resistance R_f




$$\text{Gain} = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i}$$

$$61 = 1 + \frac{R_f}{R_i}$$

$$\therefore R_f = \cancel{R_i} \cdot 60 \times R_i$$

$$\underline{R_f = 60 \text{ k}\Omega}$$

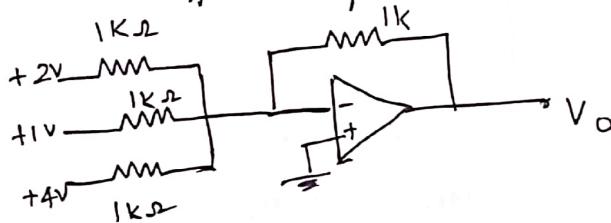4) Determine the o/p voltage in the below figure.



$$V_{out} = -(V_{in1} + V_{in2} + V_{in3}) \frac{R_f}{R_i}$$

$$V_{out} = -(2 + 1 + 4) \frac{1\text{K}}{1\text{K}}$$

$$\boxed{V_{out} = -7\text{V}}$$

5) Design a scaling adder circuit using an op-amp to give the output $V_o = -(3V_1 + 4V_2 + 5V_3)$

Soln:- for an inverting summer

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$


Let $R_f = 120\text{ k}\Omega$

$$\frac{R_f}{R_1} = 3 \Rightarrow R_1 = \frac{120}{3} = 40\text{ k}\Omega$$


$$\frac{R_f}{R_2} = 4 \Rightarrow R_2 = \frac{120}{4} = 30\text{ k}\Omega$$

$$\frac{R_f}{R_3} = 5 \Rightarrow R_3 = \frac{120}{5} = 24\text{ k}\Omega$$

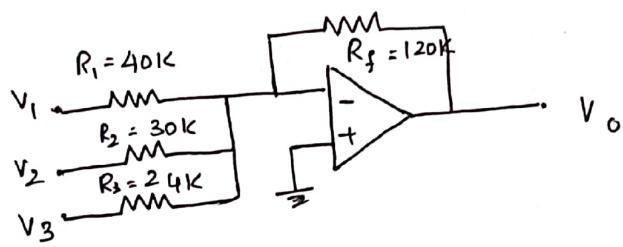∴ the summer circuit is as shown in the figure below,



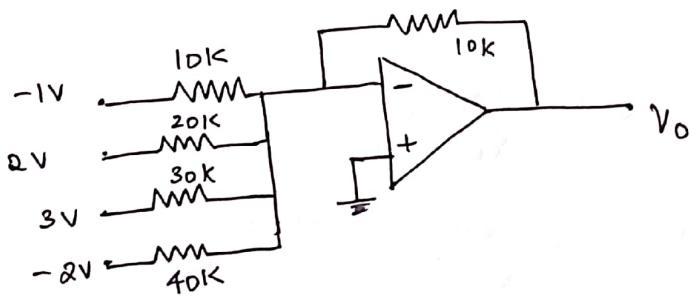6) For the circuit shown determine the output



$$V_0 = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 \right]$$

$$V_0 = - \left[\frac{10 \times 10^3}{10 \times 10^3} \times (-1) + \frac{10 \times 10^3}{20 \times 10^3} \times (2) + \frac{10 \times 10^3}{30 \times 10^3} \times (3) + \frac{10 \times 10^3}{40 \times 10^3} \times (-2) \right]$$

$$V_0 = - \left[-1 + 1 + 1 - 0.5 \right]$$

$$\boxed{V_0 = -0.5\text{ V}}$$

7) Design the op-amp circuit which can give output as

$$V_o = 2V_1 - 3V_2 + 4V_3 - 5V_4$$

Soln: The positive and -ve terms can be added separately using two adder ie., $2V_1 - 3V_2 + 4V_3 - 5V_4 = (2V_1 + 4V_3) - (3V_2 + 5V_4)$

Consider $2V_1 + 4V_3$

$$\text{let } R_f = 100k \text{ then } V_{o1} = - \left[\frac{R_{f1}}{R_1} V_1 + \frac{R_{f2}}{R_2} V_3 \right]$$

$$\frac{R_{f1}}{R_1} = 2 \Rightarrow \frac{100 \times 10^3}{R_1} = 2 \quad \underline{R_1 = 50k\Omega}$$

$$\frac{R_{f2}}{R_2} = 4 \Rightarrow R_2 = \frac{25 \times 10^3}{4} = \underline{25k\Omega}$$

Consider $3V_2 + 5V_4$ let $R_{f2} = 120k\Omega$

$$V_{o2} = - \left[\frac{R_{f2}}{R_2} V_2 + \frac{R_{f3}}{R_4} V_4 \right]$$

$$\text{if } \frac{R_{f2}}{R_2} = 3 \Rightarrow R_2 = \frac{120 \times 10^3}{3} = 60k\Omega$$

$$\frac{R_{f3}}{R_4} = 5 \Rightarrow R_4 = \frac{R_{f3}}{5} = \frac{120 \times 10^3}{5} = \underline{24k\Omega}$$


a subtractor with all resistances of $R = 100k\Omega$ can be used,

therefore o/p of subtractor $V_2 - V_1 = V_{o2} - V_{o1}$



$$V_o = V_{o2} - V_{o1} = -3V_2 - 5V_4 - (-2V_1 - 4V_3)$$

$$V_o = 2V_1 - 3V_2 + 4V_3 - 5V_4$$
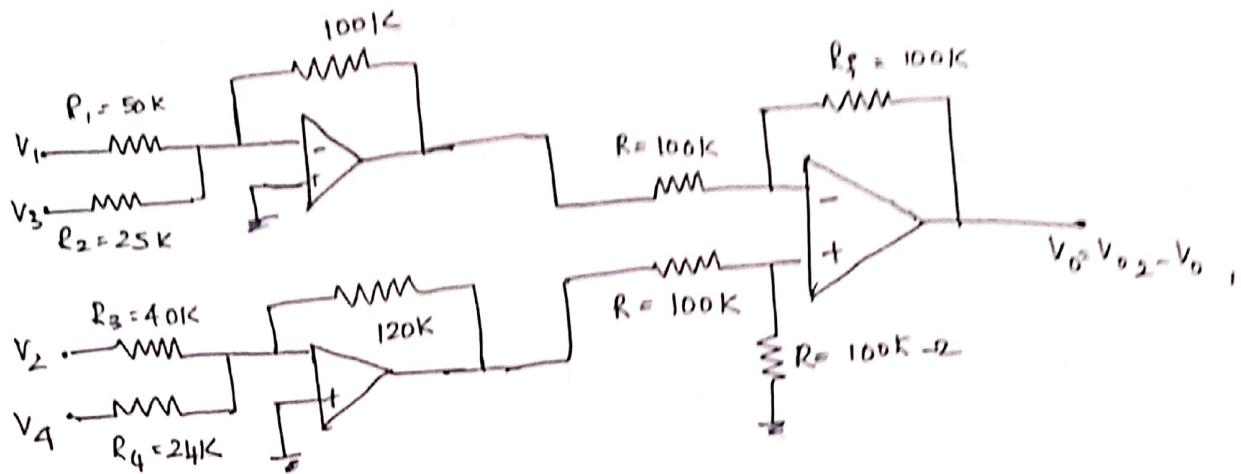
$$\boxed{V_o = 2V_1 - 3V_2 + 4V_3 - 5V_4}$$



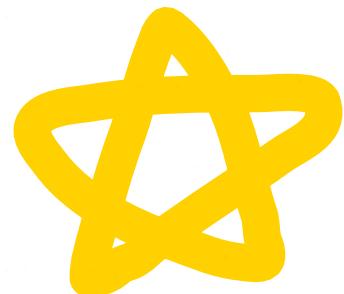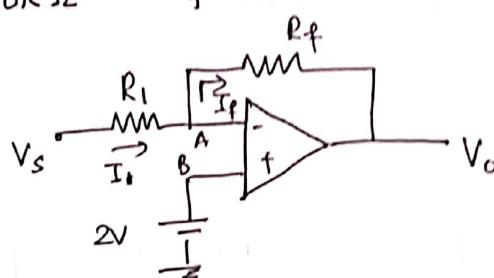8) Consider an ideal op-amps shown in below circuit when $R_1 = 10k\Omega$ $R_f = 30k\Omega$ $V_{GS} = 4V$ find V_o



$$\text{from virtual ground } V_A = V_B = 2V$$

$$I = \frac{V_s - V_A}{R_1} = \frac{4 - 2}{10 \times 10^3} = \frac{2}{10 \times 10^3} \text{ A}$$


$$I = 0.2 \text{ mA}$$

$$I_f = \frac{V_A - V_o}{R_f} = \frac{2 - V_o}{30 \text{ k}\Omega} \quad \text{wkt } I_f = I$$

$$2 - 0.2 \times 10^{-3} \times 30 \text{ k}\Omega = V_o$$

$$V_o = -4V$$

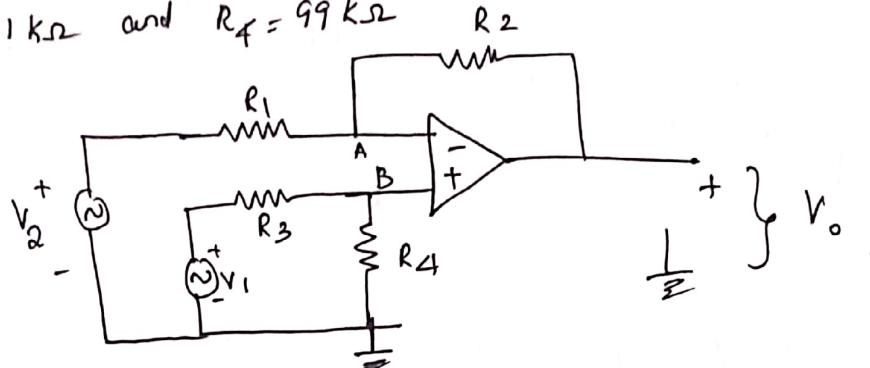9) Consider the operational amplifier circuit shown in figure below, assuming it to be ideal the output voltage is given by $V_o = A_1 V_1 + A_2 V_2$. Find the values of A_1 and A_2 for resistor combination $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_3 = 10.1 \text{ k}\Omega$ and $R_f = 99 \text{ k}\Omega$



Soln: using super position theorem, v_0 can be ~~determined~~ determined.

Let $V_1 = 0$ the o/p is due to i/p V_2

$$\therefore V_o = V_2 \left[-\frac{R_2}{R_1} \right] \rightarrow \text{inverting amplifier}$$

Let $V_2 = 0$, the op is only due to $i/p V_1 \rightarrow$ non-inverting amplifier

$$V_B = V_1 \left(\frac{1 + R_f}{R_1} \right)$$

$$V_B = V_I \left[\frac{1 + R_2}{R_1} \right] - V_I$$

the potential at point B is i.e., V_B is given by .

$$V_B = \frac{V_1 R_4}{R_3 + R_4}$$

$$\therefore V_{o_1} = V_B \left[1 + \frac{R_2}{R_1} \right] = \frac{V_1 R_4}{R_3 + R_4} \left[1 + \frac{R_2}{R_1} \right]$$

combining both,

$$V_o = V_{o1} + V_{o2} = \frac{V_1 R_4}{R_3 + R_4} + \frac{V_1 R_4}{(R_3 + R_4) R_1} + V_2 \left[-\frac{R_3}{R_1} \right]$$

$$V_o = V_1 \left[\frac{R_4}{R_3 + R_4} + \frac{R_2 R_4}{(R_3 + R_4) R_1} \right] + V_2 \left[\frac{-R_2}{R_1} \right]$$

$$V_o = V_1 \frac{R_4}{R_3 + R_4} \left[1 + \frac{R_2}{R_1} \right] + V_2 \left[\frac{-R_2}{R_1} \right]$$

Comparing the above eqn with given eqn,

$$V_o = V_1 A_1 + V_2 A_2$$

$$\text{we get, } A_1 = \frac{R_4}{R_3 + R_4} \left[1 + \frac{R_2}{R_1} \right]$$

$$A_1 = \frac{99 \times 10^3}{109.1 \times 10^3} \left[1 + \frac{160 \times 10^3}{10 \times 10^3} \right]$$

$$A_1 = \frac{99}{109.1} \left[\frac{110}{10} \right]$$

$$\underline{\underline{A_1 = 9.9817}}$$

$$A_2 = -\frac{R_2}{R_1} = -10$$

10) A differential amplifier has a typical common mode gain of 35dB and CMRR of 72dB. Find the output voltage (V_o) when input voltages are 0.16mV and 0.18mV.

$$\text{Soh: } \text{CMRR} = \frac{A_d}{A_c}$$

$$20 \log A_d = 35 \text{ dB}$$

$$A_d = \left(\frac{35}{20} \right)_{10}$$

$$\underline{\underline{A_d = 56.23}}$$

$$A_c = 56.23$$

$$\text{CMRR} = 72 \text{ dB} \Rightarrow 20 \log x = 72 \text{ dB}$$

$$x = 3981 = \text{CMRR}$$

$$A_d = \text{CMRR} \times A_c = 3981 \times 56.23 = 223855$$

$$= 2.23855 \times 10^5$$

V_c = common mode signal

$$V_c = \frac{V_1 + V_2}{2} = \frac{1}{2} [0.18 + 0.16] \times 10^3$$

$$V_c = 0.17 \text{ mV}$$

V_d = difference mode signal

$$V_d = (0.18 \text{ V} - 0.16 \text{ V}) = 0.02 \text{ mV}$$

$$V_d = 0.02 \text{ mV}$$

$$V_o = A_c V_c + A_d V_d = (56.23) (0.17 \text{ mV}) + (0.02 \text{ m})(2.23 \times 10^5)$$

$$\underline{\underline{V_o = 4.47 \text{ V}}}$$

A) An amplifier has mid band gain of 125 and BW of 250 kHz. i) If 4% negative feedback is introduced find the new bandwidth & gain.
 ii) If BW is restricted to 1 MHz find feedback ratio.

Soln: Given $A_v = 125$ $B_W = 250K$ $\beta = 0.04$

$$A_{vf} = \frac{A}{1 + \beta A} = \frac{125}{1 + 0.04 \times 125} = 0.83$$

$$B_{wf} = B_W (1 + A \beta) = 250 \times 10^3 (1 + 0.04 \times 125) \\ = 1.5 \text{ MHz}$$

$$B_W = 1 \text{ MHz}$$

$$1 \times 10^6 = B_W (1 + A \beta) \\ = 250 \times 10^3 (1 + 125 \times \beta)$$

$$\underline{\underline{\beta = 0.024}}$$

①