

⑤ Design a scaling adder circuit using an op-amp to give the output $V_o = -(3V_1 + 4V_2 + 5V_3)$

Ans For an inverting summer

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

Let $R_f = 120 \text{ k}\Omega$

$$\frac{R_f}{R_1} = 3 \Rightarrow R_1 = R_f / 3 = 120 \text{ k}\Omega / 3$$


$$\underline{\underline{R_1 = 40 \text{ k}\Omega}}$$

$$\frac{R_f}{R_2} = 4 \Rightarrow R_2 = R_f / 4 = 120 \text{ k}\Omega / 4$$


$$\underline{\underline{R_2 = 30 \text{ k}\Omega}}$$

$$\frac{R_f}{R_3} = 5 \Rightarrow R_3 = R_f / 5 = 120 \text{ k}\Omega / 5$$
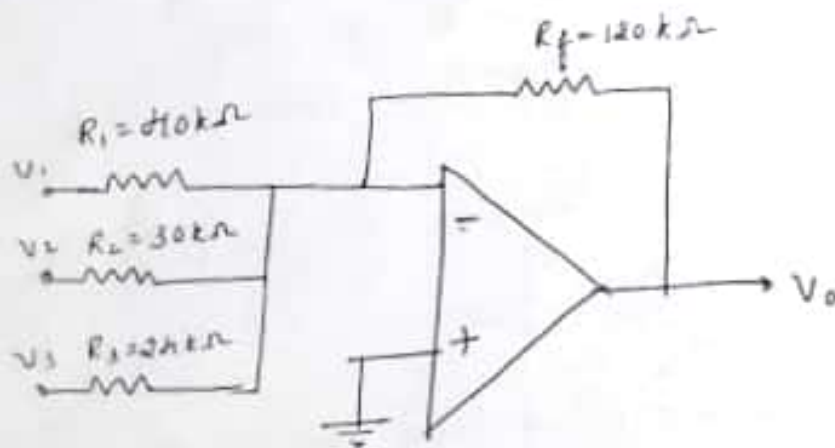
$$\underline{\underline{R_3 = 24 \text{ k}\Omega}}$$



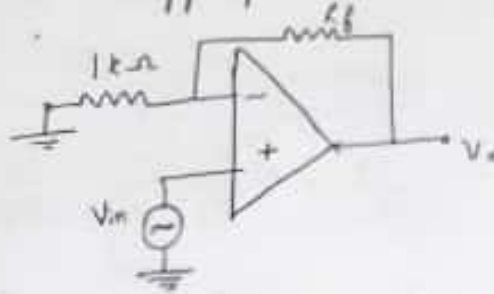- 2) For op-amp shown in figure the gain required is 61. Determine the appropriate value of feedback resistance R_f .



From figure: $R_i = 1k\Omega$ and gain required is 61

$$\text{Gain} = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i}$$


$$61 = 1 + \frac{R_f}{R_i}$$

$$\frac{R_f}{R_i} = 60$$

$$R_f = 60 \times 1k\Omega = 60k\Omega$$

$$\boxed{R_f = 60k\Omega}$$

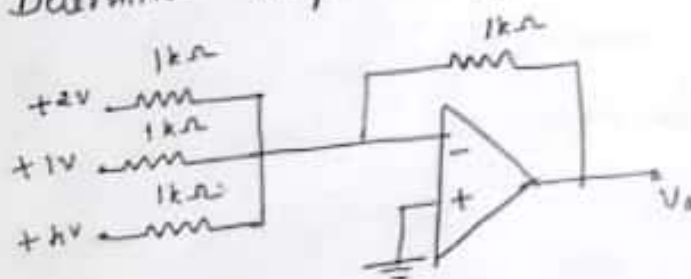- 3) Determine output voltage in below figure



$$V_{out} = -(V_{in1} + V_{in2} + V_{in3}) \frac{R_f}{R_i}$$

$$= -(2 + 1 + 4) \frac{1k\Omega}{1k\Omega}$$

$$\boxed{V_{out} = -7V}$$

- 4) Design the value of an inductor to be used in Colpitts oscillator to generate a frequency of 10 MHz. The circuit is used capacitor $C_1 = 100 \text{ pF}$ and $C_2 = 50 \text{ pF}$.

Given

$$C_1 = 100 \text{ pF}$$

$$C_2 = 50 \text{ pF}$$

$$f = 10 \text{ MHz}$$

$$L = ?$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = 33.33 \text{ pF}$$

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}} \Rightarrow L = \frac{1}{(2\pi f)^2 C_{eq}}$$

$$f = \underline{\underline{7.6 \mu\text{H}}}$$

- 5) Calculate frequency of oscillations of Hartley oscillator having $L_1 = 0.5 \text{ mH}$, $L_2 = 1 \text{ mH}$ and $C = 0.2 \mu\text{F}$.

Given

$$L_1 = 0.5 \text{ mH}$$

$$L_2 = 1 \text{ mH}$$

$$C = 0.2 \mu\text{F}$$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$L_{eq} = L_1 + L_2 = 1.5 \text{ mH}$$

$$f = \underline{\underline{9.12 \text{ kHz}}}$$

- 6) In a Hartley oscillator $L_1 = 20 \mu\text{H}$, $L_2 = 2 \text{ mH}$ and C is variable. Find range of C if frequency is to be varied from 1 MHz to 2.5 MHz. Neglect mutual inductance.

Given

$$L_1 = 20 \mu\text{H}$$

$$L_2 = 2 \text{ mH}$$

$$f_1 = 1 \text{ MHz}$$

$$f_2 = 2.5 \text{ MHz}$$

$$L_{eq} = L_1 + L_2 = \underline{\underline{2.02 \text{ mH}}}$$

$$f_1 = 1 \text{ MHz} \quad f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$C_1 = \frac{1}{(2\pi f_1)^2 L_{eq}} = 12.539 \text{ pF}$$


$$f_2 = 2.5 \text{ MHz}$$

$$C_2 = \frac{1}{(2\pi f_2)^2 L_{eq}} = \underline{\underline{2.006 \text{ pF}}}$$

(59)

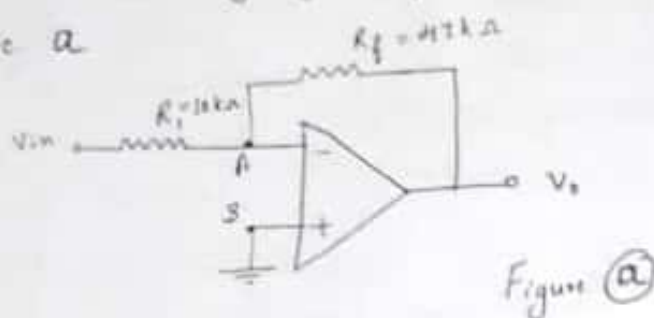Problems

- ① Determine the voltage gain of the op-amp circuit shown in figure a



Given

$$R_i = 10k\Omega$$

$$R_f = 47k\Omega$$

The circuit is inverting amplifier.

$$\text{Gain} = \frac{V_o}{V_{in}} = -\frac{R_f}{R_i} = -\frac{47k\Omega}{10k\Omega} = -4.7$$

- ② A sine wave of 0.5V peak voltage is applied to an inverting amplifier using $R_i = 10k\Omega$ and $R_f = 50k\Omega$. It uses the supply voltage of $\pm 12V$. Determine output

If now the amplitude of input sine wave is increased to 5V, what will be the possible output?

Case 1: For inverting amplifier, $\text{Gain} = -\frac{R_f}{R_i} = -\frac{50k\Omega}{10k\Omega} = -5$

If $V_{in} = 0.5V \Rightarrow V_o = V_{in} \times \text{Gain} = 0.5 \times 5 = \underline{2.5V \text{ peak}}$

The output waveform is inverted i.e. inverted with respect to input.

Case 2: If $V = 5V$

$$V_o = V_{in} \times \text{Gain} = 5 \times 5 = 25V \text{ peak}$$

But practically op-amp output saturates at $\pm 12V$ as i.e., at supply voltage used. So portion above $+12V$ and $-12V$ will be clipped and output will be 180° phase shifted w.r.t input.

Problems

- 1) In a RC phase shift oscillator, the phase shift n/w uses resistances each of $4.7k\Omega$ and capacitors each of $0.47\mu F$ find frequency of oscillation.

Given

$$R = 4.7k\Omega$$

$$C = 0.47\mu F$$

$$f = \frac{1}{2\pi\sqrt{6}RC}$$

$$f = \frac{1}{(2\pi)(\sqrt{6})(4.7 \times 10^3)(0.47 \times 10^{-6})}$$

$$\underline{\underline{f = 29.413 \text{ Hz}}}$$

Design RC phase shift oscillator using CE amplifier for frequency 900 kHz .

$$f = 900 \text{ kHz}$$

$$\text{Let } C = 1 \mu F$$

$$f = \frac{1}{2\pi\sqrt{6}RC}$$

$$R = \frac{1}{(2\pi)\sqrt{6}(900 \times 10^3)(1 \times 10^{-6})}$$

$$\underline{\underline{R = 72.1941 \text{ k}\Omega}}$$

In a Colpitts oscillator the desired frequency is 500 kHz estimate L , assuming $C = 1000 \text{ pF}$

For Colpitts oscillator $C_1 = C_2 = C = 1000 \text{ pF}$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = 500 \text{ pF}$$

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}} \Rightarrow L = \frac{1}{(2\pi f)^2 C_{eq}}$$

$$\underline{\underline{L = 202.64 \mu H}}$$