

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

August 2023 Semester End Make-Up Examinations

Programme: B.E.

Branch: Common to all Branches

Course Code: 22EE1ESEEE

Course: ELEMENTS OF ELECTRICAL ENGINEERING

Semester: I

Duration: 3 hrs.

Max Marks: 100

Date: 11.08.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1 a) State and explain Ohm's law, mention its limitations. 05
 b) With neat sketch, explain the construction of the various parts of a DC motor. 08
 c) Find currents in the battery, the current in each branch and potential difference across AB in the network shown in figure 1. 07

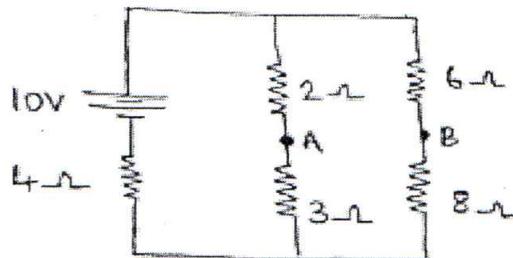


Figure 1

OR

2 a) State and explain Kirchhoff's laws. 05
 b) Explain the characteristics of a DC series motor
 (i) Torque V/S Armature current
 (ii) Speed V/S Armature current. 08
 c) A DC shunt motor runs at 750 rpm from 250V supply and taking a full load line current of 60A, its armature resistance is 0.4Ω and field resistance of 125Ω . Assuming 2 volt brush drop and negligible armature reaction effect, find the no-load speed for a no-load current of 6A. 07

UNIT - II

3 a) Define RMS value of a sinusoidal varying alternating current and find its relation with its maximum value. 05
 b) Derive an equation for the power consumed by an RL series circuit. Draw the waveforms of voltage, current and power. 08
 c) A resistor of 100Ω is connected in series with a $50\ \mu\text{F}$ capacitor to a supply of 200V, 50Hz. Find (i) the impedance (ii) the current (iii) the power factor (iv) the phase angle (v) the voltage across resistor and capacitor. 07

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.