

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## February / March 2024 Semester End Main Examinations

**Programme: B.E.**

**Semester: I / II**

**Branch: Common to all Branches**


**Duration: 3 hrs.**

**Course Code: 22EE1ESIEE / 22EE2ESIEE**


**Max Marks: 100**

**Course: Introduction to Electrical Engineering**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.
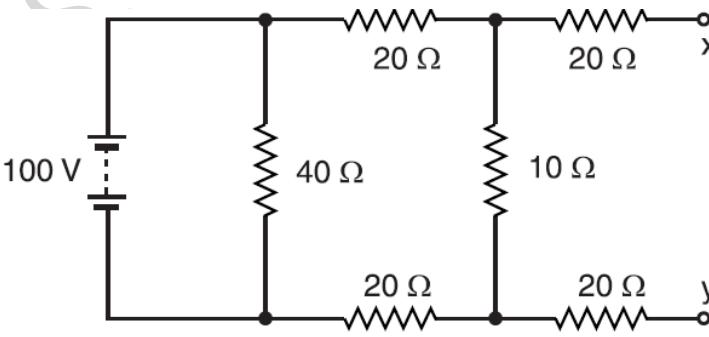
<b>UNIT - I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>
1	a)	List the differences between conventional and non-conventional sources of energy.	<i>CO1</i>	<i>PO1</i>	<b>06</b>
	b)	With a neat schematic diagram, explain the hydroelectric power generation.	<i>CO1</i>	<i>PO1</i>	<b>06</b>
	c)	Wheatstone bridge ABCD has the following details; $AB = 1000 \Omega$ ; $BC = 100 \Omega$ ; $CD = 450 \Omega$ ; $DA = 5000 \Omega$ . A Galvanometer of resistance $500 \Omega$ is connected between B and D. A 4.5 V battery of negligible resistance is connected between A and C with A positive. Apply Kirchhoff's laws and find the magnitude and direction of Galvanometer current.	<i>CO1</i>	<i>PO1</i>	<b>08</b>
<b>UNIT - II</b>					
2	a)	Calculate the power which would be dissipated in a $50 \Omega$ resistor connected across xy in the network shown in Fig 2a using Thevenin's theorem	<i>CO2</i>	<i>PO2</i>	<b>08</b>
					
		Fig.2a			
	b)	State and Explain Faraday's Laws of Electromagnetic induction	<i>CO1</i>	<i>PO1</i>	<b>06</b>
	c)	A solenoid with 900 turns has a total flux of $1.33 \times 10^{-7}$ Wb through its air core when the coil current is 100 mA. If the flux takes 75 ms to grow from zero to its maximum level, calculate the inductance of the coil. Also, calculate the induced EMF in the coil during the flux growth.	<i>CO2</i>	<i>PO2</i>	<b>06</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
Revealing of identification, appeal to evaluator will be treated as malpractice.
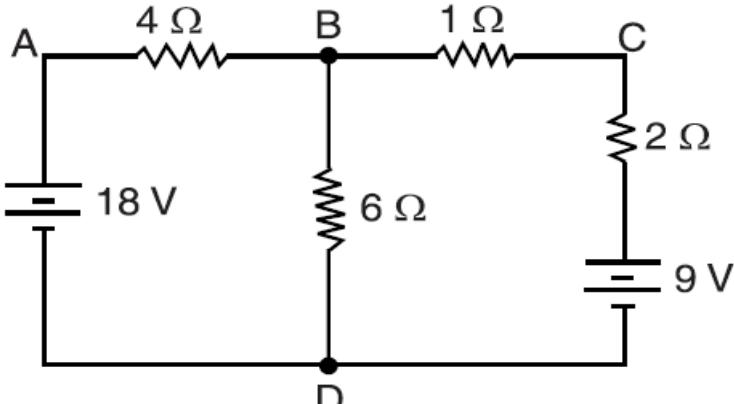
<b>OR</b>					
3	a)	Find the currents in the various branches of the circuit shown in Fig 3a using superposition theorem	CO2	PO2	<b>08</b>
			2023-24		
Fig.3a					
<b>UNIT - III</b>					
4	a)	With a neat sketch of voltage and current waveforms and phasor diagram, explain the behavior of RLC circuit for AC Voltage.	CO2	PO2	<b>10</b>
b) Define the terms with expressions:			CO1	PO1	<b>10</b>
a) RMS value. b) Average value. c) Phase angle. d) Amplitude value. e) Form Factor.					
<b>UNIT - IV</b>					
5	a)	Derive the EMF equation of a transformer.	CO2	PO2	<b>07</b>
b) A single phase 100 kVA transformer has 500 turns in the primary and 1200 turns in the secondary. The cross-sectional area of the core is 80 sq. cm. If the primary winding is connected to a 50 Hz supply at 500 V, calculate (i) Peak flux-density, and (ii) Voltage induced in the secondary (iii) Primary and Secondary currents.			CO2	PO2	<b>06</b>
c) Obtain an expression for armature torque in a DC motor.			CO2	PO2	<b>07</b>
<b>OR</b>					
6	a)	With a neat sketch explain the construction and working of a DC motor.	CO1	PO1	<b>07</b>
b) A 200-kVA transformer has an efficiency of 98% at full load. If the maximum efficiency occurs at three quarters of its full-load,			CO2	PO2	<b>08</b>

		calculate the efficiency at half load. Assume negligible magnetizing current and p.f. 0.8 at all loads.																																											
	c)	A DC series motor takes an armature current of 110 A at 480 V. The armature circuit and series field resistance together is $0.2 \Omega$ . The machine has 6-poles and the armature is lap-connected with 864 conductors. The flux per pole is 0.05 Wb. Calculate: (i) Speed and (ii) Gross torque developed by the armature.	CO2	PO2	<b>05</b>																																								
		<b>UNIT - V</b>																																											
7	a)	List the demerits of fuse and with a neat sketch explain the working principle of Miniature Circuit Breaker (MCB).	CO3	PO6	<b>06</b>																																								
	b)	A household has different electrical appliances which run for a certain duration in a day.  <table border="1"> <thead> <tr> <th>Sl. No</th> <th>Appliance</th> <th>Power rating (W)</th> <th>Quantity</th> <th>No. of Hours per day</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Water Geyser</td> <td>2000</td> <td>2</td> <td>1</td> </tr> <tr> <td>2</td> <td>TV</td> <td>100</td> <td>1</td> <td>10</td> </tr> <tr> <td>3</td> <td>Lamps</td> <td>40</td> <td>5</td> <td>6</td> </tr> <tr> <td>4</td> <td>Fan</td> <td>60</td> <td>2</td> <td>10</td> </tr> <tr> <td>5</td> <td>Laptop</td> <td>150</td> <td>1</td> <td>10</td> </tr> <tr> <td>6</td> <td>Fridge</td> <td>500</td> <td>1</td> <td>2</td> </tr> <tr> <td>7</td> <td>Washing Machine</td> <td>1000</td> <td>1</td> <td>1</td> </tr> </tbody> </table> If a 3 kW Energy Meter is installed in the house, cost/kW is Rs.100/- and cost/unit is Rs.7/-. Calculate the electricity bill for the month of Jan 2023.	Sl. No	Appliance	Power rating (W)	Quantity	No. of Hours per day	1	Water Geyser	2000	2	1	2	TV	100	1	10	3	Lamps	40	5	6	4	Fan	60	2	10	5	Laptop	150	1	10	6	Fridge	500	1	2	7	Washing Machine	1000	1	1	CO3	PO6	<b>08</b>
Sl. No	Appliance	Power rating (W)	Quantity	No. of Hours per day																																									
1	Water Geyser	2000	2	1																																									
2	TV	100	1	10																																									
3	Lamps	40	5	6																																									
4	Fan	60	2	10																																									
5	Laptop	150	1	10																																									
6	Fridge	500	1	2																																									
7	Washing Machine	1000	1	1																																									
	c)	With a neat block diagram explain the operation of Electric Vehicle.	CO2	PO2	<b>06</b>																																								

\*\*\*\*\*