

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## April 2025 Semester End Make-Up Examinations

**Programme: B.E.**

**Branch: Common to all Branches**

**Course Code: 22EE1ESIEE**



**Course: Introduction to Electrical Engineering**

**Semester: I**



**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

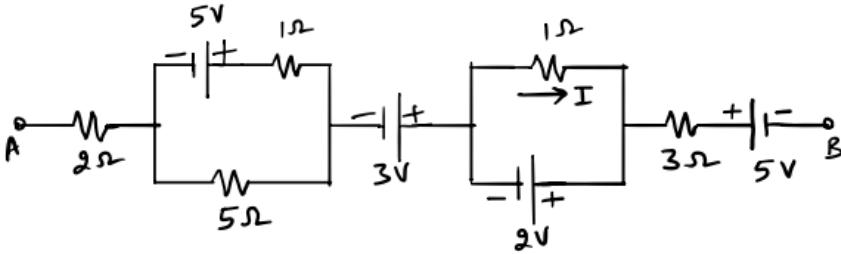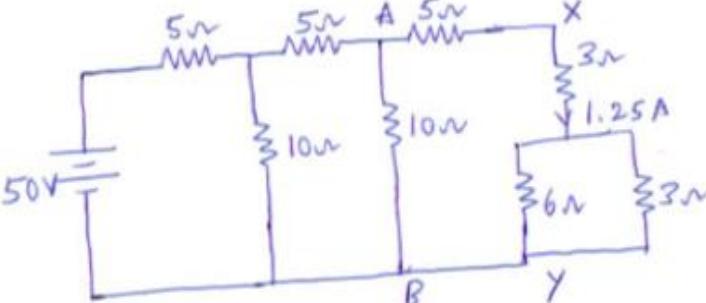UNIT - I			CO	PO	Marks
1	a)	Explain construction and working of nuclear power plant, with neat diagram.	CO1	PO1	<b>08</b>
	b)	For the given network shown in Fig. 1(b) find, current (I) and $V_{AB}$ using Kirchhoff's laws.	CO2	PO1	<b>08</b>
		 <p>Fig. 1(b)</p>			
	c)	State Ohms law and list its limitations.	CO1	PO1	<b>04</b>
OR					
2	a)	Explain the working of Hydel Power plant with a neat diagram.	CO1	PO1	<b>08</b>
	b)	Determine the current supplied by the source and voltage across 3 Ohm resistor. Also determine the equivalent resistance across the terminals AB.	CO2	PO1	<b>07</b>
		 <p>Fig 2b)</p>			
	c)	State and explain KVL and KCL	CO1	PO1	<b>05</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.
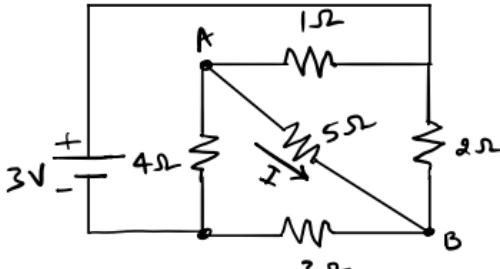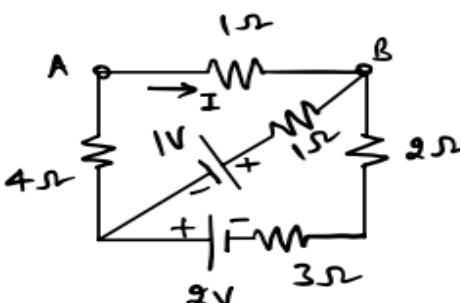
<b>UNIT - II</b>					
3	a)	Derive an expression for energy stored in an Inductor. Also derive for co-efficient of coupling.	CO1	PO1	<b>08</b>
	b)	For the circuit shown in Fig 3(b), find current (I) in branch AB, using Thevenin's theorem	CO2	PO2	<b>08</b>
					
		Fig. 3(b)			
	c)	Differentiate between statically induced EMF and dynamically induced EMF.	CO1	PO1	<b>04</b>
<b>OR</b>					
4	a)	State Faraday's laws and Lenz's law of electromagnetic induction.	CO1	PO1	<b>06</b>
	b)	For the circuit shown in Fig 4(b), find current (I) in branch AB, using superposition theorem.	CO2	PO2	<b>08</b>
					
		Fig. 4(b)			
	c)	Two coupled coils of self-inductances 0.8 H and 0.20 H have a co-efficient of coupling 0.9. Find (i) Mutual inductance. (ii) $N_1/N_2$ .	CO2	PO2	<b>06</b>
<b>UNIT - III</b>					
5	a)	How current behaves when a pure sinusoidal voltage of $V = V_m \sin \omega t$ is applied across a series RLC circuit. Explain with proper phasor diagram and waveforms.	CO2	PO2	<b>10</b>
	b)	Define the terms with expressions: <ol style="list-style-type: none"> <li>RMS value.</li> <li>Average value.</li> <li>Phase angle.</li> <li>Amplitude value.</li> <li>Form Factor.</li> </ol>	CO1	PO1	<b>10</b>
		<b>OR</b>			
6	a)	Define the following with respect to alternating current: <ol style="list-style-type: none"> <li>Frequency</li> <li>Time period</li> <li>phase</li> <li>phase difference</li> <li>peak factor</li> </ol>	CO1	PO1	<b>10</b>

	b)	Explain the nature of current in a series RL, pure resistive and pure inductive single phase AC circuit	CO1	PO1	10																																					
		<b>UNIT – IV</b>																																								
7	a)	Derive condition for maximum efficiency of a transformer.	CO2	PO2	06																																					
	b)	A 200 kVA transformer has efficiency of 98% at full load upf lagging. If maximum efficiency occurs at $3/4^{\text{th}}$ of its full load 0.8 pf, calculate efficiency at half of its full load 0.8 pf.	CO2	PO2	08																																					
	c)	With necessary circuit and equations, explain different types of DC motors.	CO1	PO1	06																																					
		<b>OR</b>																																								
8	a)	Derive torque equation of a DC motor.	CO1	PO1	06																																					
	b)	A 240 V, 4 pole DC shunt motor running at 1000 rpm delivers 5 kW with an armature current of 50 A and field current of 1 A. Armature winding is wave connected and has 540 conductors. Armature resistance is 0.1 ohms and drop at each brush is 1 V. Find a) Gross torque. b) Shaft torque. c) Useful flux/pole. d) Rotational losses.	CO2	PO2	08																																					
	c)	How transformers are classified based on construction of core. Differentiate with neat sketch.	CO1	PO1	06																																					
		<b>UNIT - V</b>																																								
9	a)	With block diagram, explain working of Electric Vehicle.	CO1	PO1	06																																					
	b)	A household has different electrical appliances which run for a certain duration in a day.	CO4	PO6	08																																					
		<table border="1"> <thead> <tr> <th>Sl. No</th> <th>Appliance</th> <th>Power rating (W)</th> <th>Quantity</th> <th>No. of Hours per day</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Heater</td> <td>1500</td> <td>1</td> <td>2</td> </tr> <tr> <td>2</td> <td>Fridge</td> <td>200</td> <td>1</td> <td>2</td> </tr> <tr> <td>3</td> <td>Washing Machine</td> <td>500</td> <td>1</td> <td>2</td> </tr> <tr> <td>4</td> <td>Mixer</td> <td>400</td> <td>1</td> <td>0.5</td> </tr> <tr> <td>5</td> <td>Lighting Load</td> <td>10</td> <td>8</td> <td>4</td> </tr> <tr> <td>6</td> <td>TV</td> <td>60</td> <td>1</td> <td>3</td> </tr> <tr> <td>7</td> <td>Fan</td> <td>60</td> <td>4</td> <td>3</td> </tr> </tbody> </table> <p>If a 5 kW Energy Meter is installed in the house, cost/kW is Rs. 50 and cost/unit for first 100 units is Rs 7/- and remaining units is Rs 10/-. Calculate the electricity bill for the month of Feb 2025.</p>				Sl. No	Appliance	Power rating (W)	Quantity	No. of Hours per day	1	Heater	1500	1	2	2	Fridge	200	1	2	3	Washing Machine	500	1	2	4	Mixer	400	1	0.5	5	Lighting Load	10	8	4	6	TV	60	1	3	7	Fan
Sl. No	Appliance	Power rating (W)	Quantity	No. of Hours per day																																						
1	Heater	1500	1	2																																						
2	Fridge	200	1	2																																						
3	Washing Machine	500	1	2																																						
4	Mixer	400	1	0.5																																						
5	Lighting Load	10	8	4																																						
6	TV	60	1	3																																						
7	Fan	60	4	3																																						
	c)	What is earthing? explain plate earthing with a neat sketch.																																								
		<b>OR</b>																																								
10	a)	Discuss the precautions to be taken to avoid electric shock.																																								
	b)	Discuss plate earthing with a neat diagram.																																								
	c)	Explain the working of fuse and define the following: i) Rated current of fuse ii) fusing current iii) fusing factor.																																								

\*\*\*\*\*