

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## May 2023 Semester End Main Examinations

**Programme: B.E.**

**Branch: Common to all Branches**

**Course Code: 18EE1ESELE / 18EE2ESELE**

**Course: Elements of Electrical Engineering**

**Semester: I / II**

**Duration: 3 hrs.**


**Max Marks: 100**

**Date: 16.05.2023**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

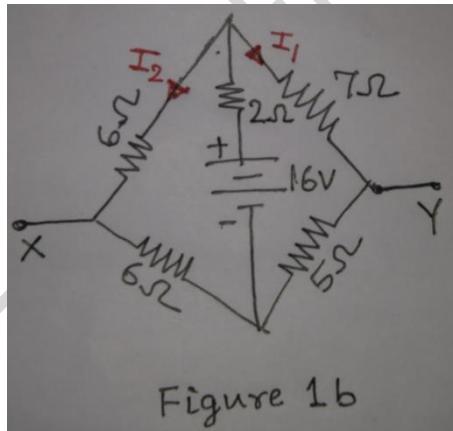1. a) State and prove Superposition theorem for dc circuit. **07**  
b) Determine  $I_1$ ,  $I_2$  and  $V_{XY}$  for the network shown in figure 1b using Kirchhoff's laws. **05**



c) With the help of neat sketch, name the parts of a dc machine and function of each part. **08**

### OR

2. a) Deduce the expression for armature torque in a dc motor. **06**  
b) A 4 – Pole, 500V DC Shunt motor has 720 wave connected armature conductors. The full load armature current is 60A and flux/pole is 0.03wb. Armature resistance is  $0.2\Omega$  and contact drop is 1V per brush. Calculate the full load speed of motor. **06**  
c) Compute : **08**  
(i) the current at node D and its direction  
(ii) all the branch currents  
(iii) voltage across A & D terminals for the circuit shown in figure 2c.

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

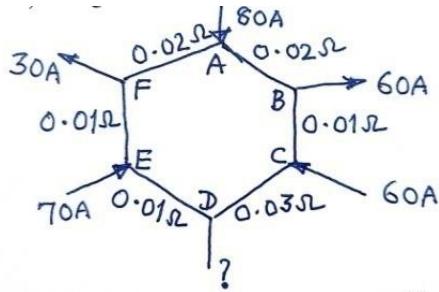


Figure 2 c

## UNIT - II

3. a) Derive the expression for average value and effective value of an sinusoidal alternating current in terms of its maximum value. **07**

b) A voltage of  $v=200 \sin(377t-\pi/2)$ volts is applied to an ac circuit and the current in the circuit is  $i=20\sin(377t-\pi/4)$  Amperes. Determine (i) Impedance (ii) frequency (iii) circuit constants (iv) power factor (v) active power (vi) reactive power. **07**

c) Show that in a pure inductive circuit, the average power consumed is zero. Sketch the waveforms of voltage, current & power **06**

## UNIT - III

4. a) With the help of circuit diagram & phasor diagram, derive the relationship between the line & phase values of voltage & current in 3 phase star connected load. **07**

b) With sketches distinguish between salient pole & non salient pole rotors. **07**

c) A three phase ,50Hz,16 pole alternator with star connected armature winding has 144 slots with 10 conductors/slot. The flux /pole is 0.03 weber. Take winding factor of 0.96, Compute i) Synchronous speed ii) Phase emf and iii) Line emf. **06**

## OR

5. a) Derive an expression for phase emf & line emf of a three-phase star connected alternator considering pitch factor & distribution factor. **07**

b) With the help of circuit diagram and phasor diagram, show that two wattmeter's are sufficient to measure i) active power ii) power factor in a balanced star connected load. **07**

c) Three identical impedances each of  $(6+j8) \Omega$  are connected in star across 400V,3phase, 50Hz ac supply. Determine (i) phase current (ii) phase power factor (iii) real power and (iv) apparent power. **06**

## UNIT - IV

6. a) Explain principle of operation of a single-phase transformer and derive the emf equation. **06**

b) A 25 kVA, single phase 11000/415V, 50Hz transformer has 80 turns on the secondary. Determine (i) the number of primary turns (ii) maximum value of core flux (iii) the rated primary and secondary currents. **06**

c) Deduce the condition for maximum efficiency of a single-phase transformer and hence obtain equation for maximum efficiency at unity power factor. **08**

## UNIT - V

7. a) With the help of neat rotors of sketches, compare the features of rotors of three phase induction motors. **06**

b) A 12 pole, 3 phase alternator is coupled to an engine running at 500rpm. It supplies an induction motor, which has a full load speed of 1440rpm. Find (i) the percentage slip (ii) the number of poles of the motor (iii) frequency of rotor current at full load. **06**

c) What is earthing? Why earthing is needed? With a neat sketch, explain the pipe earthing method. **08**

\*\*\*\*\*