

U.S.N.

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

January / February 2025 Semester End Main Examinations

Programme: B.E.

Branch: Electrical and Electronics Engineering

Course Code: 22EE3PCECT




Course: Electrical Circuit Theory





Semester: III




Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

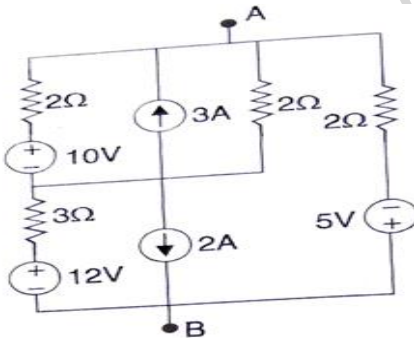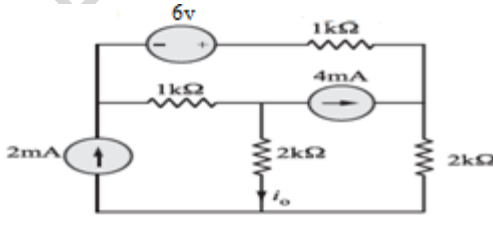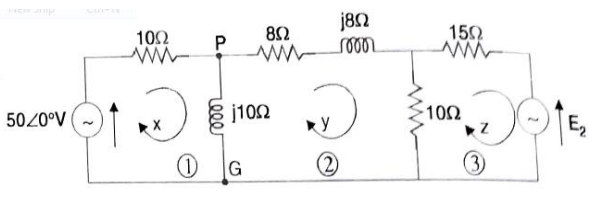Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.			UNIT - I	CO	PO	Marks
	1.	a)	Reduce the network shown in figure to single voltage source in series with a resistance between the terminals A and B. 	CO2	PO2	08
		b)	Apply super-mesh analysis, determine current " i_o " for the network shown in figure below 	CO2	PO2	06
		c)	Derive an expression for Delta to star converter.	CO1	PO1	06
			OR			
	2.	a)	In the circuit shown, determine the value of ' E_2 ' by mesh analysis. Such that the current through the $(8 + j8) \Omega$ impedance is zero. 	CO2	PO2	10

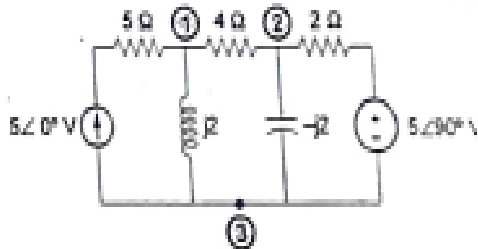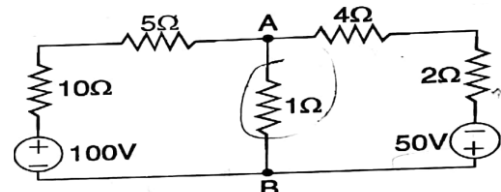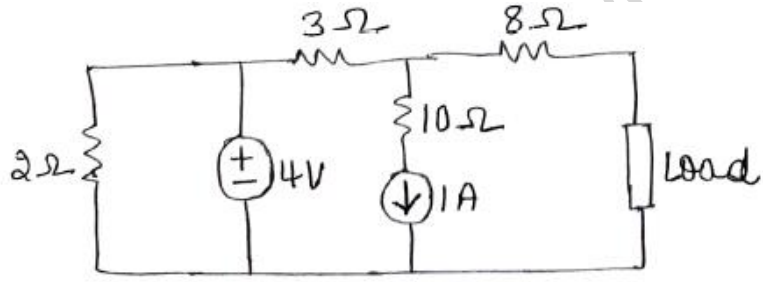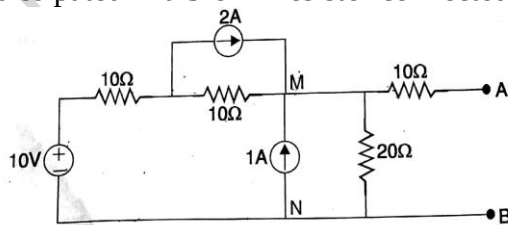	b)	In the network shown in Figure, determine node voltage by nodal analysis method. 	CO2	PO2	10
		UNIT - II			
3.	a)	Determine the current through branch 'AB' in the network shown in the figure using superposition theorem. 	CO2	PO2	10
	b)	Determine Norton's equivalent circuit as shown in Fig Q3(b)  Fig Q3(b)	CO2	PO2	10
		OR			
4.	a)	State and explain Thevenin's theorem.	CO2	PO2	10
	b)	Find the Thevenin's equivalent circuit at the terminals A, B for the network shown in figure and hence determine the power dissipated in a 5-ohm resistor connected between A and B. 	CO2	PO2	10
		UNIT - III			
5.	a)	Derive the expression for resonant frequency in terms half power frequencies	CO2	PO2	10
	b)	In a series circuit $R = 6 \Omega$, $\omega_0 = 4.1 \times 10^6$ rad/sec, band width = 10^5 rad/sec. Compute L, C, half power frequencies and Q.	CO2	PO2	10

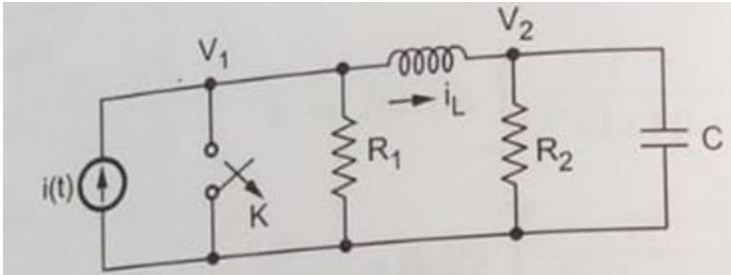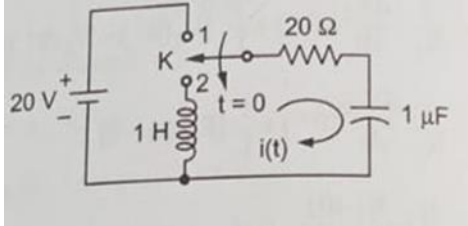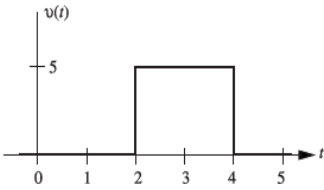		OR			
6	a)	The network shown in figure has two independent node pairs of the switch K is opened at $t=0$, find the following quantities at $t=0$ i) V_1 ii) V_2 iii) dV_1/dt iii) dV_2/dt. 	CO2	P02	10
	b)	In the circuit as shown in the fig the switch K is changed from position 1 to 2 at $t=0$. The steady state having been reached before switching Find values of $i(t)$, $di(t)/dt$ and $d^2i(t)/d(t^2)$ at $t=0+$ 	CO2	P02	10
		UNIT - IV			
7.	a)	State and prove initial value and final value theorem.	CO3	P02	10
	b)	Express the voltage pulse shown in Fig. in terms of unit step function and then find $V(s)$ also determine $L\{dv(t)/d(t)\}$ 	CO3	P02	10
		OR			
8.	a)	Obtain the Laplace transform of (i) Unit step function (ii) Impulse function (iii) Sinusoidal function	CO3	PO2	10
	b)	State and prove initial and final value theorem.	CO3	PO2	10
		UNIT - V			
9.	a)	Determine the Z-parameters for the circuit shown in the Fig.	CO4	P03	10

	b)	Obtain the h-parameters of the network shown in Fig. Give its equivalent circuit.	CO4	PO3	10
		OR			
10.	a)	Obtain the Z-parameters in terms of Y-parameters.	CO4	PO3	10
	b)	Find Z and h-parameters given in Fig.	CO4	PO3	10
