

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

May 2023 Semester End Main Examinations

Programme: B.E.

Branch: Electrical & Electronics Engineering

Course Code: 22EE3PCECT

Course: ELECTRICAL CIRCUIT THEORY

Semester: III

Duration: 3 hrs.


Max Marks: 100

Date: 17.05.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.


UNIT - I

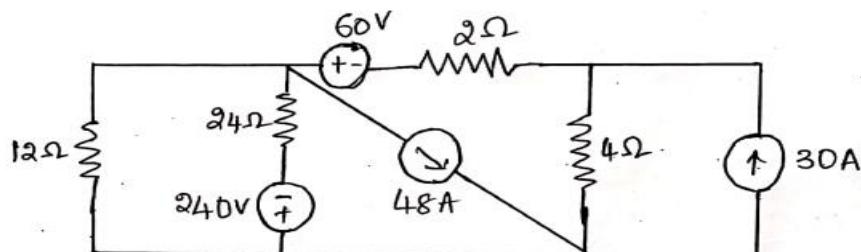1 a) Explain about circuit elements. **04**
 b) Determine the current in 12Ω resistor shown in fig(1b) using source transformation method. **08**



fig(1b)

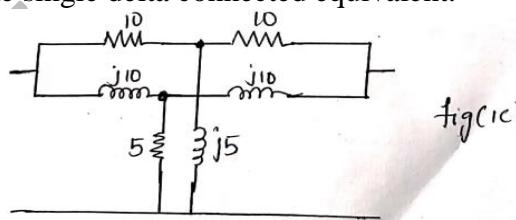
c) The network shown in the fig(1c) consists of two star connected circuits in parallel. Obtain the single delta connected equivalent. **08**



fig(1c)


OR

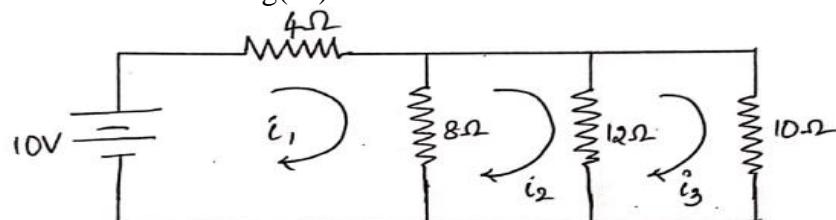2 a) Find the output power from the voltage source using mesh current analysis, for the circuit shown in fig(2a) **10**




fig(2a)

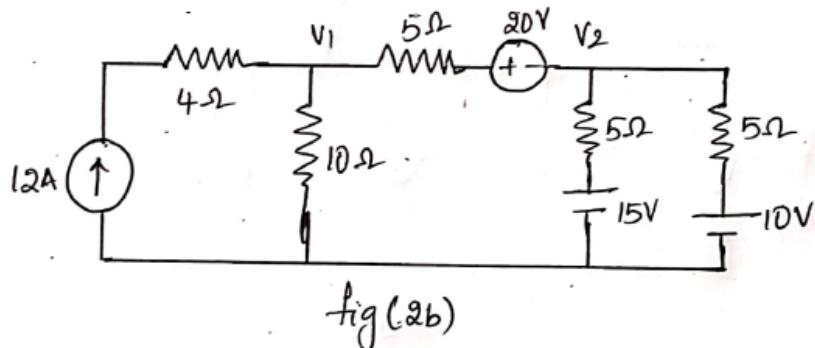b) using node voltage analysis, find the voltages V_1 and V_2 of the circuit shown 10




UNIT - II

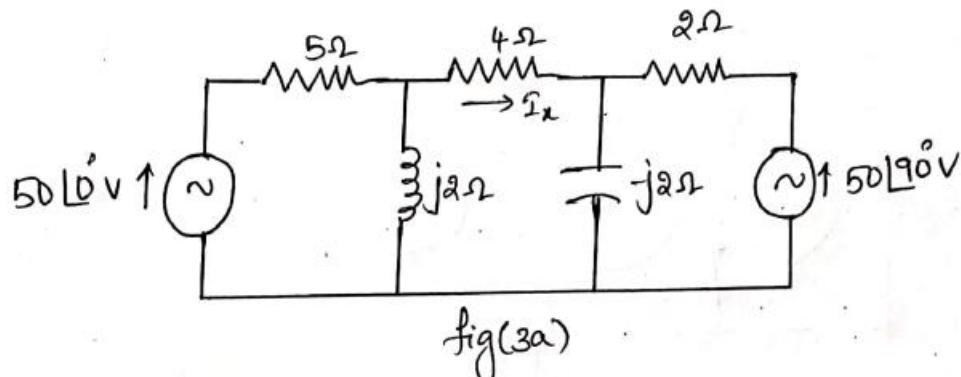3 a) In the circuit shown in fig(3a), find I_x using Superposition theorem. 09



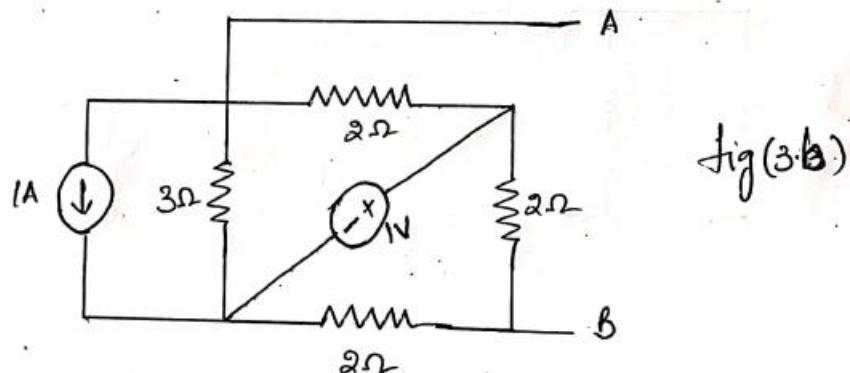b) Determine the current through 1Ω resistor connected across AB in the network shown in fig(3b) using Norton's theorem. 11



UNIT - III

4 a) Prove that $f_r = \sqrt{f_1 f_2}$ in a series resonant RLC circuit. 05

b) Derive expression for f_r in a parallel resonant RLC circuit? and compare series and parallel resonant circuits. 08

c) A series RLC circuit has $R=10\Omega$, $L=0.1\text{H}$ and $C=100\mu\text{F}$ is connected across a 200V, variable frequency source. Find (a) The Resonant frequency, (b) Impedance at this frequency, (c) the voltage drop across inductance and capacitance at the frequency, (d) Quality factor, (e) Bandwidth. 07

OR

5 a) Derive expression for current flowing through inductor in a DC excited RL series circuit. And also derive expressions for voltage and power across R and L with required plots. 10

b) Switch 'K' is closed at $t=0$ in the network shown in Fig.5.b with capacitor uncharged. Determine i , di/dt , d^2i/dt^2 at $t = 0_+$. 10


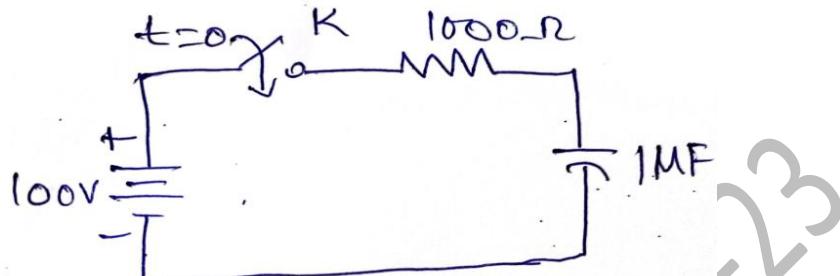


Fig. 5.b

UNIT - IV

6 a) State and prove initial and final value theorem in Laplace transformation. 10

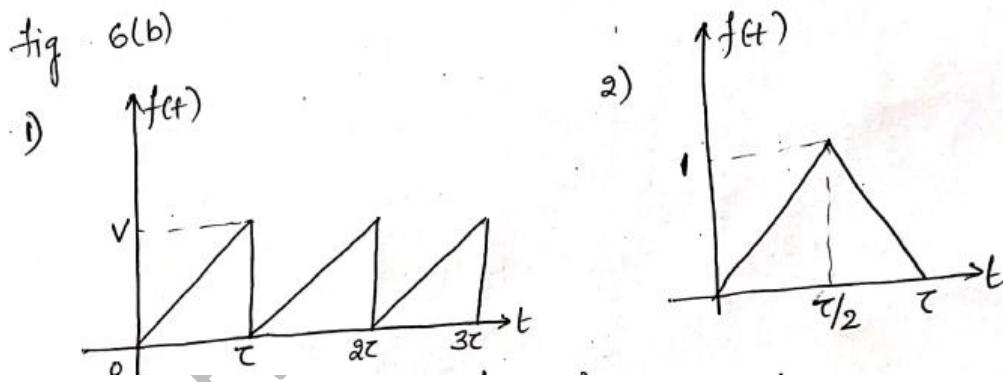b) Write time domain equations and find laplace transform for the following signals shown in fig(6b) 10



UNIT - V

7 a) Define and explain Z parameters and ABCD parameters. 10

b) Determine 'Y' parameter of the network shown in Fig.7. b. 10

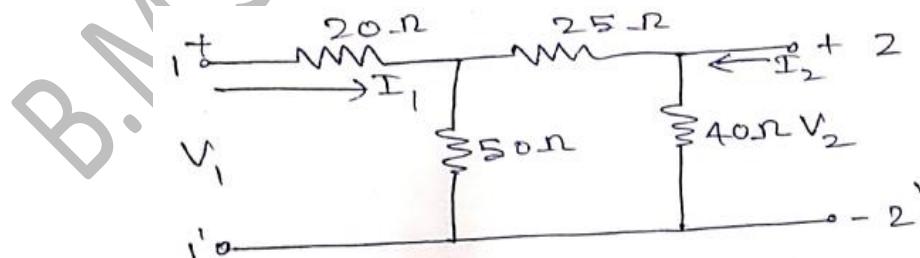


Fig. 7.b
