

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

April 2024 Semester End Main Examinations

Programme: B.E.

Branch: Electrical and Electronics Engineering

Course Code: 19EE3PCEEM


Course: Electrical and Electronic Measurements

Semester: III

Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

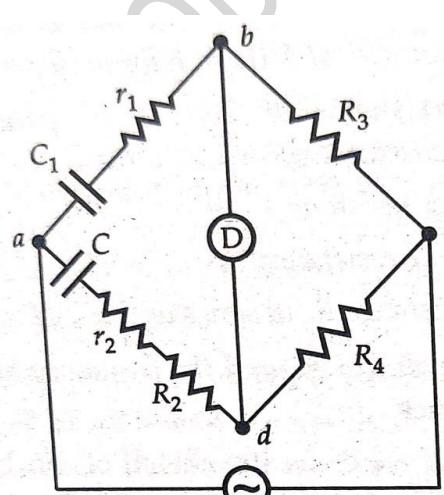UNIT - I			CO	PO	Marks
1	a)	Arrive at the expression for bridge sensitivity of a Wheatstone bridge.	CO1	PO1	08
	b)	The four arms of an ac bridge are as shown in Fig.1b. A supply of 450Hz is given to the bridge. At balance $R_2=4.8\Omega$, $R_3= 2000\Omega$, $R_4=2850\Omega$ and $C_2=0.5\mu F$ and $r_2 =0.4\Omega$. Determine the value of imperfect capacitor C_1 and its equivalent resistance r_1 and also the dissipating factor for this capacitor.	CO1	PO2	06
	c)	 <p>Describe the various factors that causes errors in AC bridges measurements and suggest the method of minimization for the same.</p>	CO1	PO1	06
OR					
2	a)	Derive the equations for balance in case of Anderson's bridge. Draw the phasor diagram for balance condition.	CO1	PO2	07
	b)	A Wheatstone's bridge circuit arrangement is as follows : ratio arms: P=1000Ω and Q=100Ω, standard resistance S=200Ω and the test resistance R=2005Ω. The battery has an emf of 5V and	CO1	PO2	07

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

		negligible internal resistance. The galvanometer has a current sensitivity of 10 mm/ μ A and an internal resistance of 100 Ω . Determine the deflection of the galvanometer and the sensitivity of the bridge in terms of deflection per unit change in resistance.			
	c)	Discuss the sources and the null detectors that are used for a.c. bridges.	CO1	PO1	06
		UNIT - II			
3	a)	Explain the Construction and operation of single-phase dynamometer type power factor meter.	CO1	PO1	07
	b)	A wattmeter has a current coil of resistance 0.03 ohm and a pressure coil of resistance 6000 ohms is connected to measure the power consumed by a load. Determine the percentage error if the wattmeter is so connected that: 1) the current coil is on the load side 2) the pressure coil is on the load side If the load takes 20A at a voltage of 220V and 0.6 powerfactor.	CO2	PO2	06
	c)	Enumerate the special features incorporated in the dynamometer wattmeter when used to measure power in circuits of low power factor	CO2	PO2	07
		UNIT - III			
4	a)	With necessary circuit diagram and phasor explain Silsbee's method for CT testing	CO2	PO2	08
	b)	A 1000/5A ,50Hz current transformer has a secondary burden comprising a non-inductive impedance of 1.6 Ω . The primary winding has one turn. Determine the flux in the core and ratio error at full load. Neglect leakage reactance and assume iron loss in the core to be 1.5W at full load. The magnetizing mmF is 100A.	CO2	PO2	08
	c)	Describe how a DC potentiometer can be used for a Calibration of dc voltmeter.	CO2	PO2	04
		OR			
5	a)	Enumerate the use of instrument transformer for range extension.	CO2	PO1	04
	b)	A current transformer has a bar primary and 200 secondary winding turns. The secondary winding burden is an ammeter of resistance 1.2 Ω and reactance 0.5 Ω , the secondary winding has a resistance of 0.2 Ω and reactance of 0.3 Ω . The core requires the equivalent of an mmf of 100A for magnetization and 50A for core losses. Determine the primary winding current when the ammeter in the secondary winding indicates 5A.	CO2	PO2	08
	c)	With the circuit diagram explain the steps used for measurement using Crompton's type dc potentiometer	CO2	PO2	08
		UNIT - IV			
6	a)	List any four advantages of digital voltmeters over conventional analog voltmeters.	CO2	PO1	04

	b)	With a neat block diagram explain the working of integrating type DVM.	CO2	PO1	08
	c)	With a neat block diagram explain the working of digital oscilloscope.	CO2	PO1	08
		UNIT - V			
7	a)	With necessary diagram explain the construction and working of LVDT.	CO3	PO1	07
	b)	Prove that gauge factor of strain gauge is given by $G_f = 1+2u$, where u is poisson's ratio.	CO3	PO2	08
	c)	Explain the working principle of piezoelectric transducers	CO3	PO1	05

B.M.S.C.E. - ODD SEM 2023-24