

U.S.N.								
--------	--	--	--	--	--	--	--	--

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## January / February 2025 Semester End Main Examinations

**Programme: B.E.**

**Semester: III**

**Branch: Electrical and Electronics Engineering**

**Duration: 3 hrs.**

**Course Code: 23EE3PCMNI**

**Max Marks: 100**

**Course: Measurements and Instrumentation**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

<b>UNIT - I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>
1	a)	With a neat circuit diagram arrive at the balance condition of Wheatstone bridge	CO2	PO2	<b>08</b>
	b)	In the wheatstone bridge , the value of resistance of various arms are: $P=1000\Omega$ , $Q=100 \Omega$ , $R=2005 \Omega$ and $S=200 \Omega$ . The battery has an emf of 5V & negligible internal resistance. The galvanometer has a current sensitivity of $10\text{mm}/\mu\text{A}$ & an internal resistance of $100 \Omega$ . Calculate the deflection of galvanometer & the sensitivity of the bridge in terms of deflection per unit change in resistance.	CO2	PO2	<b>08</b>
	c)	Explain the loss of charge method?	CO1	PO1	<b>04</b>
<b>OR</b>					
2	a)	With a neat circuit diagram arrive at the balance condition of Kelvin double bridge.	CO1	PO1	<b>10</b>
	b)	With the circuit diagram explain the working of Crompton's type(Lab. Type) DC potentiometer.	CO2	PO1	<b>10</b>
<b>UNIT - II</b>					
3	a)	Describe the sources and the null detectors that are used for a.c. bridges	CO2	PO1	<b>06</b>
	b)	Derive the equations for balance in case of Maxwell's inductance capacitance bridge. Draw the phasor diagram for balance condition.	CO2	PO2	<b>08</b>
	c)	A maxwell's capacitance bridge is used to measure an unknown inductance in comparison with capacitance. The various values at balance are $R_2=400\Omega$ ; $R_3=600\Omega$ ; $R_4=1000\Omega$ ; $C_4=0.5\mu\text{F}$ , calculate the values of $R_1$ & $L_1$ . Calculate also the value of storage (Q) factor of coil if the frequency is 1000 Hz.	CO2	PO2	<b>06</b>
<b>OR</b>					
4	a)	Describe working of Schering bridge. Derive the equation for capacitance & dissipation factor.	CO2	PO2	<b>08</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

	b)	Derive the equation of balance for an Anderson's bridge. Discuss the advantages & disadvantages of the bridge	CO2	PO2	<b>08</b>
	c)	What are the causes for errors in A.C.bridge & their compensations?	CO2	PO1	<b>04</b>
<b>UNIT - III</b>					
5	a)	With the help of a block diagram explain the working of Electronic energy meter.	CO2	PO2	<b>06</b>
	b)	Explain the special features incorporated in the dynamometer wattmeter when used to measure power in circuits of low power factor.	CO2	PO1	<b>06</b>
	c)	A wattmeter has a current coil of 0.03 ohm resistance & a pressure coil of 6000 ohm resistance. Calculate the percentage error if the wattmeter is so connected that (i) The current coil is on the load side,ii) the pressure coil is on the load side (a) if the load takes 20A at a voltage of 220V and 0.6 p.f. in each case(b) what load current would give equal errors with the two connections?	CO2	PO2	<b>08</b>
<b>OR</b>					
6	a)	Explain single phase electrodynamic type power factor meter?	CO1	PO1	<b>06</b>
	b)	Using relevant phasor diagram, derive an expression for phase angle error in C.T	CO2	PO2	<b>08</b>
	c)	Explain the construction & working of LPF wattmeter?	CO2	PO1	<b>06</b>
<b>UNIT - IV</b>					
7	a)	What are the advantages of electronic instruments?	CO1	PO1	<b>06</b>
	b)	Describe various factors which are taken into consideration while selecting an electronic type analog voltmeter.	CO1	PO1	<b>08</b>
	c)	Explain with help of block diagram, the various parts of an electronic multimeter?	CO2	PO1	<b>06</b>
<b>OR</b>					
8	a)	Give the comparison between electronic meters & conventional analog meters	CO1	PO1	<b>06</b>
	b)	With block diagram explain working of Ramp type DVM	CO2	PO1	<b>08</b>
	c)	Explain servo balancing potentiometer type DVM	CO2	PO1	<b>06</b>
<b>UNIT - V</b>					
9	a)	Explain the construction of wire gauges & derive the expression for the gauge factor.	CO2	PO2	<b>10</b>
	b)	With necessary diagram explain the construction and working of LVDT	CO2	PO1	<b>10</b>
<b>OR</b>					
10	a)	What is piezoelectric & Hall effect transducers?	CO2	PO1	<b>10</b>
	b)	Explain temperature sensors devices, RTD's, thermistors, Thermocouples	CO2	PO1	<b>10</b>

\*\*\*\*\*