

U.S.N.								
--------	--	--	--	--	--	--	--	--

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

April 2024 Semester End Main Examinations

Programme: B.E.

Branch: Electrical and Electronics Engineering

Course Code: 23EE3PCTDC

Course: Transformers and DC Machines

Semester: III

Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

			UNIT - I	CO	PO	Marks
Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.	1	a)	Discuss the losses and methods of reducing losses in transformer.	CO1	PO1,2, 3	06
		b)	Draw the vector diagram of a practical transformer on load supplying i) Unity power factor load ii) lagging power factor load.	CO1	PO1,2, 3	06
		c)	The OC and SC test on a 10 KVA, 500/250V, 50 Hz single phase transformer gave the following results OC Test (LV side): 25 V, 3 A, 200W SC Test (HV side): 15 V, 30A, 300W Calculate i) efficiency at UPF ii) maximum efficiency at UPF iii) regulation at full load 0.8 pf lag.	CO1	PO1,2, 3	08
			UNIT - II			
	2	a)	With neat sketch, explain the three phase star - delta connected transformer.	CO2	PO3,4	10
		b)	Discuss the necessity and conditions for parallel operation of phase transformers	CO2	PO3,4	10
			OR			
	3	a)	With neat sketch, explain the three phase delta - star connected transformer.	CO2	PO3,4	10
		b)	Derive an expression for saving in conductor material in an autotransformer over a two-winding transformers of equal rating. State the advantages and disadvantages of autotransformer over two-winding transformers.	CO2	PO3,4	10
			UNIT - III			
	4	a)	With relevant diagrams, explain armature reaction in D.C generators.	CO3	PO1,2, 3	10
		b)	A 4-pole shunt DC generator is delivering 20A to a load of 10Ω . If the armature resistance is 0.5Ω and the shunt field resistance is 50Ω , calculate the induced emf, voltage regulation of the machine. Allow a drop of 1V per brush.	CO3	PO1,2, 3	06

	c)	Distinguish between lap and wave winding used in a D.C. generator.	CO3	PO1,2, 3	04
		UNIT - IV			
5	a)	Explain typical T/I _a and N/I _a characteristics of D.C series and shunt motors.	CO3	PO1,2, 3	10
	b)	A 240 V series motor takes 40 A when giving its rated torque at 1500 rpm. Its armature and series field resistance is 0.18 ohm and 0.12 ohm respectively. Find the external resistance which must be added to obtain rated torque (i) at starting and (ii) at 1000 rpm	CO3	PO1,2, 3	10
		UNIT - V			
6	a)	With a neat sketch elaborate the Hopkinson's test performed on a DC machines.	CO3	PO1,2, 3	10
	b)	Explain Retardation test in detail.	CO3	PO1,2, 3	10
		OR			
7	a)	With a neat sketch elaborate the Swinburne's test performed on a DC machines.	CO3	PO1,2, 3	10
	b)	Explain field test on DC series motor in detail.	CO3	PO1,2, 3	10

B.M.S.C.E. - ODD SEMESTER