

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

August 2023 Semester End Make-Up Examinations

Programme: B.E.

Branch: Electrical & Electronics Engineering

Course Code: 22EE3PCTIM

Course: Transformers & Induction Machines

Semester: III

Duration: 3 hrs.

Max Marks: 100

Date: 11.08.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1 a) What is polarity test in transformers? Explain its need. **05**
 b) Explain how the voltage regulation and efficiency of a transformer can be predetermined by indirect tests. **07**
 c) A 30kVA 2400/120 V transformer has HV winding resistance of 0.1Ω and leakage reactance of 0.22Ω . The LV winding resistance of 0.035Ω and leakage reactance of 0.012Ω . Calculate for the transformer
 (i) Equivalent resistance as referred to HV & LV winding
 (ii) Equivalent reactance as referred to HV & LV winding
 (iii) Voltage regulation at full load 0.8 pf lag and 0.8 pf lead **08**

OR

2 a) Derive an expression for the saving of copper in an autotransformer as compared to two winding transformer. **05**
 b) Explain with a neat sketch, the Sumpner's test on single phase transformer **07**
 c) A 5kVA, 500/250V, 50Hz transformer gave the following results:
 OC test: 500V, 1A, 50W HV side readings
 SC test: 25V, 10A, 60W LV side shorted
 Determine Circuit constants and draw the equivalent circuit **08**

UNIT - II

3 a) With a circuit diagram & phasor diagram explain open delta connection. Obtain the relationship between the power transferred by V-V connected with that of $\Delta - \Delta$ connected transformers. **06**
 b) Explain with necessary diagrams how two 1-phase transformers can be used to convert 3-phase supply to 2-phase supply. **06**
 c) Two transformers are connected in parallel to share a common load of 100kVA at 0.8 lagging power factor. Their impedances in secondary terms are $Z_A = (0.15+j0.5) \Omega$ and $Z_B = (0.1+j0.6) \Omega$. Find kVA load shared by each transformer. Which transformer takes more load. Show the connection diagram. **08**

UNIT - III

4 a) Derive an expression for starting torque produced in three phase induction motor. 06

b) Show that ratio of mechanical power developed to rotor copper loss is $\frac{1-s}{s}$ where s is the slip. 06

c) An 18650W, 4 pole, 50Hz, 3-phase Induction Motor has friction and windage losses of 2.5 percent of the output. The full load slip is 4% Compute for full load

- (i) the rotor copper loss
- (ii) the rotor input
- (iii) the shaft Torque

the motor efficiency if the stator copper loss is 2000W

OR

5 a) Explain the working of an induction generator with a neat sketch 06

b) Draw the equivalent circuit for a 3-phase induction motor and explain how mechanical power developed is taken care in the equivalent circuit. 06

c) A 746-kW, 3-phase, 50-Hz, 16-pole induction motor has a rotor impedance of $(0.02 + j 0.15) \Omega$ at standstill. Full-load torque is obtained at 360 rpm. Calculate

- (i) the ratio of maximum to full-load torque
- (ii) the speed of maximum torque
- (iii) the rotor resistance to be added to get maximum starting torque
- (iv) Ratio of starting torque to maximum torque

UNIT - IV

6 a) Explain with neat sketch the construction and working of star-delta starter. 06

b) Explain the rotor resistance method of speed control with a neat circuit diagram 06

c) A 3-phase, 400V, 14.9kW, 50 Hz star connected induction motor gave the following test readings (line value)
No load: 400 V, 1250 W, 9A
Blocked rotor: 150 V, 4000 W, 38A
Stator copper loss is equal to rotor copper loss at stand still. Draw the circle diagram and estimate

- i) Full load current
- ii) Full load pf.
- iii) Full load slip

UNIT - V

7 a) Explain the double field revolving theory as applied to single phase Induction Motor and prove that it cannot produce any starting torque. Also, explain how to make single phase induction motor self-start. 08

b) Explain the working of a single value capacitor run induction motor. 06

c) Draw the equivalent circuit of single-phase induction motor and explain 06
