

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## August 2024 Semester End Main Examinations

**Programme: B.E.**

**Semester: IV**

**Branch: Electrical and Electronics Engineering**



**Duration: 3 hrs.**

**Course Code: 22EE4PCAEL**


**Max Marks: 100**

**Course: Analog Electronic Circuits and LIC**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

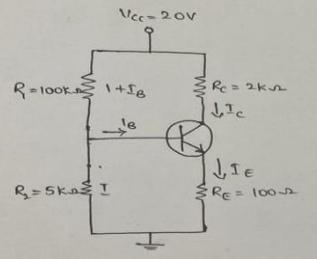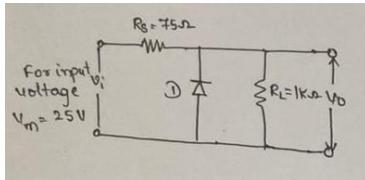UNIT - I			CO	PO	Marks
1	a)	What do you mean by wave shaping circuits? Explain the working of basic series clipper circuit.	CO2	PO I	<b>06</b>
	b)	For the circuit shown in figure, calculate $I_B$ , $V_{CE}$ , $I_C$ & stabilityfactor. Assume $\beta=50$ , $V_{BE}=0.2V$ .	CO3	PO2	<b>08</b>
		 <p>Fig. 1.b</p>			
	c)	Mention the factors affecting the operating point?	CO2	PO1	<b>06</b>
<b>OR</b>					
2	a)	Analyze the given circuit & sketch the nature of output voltage waveforms.	CO3	PO2	<b>08</b>
		 <p>Fig. 2.a</p>			
	b)	Draw and explain the operation of voltage divider bias circuit and derive the equation for stability factors.	CO3	PO2	<b>12</b>
<b>UNIT - II</b>					
3	a)	With a neat block diagram explain the basic concept of feedback amplifier. List the advantages and disadvantages of feedback.	CO2	PO1	<b>06</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
Revealing of identification, appeal to evaluator will be treated as malpractice.

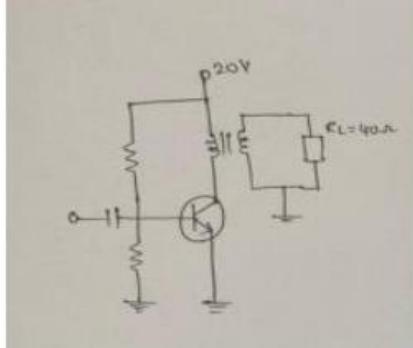	b)	Derive equation for input and output resistance with feedback for voltage series and voltage shunt feedback circuits.	CO2	PO1	<b>08</b>
	c)	Explain the characteristics of Darlington pair?	CO2	PO1	<b>06</b>
<b>UNIT - III</b>					
4	a)	Explain the working of a class B push pull amplifier?	CO2	PO1	<b>06</b>
	b)	A class -A amplifier shown in figure, operates from $V_{CC}=20V$ , draws a no-signal current of $5A$ and feeds a load of $40\Omega$ through a step-up transformer of $N_2/N_1=3.16$ . Find <ul style="list-style-type: none"> <li>i. Whether the amplifier is properly matched for maximum power transfer,</li> <li>ii. Maximum ac signal power output,</li> <li>iii. Maximum dc power input,</li> <li>iv. Conversion efficiency at maximum signal input.</li> </ul>	CO3	PO2	<b>08</b>
					
		Fig. 4.b			
	c)	Explain drain characteristics of JFET.	CO2	PO1	<b>06</b>
<b>UNIT - IV</b>					
5	a)	Explain the operation of inverting and non-inverting amplifier using op-amp. Derive gain equation.	CO3	PO1	<b>08</b>
	b)	What are the advantages and disadvantages of active filters over passive filters.	CO3	PO1	<b>06</b>
	c)	Explain the factors affecting the performance of a regulator.	CO4	PO1	<b>06</b>
<b>OR</b>					
6	a)	Explain the operation of inverting summing amplifier. Derive the equation for the output voltage.	CO2	PO1	<b>06</b>
	b)	Briefly explain first order low pass Butterworth filter.	CO4	PO2	<b>06</b>
	c)	Briefly explain with the help of the schematic diagram working of LM317 IC regulator.	CO4	PO2	<b>08</b>
<b>UNIT - V</b>					
7	a)	With the help of neat circuit diagram, explain the operation of triangular waveform generator. Derive equation for frequency of oscillations.	CO4	PO2	<b>10</b>
	b)	Explain with neat circuit diagram & waveform the operation of inverting Schmitt trigger circuit. Design a Schmitt trigger for UTP=2.5V and LTP=1.0V. $V_{sat}=12V$ & $V_{ref}=1.9V$	CO4	PO2	<b>10</b>

\*\*\*\*\*