

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

December 2023 Supplementary Examinations

Programme: B.E.

Semester: IV

Branch: Electrical and Electronics Engineering



Duration: 3 hrs.

Course Code: 22EE4PCAEL



Max Marks: 100

Course: ANALOG ELECTRONIC CIRCUITS AND LIC

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

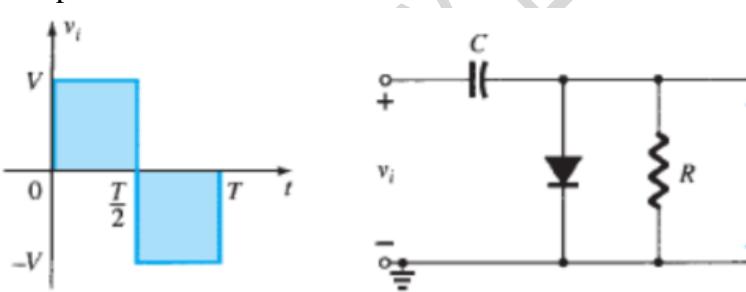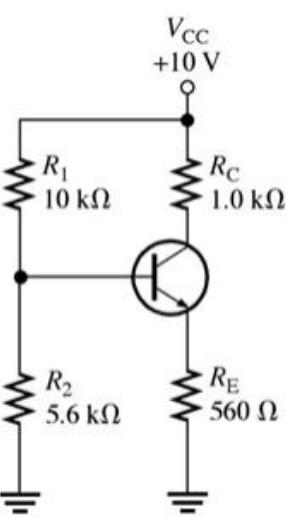UNIT - I			CO	PO	Marks
1	a)	With a neat output device characteristic of BJT explain the importance of Q Point in biasing.	CO1	PO1	05
	b)	Determine the output voltage and input – output waveform of the circuit shown in Fig. 1b. Assuming ideal diodes, $1\text{k}\Omega$ resistor and 1 Vp .	CO3	PO2	07
	c)	<p>Fig.1b</p>  <p>Determine V_{CE} and I_C in the voltage-divider biased transistor circuit. Assume $\beta_{DC} = 100$ and $I_E \approx I_C$.</p> <p>Fig.1c</p> 	CO2	PO1	08

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
Revealing of identification, appeal to evaluator will be treated as malpractice.

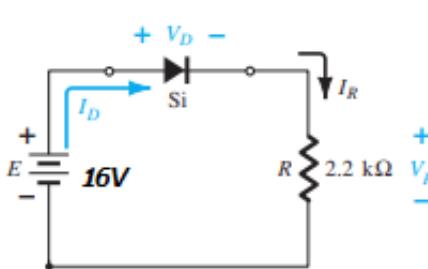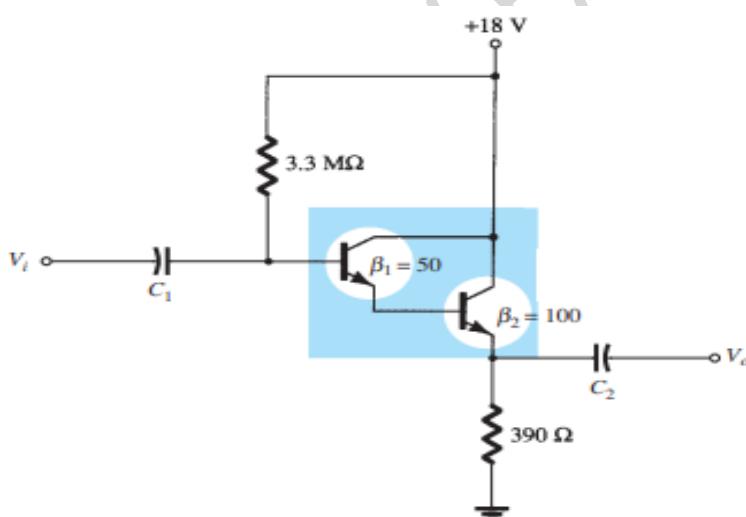OR					
2	a)	Derive expressions for A_v , A_i , Z_i and Z_o for common emitter voltage divider bias configuration using complete r_e equivalent model	CO2	PO1	08
	b)	For the series-diode shown in Fig 1c. Determine V_D , V_R and I_D	CO2	PO1	06
					
		Fig.2b			
	c)	Using exact analysis (Thevenin Theorem), obtain expressions for I_B , V_{CE} for a voltage divider bias circuit.	CO2	PO1	06
UNIT - II					
3	a)	Draw the four basic feedback network connections and mark all the significant parameters in it.	CO1	PO1	08
	b)	Determine the dc bias voltages and currents for the Darlington configuration of Fig. 3b.	CO3	PO2	07
					
		Fig.3b.			
	c)	With a neat circuit diagram explain the operation of basic cascode connection.	CO1	PO2	05
UNIT - III					
4	a)	Describe the working and construction of N channel Enhancement type MOSFET	CO1	PO2	08
	b)	Determine the efficiency of a transformer-coupled class A amplifier for a supply of 12 V and outputs of: a) $V(p) = 12$ V. b) $V(p) = 6$ V.	CO2	PO2	04
	c)	With a relevant circuit explain DC bias and AC operation of a series fed Class A amplifier also arrive at the expression for maximum efficiency .	CO2	PO2	08

UNIT - IV					
5	a)	With neat circuit diagram and waveforms, explain the operation of a first order low pass filter. Draw the frequency response. Derive an expression for the transfer function of the filter.	CO1	PO2	08
	b)	Referring to the Fig.5b, design an adjustable positive voltage regulator using LM317 for an output voltage V_o varying from 4 to 12V and an output I_o of 1A.	CO3	PO3	07
		Fig.5b			
	c)	Describe the important features of Instrumentation amplifier	CO1	PO1	05
OR					
6	a)	With a neat circuit connection explain the operation of LM337 regulator.	CO2	PO2	08
	b)	Given a band pass filter with resonant frequency of f_r of 1000Hz and a bandwidth (B) of 3000Hz, Determine its a) quality factor b) lower cut-off frequency and c) higher cut-off frequency.	CO2	PO2	07
	c)	With neat block diagrams explain the types of linear voltage regulators.	CO2	PO2	05
UNIT - V					
7	a)	For the Schmitt trigger circuit shown in Fig.7a. $R_1 = 56k\Omega$, $R_2 = 150\Omega$, $V_i = 1 V_{pp}$ sine wave of frequency 50Hz, $V_{ref} = 0V$ and op amp 741 is used with supply voltages of $\pm 15V$ and the saturation voltages are $\pm 13V$. Determine the threshold voltages V_{UT} and V_{LT} and draw the input and output waveforms. Also, plot the hysteresis voltage curve.	CO2	PO2	06
		Fig.7a.			

	b)	With a neat circuit diagram enumerate the operation of voltage to current converter with grounded load.	CO2	PO2	07
	c)	With a neat circuit diagram explain triangular wave generator	CO2	PO2	07

SUPPLEMENTARY EXAMS 2023