

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

August 2024 Semester End Main Examinations

Programme: B.E.

Branch: Electrical and Electronics Engineering

Course Code: 23EE4PCAEL

Course: Analog Electronics and Linear Integrated Circuits

Semester: IV

Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I			CO	PO	Marks
1	a)	Explain the input and output characteristics of a transistor in CE configuration.	<i>CO1</i>	<i>PO1</i>	08
	b)	Define α_{dc} and β_{dc} of a transistor. For a transistor, the base current is $100\mu A$ and the collector current is $2.9\mu A$. Find α_{dc} and β_{dc} .	<i>CO3</i>	<i>PO2</i>	06
	c)	Define the three voltage stability factors.	<i>CO1</i>	<i>PO1</i>	06
OR					
2	a)	Analyse the Common Emitter transistor circuit using a simplified hybrid model.	<i>CO1</i>	<i>PO1</i>	10
	b)	Explain the Voltage Divider Bias configuration of a transistor.	<i>CO1</i>	<i>PO1</i>	10
UNIT - II					
3	a)	With the help of a neat diagram explain the operation and characteristics of <i>p</i> -channel depletion type MOSFET.	<i>CO1</i>	<i>PO1</i>	12
	b)	Determine I_{DQ} , V_{GSQ} , and V_{DS} for the network of Figure 3b	<i>CO2</i>	<i>PO1</i>	08
Figure 3b					

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

UNIT - III					
4	a)	Draw the AC equivalent circuit using an approximate hybrid equivalent model for the BJT voltage divider bias configuration. Write the expressions for input impedance, output impedance, voltage gain, and current gain.	<i>CO1</i>	<i>PO2</i>	08
	b)	Explain class B- Push-Pull Amplifier.	<i>CO1</i>	<i>PO1</i>	12
UNIT - IV					
5	a)	Define Input Offset current, Input Resistance, CMRR, Slew Rate, and Voltage Gain of op-amp.	<i>CO3</i>	<i>PO2</i>	10
	b)	Explain op-amp as inverting and non-inverting amplifiers.	<i>CO2</i>	<i>PO1</i>	10
OR					
6	a)	What are the characteristics of an ideal op-amp?	<i>CO1</i>	<i>PO1</i>	07
	b)	Explain inverting summing and averaging amplifiers.	<i>CO1</i>	<i>PO1</i>	06
	c)	Explain op-amp as a differentiator amplifier	<i>CO1</i>	<i>PO1</i>	07
UNIT - V					
7	a)	Briefly explain the operation of the second-order high-pass Butterworth filter.	<i>CO3</i>	<i>CO2</i>	06
	b)	With the help of a neat circuit diagram, explain the operation of the triangular generator op-amp application. Derive an equation for the frequency of oscillations.	<i>CO2</i>	<i>CO2</i>	08
	c)	Explain with a neat circuit diagram & waveform the operation of inverting the Schmitt trigger circuit.	<i>CO2</i>	<i>CO2</i>	06
