

U.S.N.

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

June 2025 Semester End Main Examinations

Programme: B.E.

Semester: IV

Branch: Electrical and Electronics Engineering


Duration: 3 hrs.




Course Code: 23EE4PCAEL



Max Marks: 100


Course: Analog Electronics and Linear Integrated Circuits

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

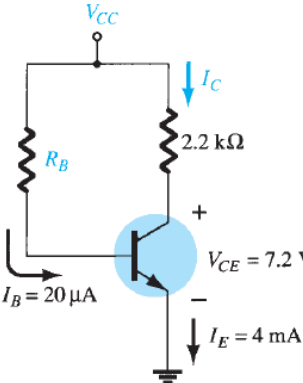Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.			UNIT - I	CO	PO	Marks
	1	a)	What the major difference between a bipolar and a unipolar device? Why is BJT known as a bipolar device? How must the two transistor junctions be biased for proper transistor amplifier operation for a common base configuration.	CO2	PO1	06
		b)	Determine the following for the fixed-bias configuration of Fig. 1b. a. I_C . b. V_{CC} . c. β . d. R_B .	CO3	PO2	08
			 Fig 1b			
		c)	Given $I_{E(dc)} = 1.2 \text{ mA}$, $\beta = 120$, and $r_o = 40 \text{ k}\Omega$, sketch the following: a. Common-emitter hybrid equivalent model. b. Common-emitter r_e equivalent model.	CO3	PO2	06
			OR			
	2	a)	Describe the operation of an n-channel BJT in Common-Emitter configuration. Draw the input and output characteristics.	CO2	PO1	06
		b)	For the voltage-divider bias configuration of Fig. 2b, determine: a. I_Q d. V_B e. V_E f. R_1	CO3	PO2	08

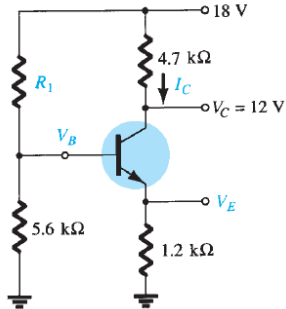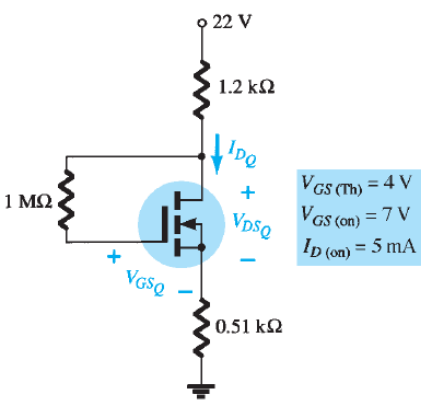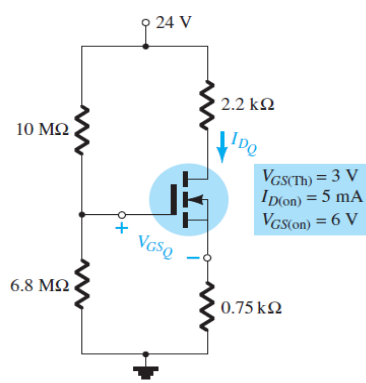		 Fig 2b			
	c)	Given $h_{ie} = 2.4 \text{ k}\Omega$, $h_{fe} = 100$, $h_{re} = 4 \times 10^{-4}$, and $h_{oe} = 25 \text{ mS}$, sketch the following: a. Common-emitter hybrid equivalent model. b. Common-emitter r_e equivalent model.	CO3	PO2	06
		UNIT - II			
3	a)	With a neat circuit diagram, illustrate the operation of an n-channel enhancement type MOSFET. Draw its output and transfer characteristics.	CO1	PO1	10
	b)	For the network of Fig. 3 b , determine: a. I_{DQ}. b. V_{GSQ} and V_{DSQ}. c. V_D and V_S . d. V_{DS} .  Fig 3.b	CO3	PO2	10
		OR			
4	a)	With a neat circuit diagram, illustrate the operation of an n-channel depletion type MOSFET. Draw its output and transfer characteristics.	CO1	PO1	10
	b)	For the voltage-divider configuration of Fig. 4b, determine: a. I_{DQ} and V_{GSQ}. b. V_D and V_S .  Fig 4b	CO3	PO2	10

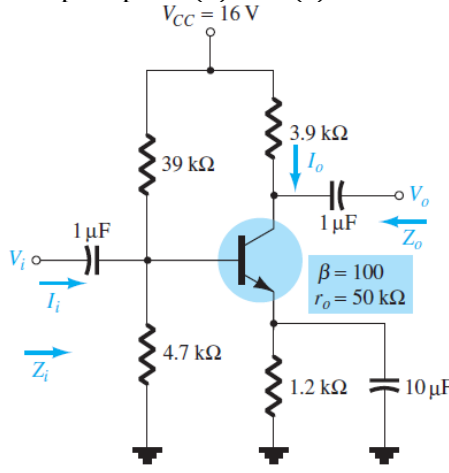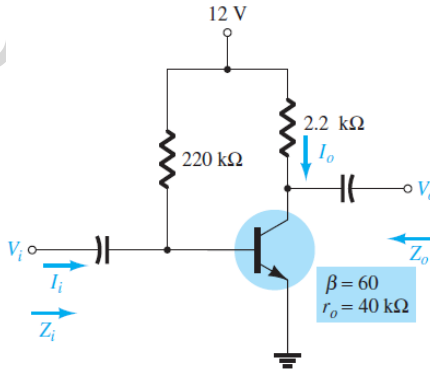		UNIT - III			
5	a)	For the network of Fig. 5a : a. Determine r_e . b. Calculate Z_i and Z_o . c. Find A_v . d. Repeat parts (b) and (c) with $r_o = 25\text{k}\Omega$.  Fig 5 a	CO3	PO2	12
	b)	Explain the operating principle of series fed class A amplifier. Obtain the expressions for output power, efficiency and maximum efficiency.	CO2	PO2	08
		OR			
6	a)	For the network shown in fig 6a: a. Determine r_e . b. Find h_{fe} and h_{ie} c. Find Z_i and Z_o using the hybrid parameters. d. Calculate A_v and A_i using the hybrid parameters. e. Determine Z_i and Z_o if $h_{oe} = 50 \text{ mS}$. f. Determine A_v and A_i if $h_{oe} = 50 \text{ mS}$.  Fig 6 a	CO3	PO2	12
	b)	Explain the operating principle of class B push pull amplifier. Obtain the expressions for output power, efficiency and maximum efficiency.	CO2	PO2	08
		UNIT - IV			
7	a)	Define the following terms with reference to an op-amp	CO1	PO1	06

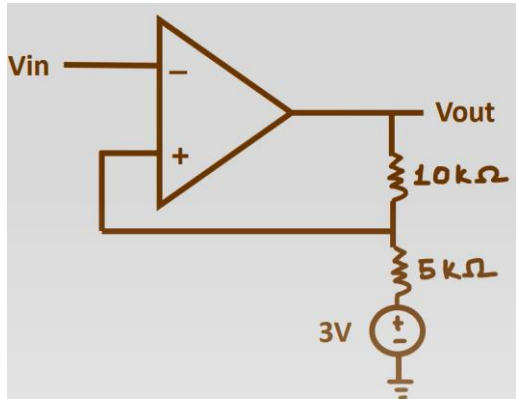		i. Input offset voltage ii. Input bias current iii. Power supply rejection ratio			
	b)	Design an op-amp differentiator that will differentiate an input signal with $f_{\max}=100\text{Hz}$. Draw the output waveform for a square wave input of 1V peak at 100Hz applied to the differentiator. Assume $C_1=0.1\mu\text{F}$.	CO4	PO3	08
	c)	With neat circuit diagrams, describe the working of inverting and non-inverting op-amp configurations. Derive the expression of output voltage in both the cases. Plot the waveforms for a sinusoidal input	CO2	PO2	06
		OR			
8	a)	List any six characteristics of an ideal op-amp	CO1	PO1	06
	b)	Design and draw an op-amp adder circuit to get the output expression as $V_o=-(3.5V_1+2.5V_2+0.5V_3)$. Assume the feedback resistor to be $1\text{k}\Omega$.	CO4	PO4	08
	c)	With neat circuit diagram and waveforms, explain the operation of an op-amp integrator.	CO2	PO2	06
		UNIT - V			
9	a)	With neat circuit diagram and waveforms, explain the operation of a second order low pass filter. Draw the frequency response. Derive an expression for the transfer function of the filter.	CO3	PO2	10
	b)	With relevant circuit diagram and waveforms describe the operation of a triangular wave generator. Derive the expression for frequency of operation.	CO3	PO2	10
		OR			
10	a)	With neat circuit diagram and waveforms, explain the operation of an Astable Multivibrator circuit. Derive an expression for the total time period of the output waveform.	CO3	PO2	10
	b)	For the Schmitt trigger shown in fig 10. b with a saturation voltage of $\pm 15\text{V}$, find Upper and lower threshold voltages. Plot the hysteresis curve	CO3	PO2	10
		 Fig 10 b			
