

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## October 2024 Supplementary Examinations

**Programme: B.E.**

**Semester: IV**

**Branch: Electrical and Electronics Engineering**

**Duration: 3 hrs.**

**Course Code: 23EE4PCAEL**

**Max Marks: 100**

**Course: Analog Electronics and Linear Integrated Circuits**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

UNIT - I			CO	PO	Marks
1	a)	Describe the working of npn transistor in Common Emitter configuration. Draw the input and output characteristics. Mark all the regions of operation and load line.	CO1	PO1	<b>10</b>
	b)	i) Given $\beta=120$ , $r_e=4.5\Omega$ , $r_o=40k\Omega$ , sketch approximate hybrid equivalent model. ii) Given $h_{ie}=1k$ , $h_{re}=2 \times 10^{-4}$ , $h_{fe}=90$ , $h_{oe}=20 \mu\text{S}$ . Sketch the $r_e$ model.	CO2	PO1	<b>10</b>
<b>OR</b>					
2	a)	What is bias stabilization? What are the factors affecting the stability of a transistor? Define stability factors and give expressions for stability factors for voltage divider bias.	CO1	PO1	<b>06</b>
	b)	What is the importance of constant current sources in an integrated circuit? i. Construct a constant current source circuit with a npn transistor. ii. Draw a modified circuit in which the output current is independent of the supply voltage.	CO2	PO1	<b>08</b>
	c)	Determine the following for the fixed-bias configuration of Fig. 2c. a. $I_{BQ}$ and $I_{CQ}$ . b. $V_{CEQ}$ . c. $V_B$ and $V_C$ . d. $V_{BC}$ .	CO2	PO3	<b>06</b>
Fig. 2c.					
UNIT - II					
3	a)	With a neat circuit diagram, illustrate the operation of an n-channel enhancement type MOSFET. Draw its output and transfer characteristics.	CO3	PO2	<b>08</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

	b)	Determine $I_{DQ}$ , $V_{GSQ}$ , and $V_{DS}$ for the network of Figure 3b	CO2	PO1	<b>08</b>
		Figure 3b			
	c)	Draw the small signal model of enhancement type MOSFET. Derive the expression for the transconductance $gm$ .	CO2	PO3	<b>04</b>
		<b>UNIT - III</b>			
4	a)	Derive the expressions for input impedance, output impedance and voltage gain of a common emitter fixed bias configuration in re model. For the network with $R_B=470k\Omega$ , $R_c=3k\Omega$ , $V_{cc}=12V$ , $\beta=100$ and $r_o=50k\Omega$ , find the values of $Z_i$ , $Z_o$ and $A_v$ .	CO1	PO1	<b>10</b>
	b)	Explain the operating principle of transformer coupled class A amplifier. Draw the characteristics with load lines. Obtain the expressions for output power, efficiency and maximum efficiency.	CO2	PO1	<b>10</b>
		<b>UNIT - IV</b>			
5	a)	List any eight characteristics of an ideal op-amp	CO2	PO1	<b>06</b>
	b)	Define the following terms with reference to an op-amp i. Input offset voltage ii. Input bias current iii. Power supply rejection ratio	CO2	PO1	<b>06</b>
	c)	Design an op-amp differentiator that will differentiate an input signal with $f_{max}=100Hz$ . Draw the output waveform for a square wave input of 1V peak at 100Hz applied to the differentiator. Assume $C1=0.1\mu F$ .	CO2	PO4	<b>08</b>
		<b>OR</b>			
6	a)	Draw the frequency response of an op-amp by deriving the expression of open-loop voltage gain as a function of frequency	CO3	PO2	<b>08</b>
	b)	Design and draw an op-amp adder circuit to get the output expression as $V_o= - (5V_1+0.5V_2+3.5V_3)$ . Assume the feedback resistor to be $1k\Omega$ .	CO2	PO3	<b>06</b>
	c)	What is CMRR in an op-amp? What is the significance of CMRR. What is the typical value of CMRR of uA741 op-amp.	CO2	PO2	<b>06</b>
		<b>UNIT - V</b>			
7	a)	With neat circuit diagram and waveforms, explain the operation of a second order low pass filter. Draw the frequency response. Derive an expression for the transfer function of the filter.	CO2	PO1	<b>10</b>
	b)	With neat circuit diagram and waveforms, explain the operation of an Astable Multivibrator circuit. Derive an expression for the total time period of the output waveform.	CO4	PO2	<b>10</b>

\*\*\*\*\*