

U.S.N.								
--------	--	--	--	--	--	--	--	--

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

July / August 2024 Semester End Main Examinations

Programme: B.E.

Branch: Electrical and Electronics Engineering

Course Code: 19EE4PCMC1

Course: Electrical Machines - I

Semester: IV

Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

			UNIT - I		
			CO	PO	Marks
Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.	1	a)	With relevant phasor diagrams, explain the operation of a practical single phase transformer under no load condition.	CO1	<i>P08, 9,12</i> 07
		b)	Discuss, Equivalent circuit diagram of transformer resistance and leakage reactance with vector diagrams.	CO1	<i>P08, 9,12</i> 07
		c)	Draw and explain the Connection diagram of Y- Δ & Δ-Δ connected three-phase transformer.	CO1	<i>P08, 9,12</i> 06
OR					
	2	a)	The results obtained from open circuit and short circuit tests on 5 kVA, 500 / 250 V, 50 Hz, single phase transformer gave the following readings, O.C. Test: 500 V, 1 A, 50 W (L.V. side open) S.C. Test: 25 V, 10A, 60 W (L.V. side shorted) Compute: (i) The efficiency on full load, 0.8 lagging P.F (ii) The voltage regulation at full load, 0.8 leading p.f.	CO1	<i>P08, 9,12</i> 10
		b)	State the advantages of single 3- phase unit transformer over bank of single phase transformers	CO1	<i>P08, 9,12</i> 05
		c)	Draw the Connection diagram of open delta connected three-phase transformer.	CO1	<i>P08, 9,12</i> 05
UNIT - II					
	3	a)	Compare a Two-winding transformer with Auto transformer in detail.	CO2	<i>P08, 9,12</i> 06
		b)	Describe with phasor, the Parallel operation of transformers with equal voltage ratios.	CO2	<i>P08, 9,12</i> 06
		c)	Explain the procedure for conducting Sumpner's test along with all precautions to be taken while conducting the test with neat diagram.	CO2	<i>P08, 9,12</i> 08

UNIT - III					
4	a)	For a 4 pole, 3 phase, 50 Hz Induction motor ratio of stator to rotor turns is 2. On a certain load, its speed is obtained to be 1455 rpm. When connected to 415 V supply. Calculate, (i) Frequency of rotor emf in running condition. ii) Magnitude of induced emf in the rotor at standstill.	CO3	P08, 9,12	10
	b)	Explain the Torque-Slip and Torque Speed characteristics of an 3-phase Induction motor	CO3	P08, 9,12	10
OR					
5	a)	A 24 pole, 50 Hz, star connected induction motor has rotor resistance of 0.016Ω per phase and rotor reactance of 0.265Ω per phase at standstill. It is achieving its full load torque at a speed of 247 rpm. Calculate the ratio of (i) full load torque to maximum torque. ii) Starting torque to maximum torque	CO3	P08, 9,12	10
	b)	List out the types of starters used for starting of 3 – phase induction motors. Explain any one method in detail.	CO3	P08, 9,12	10
UNIT - IV					
6	a)	Explain no load tests and blocked rotor tests for an 3-phase induction motor.	CO4	P08, 9,12	10
	b)	List out the factors affecting the performance of three phase induction motor.	CO4	P08, 9,12	10
UNIT - V					
7	a)	Name the types single phase Induction motor. Explain Split-phase starting methods of single induction motor.	CO4	P08, 9,12	10
	b)	Describe the construction and operating principle of single phase induction using double revolving field theory.	CO4	P08, 9,12	10
