

U.S.N.								
--------	--	--	--	--	--	--	--	--

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

January / February 2025 Semester End Main Examinations

Programme: B.E.

Semester: V

Branch: Electrical and Electronics Engineering

Duration: 3 hrs.

Course Code: 23EE5PCPEN

Max Marks: 100

Course: Power Electronics

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I			CO	PO	Marks
1	a)	Explain with a neat waveform any two types of power electronic circuits.	CO1	PO2	06
	b)	Explain diode (p-n junction) characteristics	CO1	PO2	07
	c)	Explain reverse recovery characteristics of a Diode.	CO1	PO2	07
OR					
2	a)	Explain the operation of single-phase diode bridge rectifier with R load along with waveform	CO3	PO2	07
	b)	A three-phase bridge rectifier has a purely resistive load of R . Determine (a) the efficiency, (b) the FF, (c) the RF, (d) the TUF, (e) the peak inverse (or reverse) voltage (PIV) of each diode, and (f) the peak current through a diode. The rectifier delivers $I_{dc} = 60$ A at an output voltage of $V_{dc} = 280.7$ V and the source frequency is 60 Hz.	CO4	PO3	07
	c)	Consider a single-phase full-wave rectifier with $L = 6.5$ mH, $R = 2.5 \Omega$, and $E = 10$ V. The input voltage is $V_s = 120$ V at 60 Hz. Determine (i) the steady-state load current I_0 at $\omega t = 0$, (ii) the average diode current $I_{D(av)}$, (iii) the rms diode current $I_D(rms)$, (iv) the rms output current $I_0(rms)$, and (v) the input power factor PF.	CO4	PO3	06
UNIT - II					
3	a)	What are power MOSFETs? With a neat structure, symbol explain the working of n-channel depletion type power MOSFET?	CO1	PO2	08
	b)	Explain why Isolation of gate drive circuits is required in case of MOSFETs ?	CO2	PO1, 2	07

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

	c)	Give the comparison between Power MOSFET and IGBT?	CO1	PO2	05
		OR			
4	a)	Explain the structure and working of IGBT?	CO1	PO2	08
	b)	Explain the structure and working of SiC MOSFET?	CO1	PO2	07
	c)	Explain the steady state characteristics of Enhancement type MOSFET?	CO2	PO1, 2	05
		UNIT - III			
5	a)	With a neat diagram explain the working principle and V-I characteristics of SCR?	CO2	PO1, PO2	10
	b)	A three-phase full-wave converter is operated from a three-phase Y-connected 208-V, 60-Hz supply and the load resistance is $R = 10 \Omega$. If it is required to obtain an average output voltage of 50% of the maximum possible output voltage, calculate (i) the delay angle α , (ii) the rms and average output currents, (iii) the average and rms thyristor currents, (iv) the rectification efficiency, (v) the TUF, and (vi) the input PF.	CO4	PO3	10
		OR			
6	a)	With a neat diagram and waveform explain the operation of single-phase full converter with RL load in continuous conduction mode?	CO3	PO2	10
	b)	The full converter is connected to a 120-V, 60-Hz supply. The load current I is continuous and its ripple content is negligible. The turns ratio of the transformer is unity. (i) Express the input current in a Fourier series; determine the HF of the input current, DF, and input PF. (ii) If the delay angle is $\alpha = \pi/3$, calculate V_{dc} , V_n , V_{rms} , HF, DF, and PF.	CO4	PO3	10
		UNIT - IV			
7	a)	With a neat diagram and waveform explain the working of step down DC-DC converter with RL load	CO3	PO2	08
	b)	Write the difference between DC-AC and DC-DC converter	CO3	PO2	04
	c)	The buck-boost regulator has an input voltage of $V_s = 12$ V. The duty cycle $k = 0.25$ and the switching frequency is 25 kHz. The inductance $L = 150 \mu H$ and filter capacitance $C = 220 \mu F$. The average load current $I_a = 1.25$ A. Determine (i) the average output voltage, V_a ; (ii) the peak-to-peak output voltage ripple, V_c ; (iii) the peak-to-peak ripple current of inductor, I ; (iv) the peak current of the transistor, I_p ; and (v) the critical values of L and C .	CO4	PO3	08

OR					
	8	a)	Draw the circuit diagram of ZVS resonant converter with its equivalent circuits, capacitor voltage and Inductor current waveform	CO3	PO2 08
		b)	Explain the working of a Buck-boost converter?	CO3	PO2 05
		c)	With a neat diagram and waveform explain the Fly-back converter?	CO3	PO2 07
UNIT - V					
	9	a)	With circuit diagram explain the operation of single-phase full bridge inverter supplying the R-load.	CO3	PO2 10
		b)	Explain the working of transistorized current source inverter?	CO3	PO4, 5,9 10
OR					
	10	a)	With a neat circuit diagram and waveform explain 180° mode of operation of a three-phase inverter. Give the expression for line and phase voltages for one cycle.	CO3	PO2 10
		b)	What is Multilevel Inverter? Explain two types of Multilevel inverters?	CO3	PO2 10
