

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## January / February 2025 Semester End Main Examinations

Programme: B.E.

Semester: V

Branch: Electrical and Electronics Engineering


Duration: 3 hrs.

Course Code: 23EE5PCPS1 / 22EE5PCPSA

Max Marks: 100

Course: Power System -1

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

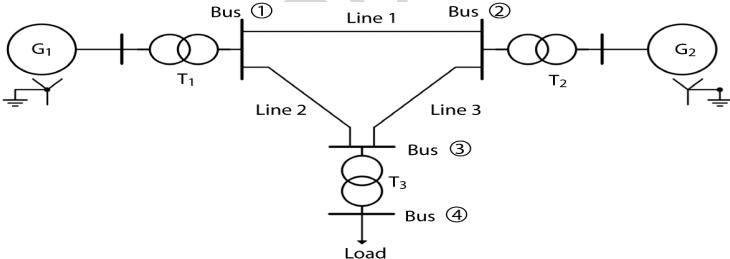UNIT - I			CO	PO	Marks																																
1	a)	<p>Derive an expression for the following:</p> <ol style="list-style-type: none"> <li>How will you change the base impedance from one set of base values to another set? (03M)</li> <li>Per unit value of a quantity on either side of transformer is same. (03M)</li> <li>Advantage the per unit value of a quantity. (04M)</li> </ol>	CO1	PO1	10																																
	b)	<p>Draw the per unit reactance diagram for the system shown in Fig. 1.b below. Choose a common base of 50 MVA, 110 kV.</p>  <p>Fig. 1.b</p> <table border="1"> <thead> <tr> <th>Items</th> <th>MVA</th> <th>kV (LL) n</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>Generator-1</td> <td>48 MVA</td> <td>20 kV</td> <td>20%</td> </tr> <tr> <td>Generator-2</td> <td>25 MVA</td> <td>13.8 kV</td> <td>15%</td> </tr> <tr> <td>Transformer-1(T1)</td> <td>50 MVA</td> <td>20/110 kV</td> <td>8%</td> </tr> <tr> <td>Transformer-2(T2)</td> <td>30 MVA</td> <td>13.8/110 kV</td> <td>6%</td> </tr> <tr> <td>Transformer-3(T3)</td> <td>50 MVA</td> <td>11/110 kV</td> <td>10%</td> </tr> <tr> <td colspan="4">Transmission line-1: 40 <math>\Omega</math>; Transmission line-2: 32 <math>\Omega</math></td></tr> <tr> <td colspan="4">Transmission line-3: 30 <math>\Omega</math>, Three phase load 60 MVA, 0.75pf lagging.</td></tr> </tbody> </table>	Items	MVA	kV (LL) n	X	Generator-1	48 MVA	20 kV	20%	Generator-2	25 MVA	13.8 kV	15%	Transformer-1(T1)	50 MVA	20/110 kV	8%	Transformer-2(T2)	30 MVA	13.8/110 kV	6%	Transformer-3(T3)	50 MVA	11/110 kV	10%	Transmission line-1: 40 $\Omega$ ; Transmission line-2: 32 $\Omega$				Transmission line-3: 30 $\Omega$ , Three phase load 60 MVA, 0.75pf lagging.				CO1	PO2	10
Items	MVA	kV (LL) n	X																																		
Generator-1	48 MVA	20 kV	20%																																		
Generator-2	25 MVA	13.8 kV	15%																																		
Transformer-1(T1)	50 MVA	20/110 kV	8%																																		
Transformer-2(T2)	30 MVA	13.8/110 kV	6%																																		
Transformer-3(T3)	50 MVA	11/110 kV	10%																																		
Transmission line-1: 40 $\Omega$ ; Transmission line-2: 32 $\Omega$																																					
Transmission line-3: 30 $\Omega$ , Three phase load 60 MVA, 0.75pf lagging.																																					
<b>OR</b>																																					
2	a)	<ol style="list-style-type: none"> <li>What is the need for base value?</li> <li>Write the equation for converting the p.u impedance expressed in one base to another.</li> <li>What are the approximations made in reactance diagram?</li> </ol>	CO1	PO1	10																																

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

	b)	<p>Draw the per unit reactance diagram for the system shown in Fig. 2 b below. Choose a base of 13.8 kV, 100 MVA in the generator circuit.</p> <p>Fig. 2 b</p>	CO1	PO2	<b>10</b>																																				
		<table border="1"> <thead> <tr> <th colspan="4">Data</th> </tr> <tr> <th>Items</th><th>MVA</th><th>KV</th><th>X</th></tr> </thead> <tbody> <tr> <td>Generator</td><td>90 MVA</td><td>13.8 kV</td><td>18%</td></tr> <tr> <td>Transformer-1(T1)</td><td>50 MVA</td><td>13.8/220 kV</td><td>10%</td></tr> <tr> <td>Transformer-2(T2)</td><td>40 MVA</td><td>220/11 kV</td><td>10%</td></tr> <tr> <td>Transformer-3(T3)</td><td>40 MVA</td><td>13.8/132 kV</td><td>10%</td></tr> <tr> <td>Transformer-4(T4)</td><td>40 MVA</td><td>132/11 kV</td><td>10%</td></tr> <tr> <td>Motor</td><td>80 MVA</td><td>10.45 kV</td><td>20%</td></tr> <tr> <td colspan="4">Three phase load 57 MVA, 0.8 pf lagging 10.45 kV</td></tr> </tbody> </table>				Data				Items	MVA	KV	X	Generator	90 MVA	13.8 kV	18%	Transformer-1(T1)	50 MVA	13.8/220 kV	10%	Transformer-2(T2)	40 MVA	220/11 kV	10%	Transformer-3(T3)	40 MVA	13.8/132 kV	10%	Transformer-4(T4)	40 MVA	132/11 kV	10%	Motor	80 MVA	10.45 kV	20%	Three phase load 57 MVA, 0.8 pf lagging 10.45 kV			
Data																																									
Items	MVA	KV	X																																						
Generator	90 MVA	13.8 kV	18%																																						
Transformer-1(T1)	50 MVA	13.8/220 kV	10%																																						
Transformer-2(T2)	40 MVA	220/11 kV	10%																																						
Transformer-3(T3)	40 MVA	13.8/132 kV	10%																																						
Transformer-4(T4)	40 MVA	132/11 kV	10%																																						
Motor	80 MVA	10.45 kV	20%																																						
Three phase load 57 MVA, 0.8 pf lagging 10.45 kV																																									
<b>UNIT - II</b>																																									
3	a)	Analyze and develop the doubling effect of the short circuit during symmetrical fault on a transmission line including wave forms.	CO2	PO2	<b>10</b>																																				
	b)	Two generators G1 and G2 are rated 15MVA, 11 kV and 10 MVA, 11 kV respectively. The generators are connected to a transformer as shown in Fig. 3 b. Calculate the sub transient current in each generator when a three-phase fault occurs on the high voltage side of the transformer.	CO2	PO2	<b>10</b>																																				
		<p>Fig. 3 b.</p>																																							
		<b>OR</b>																																							
4	a)	Analyze and develop expression for the maximum momentary current of the short circuit during symmetrical fault on a transmission line including waveforms.	CO2	PO2	<b>10</b>																																				

	b)	<p>A radial power system network is shown in Fig. 4 b. A three-phase balanced fault occurs at F. Determine the fault current and the line voltage at 11.8 kV bus under fault condition.</p>	CO2	PO2	<b>10</b>
		<b>UNIT - III</b>			
5	a)	<p>Analyze and develop the expression for:  i). Prove that a balanced set of three phase voltages will have only positive sequence components of voltages only. (05M).  ii). Complex power in terms of symmetrical components. (05M).</p>	CO2	PO2	<b>10</b>
	b)	<p>The line current in three - phase four wire system:  <math>I_a = 100\angle 30^\circ</math>; <math>I_b = 50\angle 300^\circ</math> and <math>I_c = 30\angle 180^\circ</math>  Evaluate the symmetrical components and the neutral current.</p>	CO2	PO2	<b>05</b>
	c)	<p>Draw the different configuration of transformer for zero sequence networks.</p>	CO2	PO2	<b>05</b>
		<b>OR</b>			
6	a)	<p>Analyze and develop expression for phase shift symmetrical components in Y-<math>\Delta</math> Transformer bank with positive, negative sequences voltage and current vector diagrams.</p>	CO2	PO2	<b>10</b>
	b)	<p>For the power system shown in Fig 6 b. with the data given, draw the zero sequence, positive sequence and negative sequence networks. Let base values be 50 MVA and 11 kV on generator side.</p>	CO2	PO2	<b>10</b>

<b>UNIT - IV</b>					
7	a)	Analyze and develop an expression for fault current, line current for line to line fault on unloaded generator through impedance. Draw the inter connection of sequence network.	<i>CO2</i>	<i>PO1</i>	<b>10</b>
	b)	<p>A 30 MVA, 13.2 kV synchronous generator has a solidly grounded neutral. Its positive, negative and zero sequence impedances are 0.30, 0.40 and 0.05 p.u respectively. Evaluate the following:</p> <ul style="list-style-type: none"> <li>a. What value of reactance must be placed in the generator neutral so that the fault current for a line to ground fault of zero fault impedance shall not exceed the rated line current?</li> <li>b. What value of resistance in the neutral will serve the same purpose?</li> <li>c. What value of reactance must be placed in the neutral of the generator to restrict the fault current to ground to rated line current for a double line to ground fault?</li> </ul>	<i>CO2</i>	<i>PO2</i>	<b>10</b>
<b>OR</b>					
8	a)	Analyze and develop an expression for fault current, line current for line to double line to ground fault on unloaded generator through impedance. Draw the inter connection of sequence network.	<i>CO2</i>	<i>PO1</i>	<b>10</b>
	b)	A 25 MVA, 13.2 kV alternator with solidly grounded neutral has a sub-transient reactance of 0.25 pu. The negative and zero sequence reactance are 0.35 and 0.1 pu, respectively. A line-to-line fault occurs at the terminals of an unloaded alternator. Neglecting resistance, determine the fault current and the line-to-line voltages.	<i>CO2</i>	<i>PO2</i>	<b>10</b>
<b>UNIT - V</b>					
9	a)	Analyze and develop the relation for Power-angle equation of a salient pole synchronous machine connected to an infinite bus and also draw the power angle curve.	<i>CO3</i>	<i>PO2</i>	<b>10</b>
	b)	Evaluate the SSSL of a system consisting of a generator of equivalent reactance 0.5pu connected to an infinite bus through a series reactance of 1.0 pu. The terminal voltage of the generator is held at 1.2 pu and voltage of the infinite bus is 1.0 pu.	<i>CO3</i>	<i>PO2</i>	<b>10</b>
<b>OR</b>					
10	a)	Analyze and develop an expression for application of Equal Area Criterion with the case of sudden change in input.	<i>CO3</i>	<i>PO2</i>	<b>10</b>
	b)	<p>Define the following:</p> <ul style="list-style-type: none"> <li>i. Stability.</li> <li>ii. Transient stability.</li> <li>iii. Steady state stability limit.</li> <li>iv. Swing curve.</li> <li>v. Power angle.</li> </ul>	<i>CO3</i>	<i>PO2</i>	<b>10</b>