

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

June 2025 Semester End Main Examinations

Programme: B.E.

Semester: VI

Branch: Electrical and Electronics Engineering


Duration: 3 hrs.

Course Code: 23EE6PCPS2

Max Marks: 100

Course: Power Systems-2

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

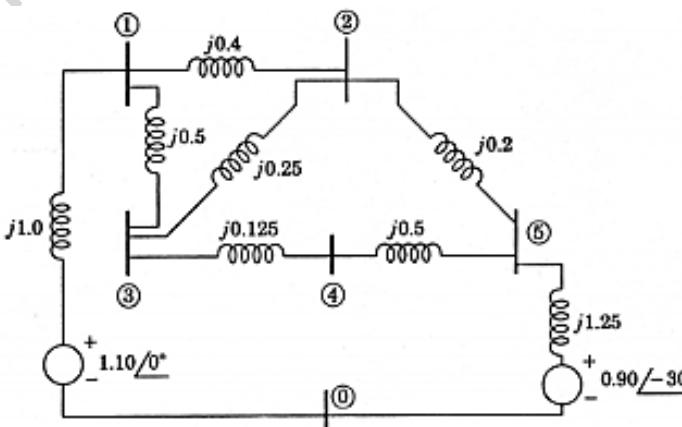UNIT - I						CO	PO	Marks						
1	a)	Define primitive network and get the performance equations in both admittance form and impedance form.						CO1	PO1	06				
	b)	For the Given data shown in Table. 1 (b), obtain Y_{bus} by inspection method.						CO2	PO2	14				
Table. 1 (b)														
OR														
2	a)	How an off-nominal turns ratio of a transformer is modeled while forming bus admittance matrix in power system.						CO1	PO1	08				
	b)	For a given diagram shown in Fig. 2 (b), obtain A, B, C and K.						CO1	PO2	12				
 <p>Fig. 2 (b)</p>														

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

UNIT - II

3 a) Derive an expression bus admittance matrix using singular transformation method. CO2 PO1 **06**

b) For a given data shown in Table. 3 (b), obtain Z_{bus} by building algorithm approach.

Element Number	Buses	Z (pu)
1	0-1	1.2 i
2	1-2	0.15 i
3	0-2	1.0 i
4	0-3	1.2 i
5	2-3	0.02 i

Table. 3 (b)

OR

4 a) Derive the generalized algorithm for finding the elements of bus impedance matrix when a link is added to the partial network. CO2 PO1 **06**

b) For the given data shown in Table 4. (b) Obtain Y_{bus} by singular transformation method. Take bus 1 as reference.

Line No.	p-q	Z (pu)	Mutual Z (pu)
1	1-2	0.6 i	--
2	1-3	0.5 i	0.2 i (1)
3	3-4	0.5 i	0.1 i (1)
4	1-2	0.4 i	--
5	2-4	0.2 i	--

Table 4. (b)

UNIT - III

5 a) Develop the Gauss-Seidel load flow model for a power system with a slack bus and (n-1) number of PQ buses. CO3 PO2 **06**

b) For a four-bus power system shown in Fig. 5 (b), generators are connected at all four buses while loads are at buses 2 and 3. Real and reactive powers are listed in the below Table 5. (b). Assuming flat voltage start, compute the voltages at all the buses at the end of first iteration using G.S. method. Take α as 1.4.

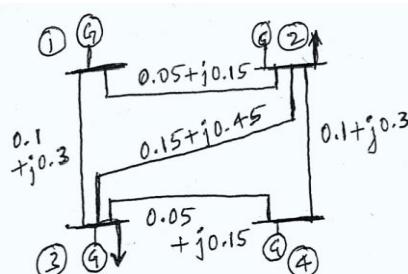
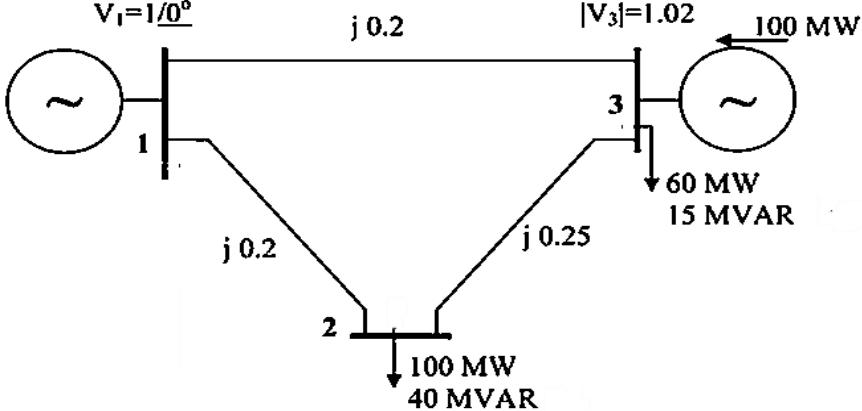
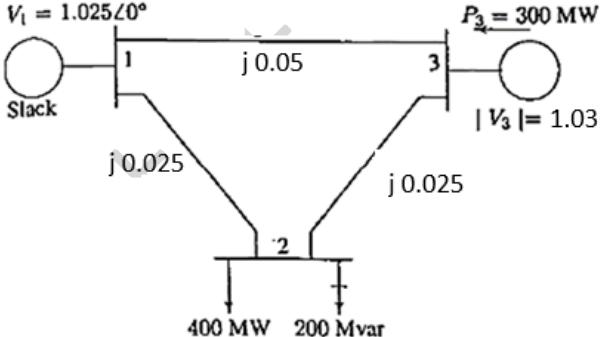


Fig. 5 (b)

Bus No.	P_i (pu)	Q_i (pu)	V_i (pu)
1	-		$1.04 0^\circ$
2	0.5	-0.2	-
3	-1	0.5	-
4	0.3	-0.1	-

Table 5. (b)

OR

6	a)	How buses are classified in power system? Explain the significance of Slack bus.	CO3	PO2	06
	b)	For the power system shown in Fig 6. (b), obtain voltages at all the buses after first iteration using G.S method. Line reactances are in p.u and Base MVA is 100. Given $0 \leq Q_{g_3} \leq 0.45$ pu.	CO3	PO3	14
		 <p>Fig 6. (b)</p>			
UNIT - IV					
7	a)	Explain the algorithm for fast decoupled load flow analysis, clearly stating all the assumptions made.	CO4	PO2	06
	b)	For the power system shown in Fig 7. (b), obtain diagonal elements of J1 and J4 in Jacobian matrix using N.R method. Line reactances are in p.u and Base MVA is 100.	CO4	PO4	14
		 <p>Fig 7. (b)</p>			
OR					
8	a)	Derive expressions for diagonal and off-diagonal elements of J1 matrices using NR method. Starting from power mismatch matrices.	CO4	PO2	06
	b)	For the power system shown in Fig 8. (b), obtain voltages at all the buses after first iteration using FDLF method. Consider a line is having half line charging admittance of j 1 pu.	CO4	PO4	14

		<p>Bus 1</p> <p>$z_{12} = 0.0 + j0.2 \text{ p.u.}$</p> <p>$V_1 = 1.06 + j0.0 \text{ p.u.}$</p> <p>$Pd_2 + jQd_2 = 0.8 + j0.4 \text{ p.u.}$</p>		
UNIT - V				
9	a)	Derive an expression for economic dispatch neglect losses.	CO5	PO2 08
	b)	Compute the loss co-efficient for the network shown in Fig.9 (b) $I_a = 1.6 - j0.4 \text{ pu}$ $Z_a = 0.15 \angle 85^\circ \text{ pu}$ $I_b = 2 - j0.5 \text{ pu}$ $Z_b = 0.15 \angle 78^\circ \text{ pu}$ $I_c = 1.8 - j0.45 \text{ pu}$ $Z_c = 0.25 \angle 85^\circ \text{ pu}$ consider $v_1 = 1.2 \angle 0^\circ \text{ pu}$ <p>Fig.9 (b)</p>	CO5	PO3 12
OR				
10	a)	Derive an expression for loss-co-efficient for a two-generating plant in economic operation of power systems.	CO5	PO2 08
	b)	Incremental Fuel Costs of Generators G1 and G2 are 10,000 Rs/MWh and 12,500 Rs/MWh respectively. Loss in the line is given by $P_{\text{loss}}(\text{pu}) = 0.5PG_1^2(\text{pu})$. Where the loss co-efficient is specified in p.u. on a 100 MVA base. Find economic scheduling for 40 MW load.	CO5	PO3 12
