

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

October 2023 Semester End Main Examinations

Programme: B.E.

Semester: I / II

Branch: Common to all Branches

Duration: 3 hrs.

Course Code: 21EC1ESBEC / 21EC2ESBEC

Max Marks: 100

Course: Basic Electronics and Communication Engineering

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may suitably assumed.

UNIT - I

1 a) Explain the working of full wave bridge rectifier with reservoir capacitor filter with the help of circuit diagram and waveform. **08**
b) Explain voltage regulator using zener diode? **06**
c) An amplifier produces an output voltage of 2 V for an input of 50 mV. If the input and output currents in this condition are, respectively, 4 mA and 200 mA, determine:
(a) the voltage gain;
(b) the current gain;
(c) the power gain. **06**

OR

2 a) Explain the working of the following circuits with the help of circuit diagram and wave form.
i. Voltage Follower
ii. Summing Amplifier **08**
b) Explain Wien Bridge Oscillator with circuit diagram and relevant expression. **07**
c) Determine the upper and lower threshold voltage, time period and frequency of the output waveform generated from Single-stage Astable oscillator with supply voltage of 15V, $R_1 = 2K\Omega$ and $R_2 = 1K$. (Assume $R = 10K\Omega$ and $C = 0.1\mu F$) **05**

UNIT - II

3 a) Illustrate the Full adder combinational logic circuit with truth table, Boolean expression and logic circuit. **05**
b) With the state table, explain the working of RS bistable realized using NOR gates. **05**
c) Explain the function of an 8-to-1 multiplexer and realize it using logic gates. **05**

d) Design an Asynchronous sequential circuit to get the square wave of frequency 12.5Hz from the input frequency of 100Hz. Also write the waveform. 05

UNIT - III

4 a) Describe the differences between RISC & CISC architecture. 06

b) Explain the different modes of operations of stepper motor with table indicating the sequence for energizing the coils. 07

c) Describe how matrix keyboard could be interfaced with 8051 microcontroller and explain its operation. 07

OR

5 a) Describe how characters are displayed in 7 segment display in common anode configuration along with the Binary and hexadecimal equivalents. 07

b) Define sensors and give its classification with examples. 06

c) Explain the working principle of UART with relevant diagram. 07

UNIT - IV

6 a) With a neat block diagram explain the components of the basic communication System. 08

b) Explain Frequency modulation with relevant waveforms. 04

c) Explain GSM System Architecture with neat diagram? 08

UNIT - V

7 a) Discuss different types of WSNs with examples. 07

b) Explain closed loop control of a personal lighting system. 06

c) Explain the role of WSN in Health care. Mention few applications. 07
