

U.S.N.								
--------	--	--	--	--	--	--	--	--

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## May 2023 Semester End Main Examinations

**Programme: B.E.**

**Semester: I**

**Branch: Common to all Branches**

**Duration: 3 hrs.**

**Course Code: 22EC1ESBEC**

**Max Marks: 100**

**Course: Basic Electronics**

**Date: 15.05.2023**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

1 a) Derive the expression for Ripple factor and efficiency of Bridge rectifier. **10**  
 b) What is a Regulated power supply? Explain with block diagram. **05**  
 c) Design a Zener regulator for following specification: Load current  $I_L = 30\text{mA}$  output voltage  $V_0 = 6.1\text{ V}$ , Zener wattage  $P_z = 400\text{mW}$ , Input voltage  $V_i = 16\pm2\text{V}$  and  $I_{Z\min} = 5\text{ mA}$ . **05**

**OR**

2 a) A half wave rectifier circuit is supplied from a 230V, 50Hz supply with a step-down ratio of 5:1 to a resistive load of  $1\text{k}\Omega$ . Diode forward resistance is  $50\Omega$ , while transformer secondary resistance is  $10\Omega$ . Calculate maximum, average, RMS value of current, DC output voltage, efficiency of rectification and ripple factor. **10**  
 b) Discuss the impact of using capacitor filter in a Bridge Rectifier with the help of circuit diagram and waveform. **06**  
 c) Determine the values of maximum and minimum values of Zener diode current for the circuit shown in Figure 1. **04**

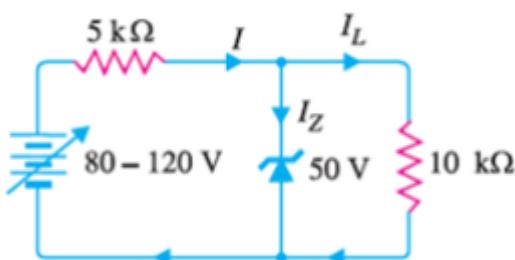


Figure 1

### UNIT - II

3 a) A circuit needs to switch ON and OFF an LED. Construct the circuit using BJT and explain the same. **07**

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

b) Identify the following V-I characteristics shown in Figure 2 and comment on the operation of circuit used to get same. **08**

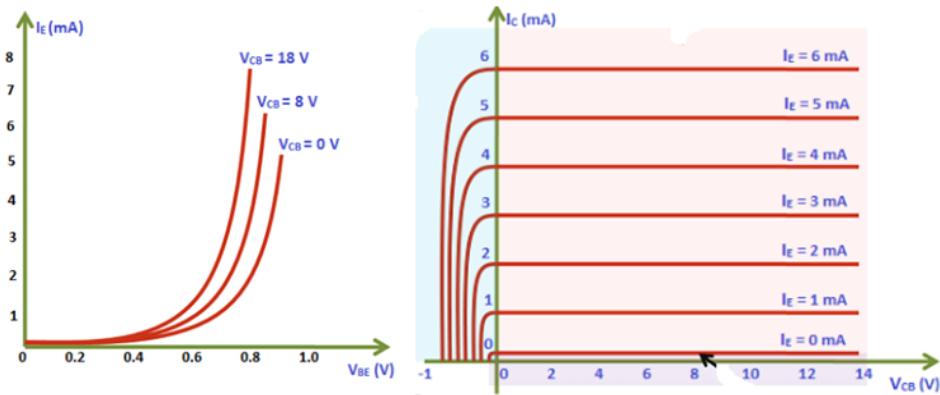


Figure 2

c) An amplifier has a bandwidth of 500 kHz and a voltage gain of 1000. **05**

- What will be the new bandwidth and gain if 10% negative feedback is introduced?
- What is the gain bandwidth product with and without feedback? Comment on the same.

### UNIT - III

4 a) Draw the circuit diagram of Hartley oscillator and explain its operation. **06**

b) Design a single op-amp circuit that performs amplified average function with a gain of 5. Draw the circuit diagram and clearly mark all the resistors values. **06**

c) Derive the expression for output voltage of an Op-Amp differentiator with a diagram. When a sine wave of 1V peak at 2kHz is applied to the circuit with the following specification:  $R_F = 1k\Omega$  and  $C_1 = 0.47\mu F$ , find its output waveform and its output equation. **08**

### UNIT - IV

5 a) Design a combinational circuit to implement full adder in terms of logic gates. **06**

b) (i) Simplify  $f(W, X, Y, Z) = \bar{W}XY\bar{Z} + XY\bar{Z} + X\bar{Y}\bar{Z} + X\bar{Y}Z$  using Boolean laws and realize using only NAND gates. **08**

(ii)  $f(A, B, C) = AB + \bar{A}BC + A\bar{C} + \bar{A}\bar{B}C$  using Boolean laws and realize using only basic gates.

c) Explain the working of SR flip-flop with the help of truth table and circuit. **06**

### OR

6 a) Discuss the different states of JK flip-flop with the help of circuit and truth table. **06**

b) Perform the following: (i) Convert the number  $(C69.5)_{16}$  to octal  
(ii) Convert  $(567.42)_8$  to decimal  
(iii) Convert  $f(A, B, C) = (A + \bar{B})(\bar{A} + C)$  into standard POS  
(iv) Prove that  $AB + C(\overline{A \oplus B}) = AB + BC + CA$  **08**

c) Discuss the universality of NAND and NOR gates. **06**

## UNIT - V

7 a) A 15KHz audio signal is used to frequency modulate a 100MHz carrier, causing a carrier deviation of 75KHz. Determine Modulation Index and Carrier swing. **04**

b) Discuss the components of a Receiver with relevant diagram and explain each of its function. **06**

c) Discuss in detail concept of cellular telephone system and evolution from 1G to 4G. **10**

\*\*\*\*\*