

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## August 2023 Semester End Make-Up Examinations

**Programme: B.E.**

**Semester: I**

**Branch: Common to all Branches**

**Duration: 3 hrs.**

**Course Code: 22EC1ESBEC**

**Max Marks: 100**

**Course: Basic Electronics**

**Date: 11.08.2023**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

1 a) Explain the forward and reverse biased condition of PN junction Diode. **05**  
 b) Derive the expression for Ripple factor and efficiency of Half-wave rectifier. **10**  
 c) Design a Zener regulator for following specification: Load current  $I_L = 20\text{mA}$  output voltage  $V_0 = 5\text{ V}$ , Zener wattage  $P_z = 500\text{mW}$ , Input voltage  $V_i = 12+2\text{V}$  and  $I_{Z\min} = 8\text{ mA}$ . **05**

### OR

2 a) What is a Regulated power supply? Explain with a block diagram. **05**  
 b) Derive the expression for Ripple factor and efficiency of Bridge rectifier. **10**  
 c) For a Silicon Diode working at a Temperature of  $250\text{C}$ , the forward voltage applied across the diode is  $0.5\text{V}$ , determine its forward current, if the reverse saturation current is  $10\text{nA}$ . **05**


### UNIT - II

3 a) With a neat diagram, explain the input and output characteristics of a transistor in common emitter configuration. **10**  
 b) Derive the expression for gain of positive and negative feedback systems. An amplifier has midband gain of 125 and a bandwidth of  $250\text{KHz}$ . If 4% negative feedback is introduced, find the new bandwidth and gain. If bandwidth is restricted to  $1\text{MHz}$ , find the feedback ratio. **10**
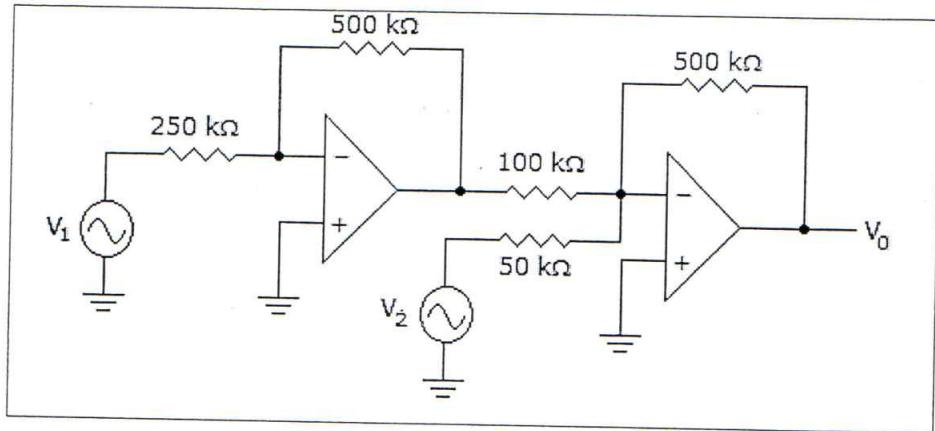
### UNIT - III

4 a) Explain operational amplifier with a neat block diagram. **05**  
 b) The equivalent electrical parameter of a crystal oscillator is  $L=3\text{H}$ ,  $C=0.05\text{pF}$ ,  $C_p=6\text{pF}$ , and  $R=1\text{K}\Omega$ . Determine the series resonant frequency and the percentage by which the parallel resonant frequency exceeds the series resonance frequency. **08**  
 c) Calculate the output voltage of the circuit shown in figure, if  $V_1 = 300\text{ mV}$  and  $V_2 = 700\text{ mV}$ . Also mention how the op-amp is configured. **07**

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.




#### UNIT - IV

5 a) Implement half adder using basic gates 05  
 b) Perform the following conversion 10  
 (i)  $(25.6)_{10} = ( )_2 = ( )_H$   
 (ii)  $(7BEF)_H = ( )_{10} = ( )_2 = ( )_8$   
 c) A logic circuit has 3 inputs A, B, C and one output Y. Y=B XOR C when A=0, and Y=C when A=1. Simplify the output expression and realize the same using logic gates 05

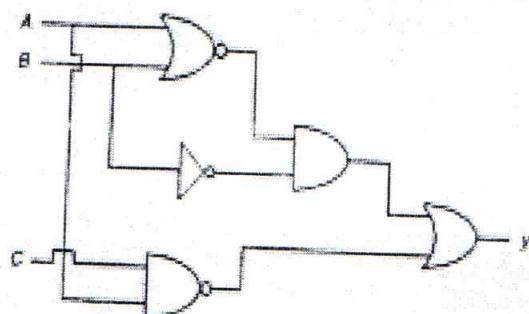**OR**

6 a) Analyze the logic circuit shown in fig. Determine the Boolean function for y and state its truth table. 06



b) Design Full Adder circuit using 2 Half adders. 08  
 c) Design a logic circuit using a minimum number of NOR gates to implement the following expression. 06

$$f(A, B, C) = \bar{A}B + B\bar{C} + BC + A\bar{B}\bar{C}$$

#### UNIT - V

7 a) With a neat block diagram, explain the components of the basic communication System. 10  
 b) Define Signal to Noise Ratio and Noise Factor with relevant equation. At a receiver of a communication system, the signal and noise voltages are given as 3.5mV and 0.75mV respectively. Determine the SNR in dB. 05  
 c) Discuss different types of computer communication networks based on their size. 05

\*\*\*\*\*