

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

May 2023 Semester End Main Examinations

Programme: B.E.

Branch: Common to all Branches

Course Code: 18EC1ESECE / 18EC2ESECE

Course: Elements of Electronics Engineering

Semester: I / II

Duration: 3 hrs.

Max Marks: 100

Date: 13.05.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
 2. Missing data, if any, may suitably assumed.

UNIT - I

1 a) Draw V-I Characteristics of diode and Indentify knee voltage and breakdown voltage on it. Define Knee voltage, breakdown voltage and PIV. **05**

b) Derive the efficiency of a rectifier which has a ripple factor of 0.48 and PIV of individual diode is V_m . Draw the rectifier circuit. **10**

c) A half wave rectifier is used to supply 50 V DC to a resistance load of $800\ \Omega$. The diode has a resistance of 25Ω . Calculate maximum ac voltage required (Assume diode is ideal). **05**

OR

2 a) Describe how zener diode used as voltage regulator. **07**

b) Explain how capacitor filter is used to reduce the ripple content of rectifier output. **06**

c) Derive the expression for ripple factor of a full wave rectifier. **07**

UNIT - II

3 a) Discuss the voltage divider biasing for transistor amplifier with relevant equations. **08**

b) Draw the circuit diagram of RC coupled transistor amplifier and explain its operation. Draw the frequency response curve of RC coupled amplifier. **08**

c) The collector current of a transistor is 100 mA and β is 75. Calculate the value of base current and emitter current. **04**

UNIT - III

4 a) Explain the working principle of RC phase shift oscillator using neat circuit diagram. **08**

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

b) Describe how OP-AMP can be used as i) Summing Amplifier ii) Integrator **08**
 c) For an inverting amplifier $R_i=100\text{ K}\Omega$ and $R_f=600\text{ K}\Omega$. What is the output voltage for an input of -3V ? **04**

UNIT - IV

5 a) Simplify and realize using NAND gate only. **06**
 i) $y = ABC + AB'C + ABC' + A'BC$
 ii) $y = AB + A'BC + AC + A'B'C$
 b) Design a full adder using two half adders. **08**
 c) Explain the operation of JK Flip flop using state table. **06**

OR

6 a) Simplify the below expression using K-Map. **06**
 i) $F = xy' + x'y'z + xyz'$
 ii) $F = a'b'c' + a'bc' + a'bc + ab'c + abc$
 b) Implement a 4x1 multiplexer using 2x1 Mux. Explain the concept. **06**
 c) Design a full adder using 3 to 8 decoder. **08**

UNIT - V

7 a) Explain the digital communication system using block diagram. **08**
 b) Briefly discuss the concept of Internet of things using suitable block diagram. **08**
 c) What is GPS system ? Explain **04**
