

U.S.N.								
--------	--	--	--	--	--	--	--	--

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## May 2023 Semester End Main Examinations

**Programme: B.E.**

**Semester: I**

**Branch: Common to all Branches**

**Duration: 3 hrs.**

**Course Code: 22EC1ESIEL**

**Max Marks: 100**

**Course: Introduction to Electronics Engineering**

**Date: 19.05.2023**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

1	a) Explain block diagram of regulated power supply with neat diagram.	10
	b) With the help of neat circuit diagram and waveforms, explain Bridge Rectifier.	07
	c) List out disadvantages of half wave rectifier.	03

### OR

2	a) With a neat diagram, explain the input and output characteristics of a transistor in common base configuration.	08
	b) Deduce the relationship between various Transistor currents and also $\alpha$ and $\beta$ of a transistor. In a common emitter transistor circuit, if $\beta = 100$ and $IB = 50\mu A$ , compute the values of $\alpha$ , $IE$ and $IC$ .	07
	c) An amplifier has mid-band gain of 125 and a bandwidth of 250 KHz. If 4% negative feedback is introduced, find the new bandwidth and gain. If bandwidth is restricted to 1MHz, find the feedback ratio.	05


### UNIT - II

3	a) Summarize the desirable characteristics of an Operational amplifier.	05
	b) Draw the circuit diagram of an OPAMP voltage follower and explain. What are the reasons for using a voltage follower?	08
	c) Draw and explain the OPAMP Wein Bridge Oscillator.	07

### UNIT - III

4	a) Convert $(0.513)_{10}$ to octal number.	04
	b) Analyze the logic circuit shown in fig. Determine the Boolean function for $y$ and state its truth table.	06

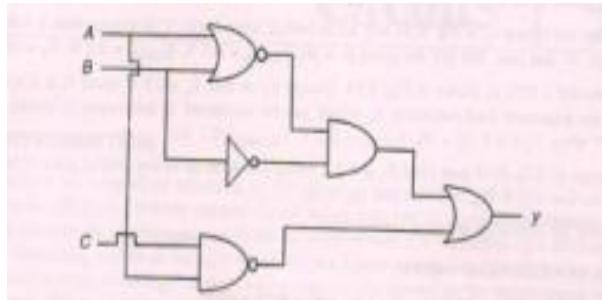**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.



c) List all the postulates and Theorems of Boolean Algebra. **10**

**OR**

5 a) Write the truth table and gate level logic diagram for the full adder, realize the same using Half adders. **10**

b) A logic circuit has 3 inputs A, B, C and one output Y.  $Y = B \text{ xor } C$  when  $A=0$ , and  $Y=C$  when  $A=1$ . Simplify the Boolean expression using Boolean laws. **05**

c) Realize all basic gates using NOR gates. **05**

**UNIT - IV**

6 a) What is an embedded system? How do you differentiate between embedded systems with general computing systems? **10**

b) With the help of block diagram explain (i) An instrumentation system and (ii) A control system. **10**

**UNIT - V**

7 a) With the help of a block diagram explain the Digital Communication system. **09**

b) Discuss the evolution of cellular communication system. **06**

c) Distinguish between different types of networks used in Computer networks. **05**

\*\*\*\*\*