

**Dept of ECE,BMSCE**  
**Course: Basic Electronics and Communication**

**Unit II**

# UNIT 2

## Logic Gates

- Logic Systems consists of Gates and Flip-flops
- Logic gates are electronic circuits designed to produce the basic logic functions such as AND, OR, etc.
- Flip-flops are memory devices capable of storing logic constants.
- The Interconnection of Gates and Flip-flops results in Logic Networks.

# Logic Gate Symbols



OR



NOR




AND



NAND



XOR

 

XNOR



Buffer



NOT

# Buffers:

- Buffers do not affect the logical state of a digital signal.
- A logic 1 input results in a logic 1 output whereas a logic 0 input results in a logic 0 output.
- Buffers are used to provide extra current drive at the output.
- The Boolean expression for the output :  $Y = X$ .

Logic Diagram




Truth Table

X	Y
0	0
1	1

# Inverters

- Inverters are used to complement the logical state.
- A logic 1 input results in a logic 0 output and vice versa.
- The Boolean expression for the output, Y, of an Inverter with an input, X, is:  $Y = \overline{X}$

Logic Diagram

 

Truth Table

X	Y
0	1
1	0

# AND Gate:

- AND gates will only produce a logic 1 output when all inputs are simultaneously at logic 1.
- Other input combination results in a logic 0 output.
- The Boolean expression for the output,  $Y = A \cdot B$

Logic Diagram



Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

# OR Gate

- OR gates will produce a logic 1 output whenever any one, or more, inputs are at logic 1.
- OR gate will only produce a logic 0 output whenever all of its inputs are at logic 0.
- The Boolean expression for the output,  $Y = A + B$

Logic Diagram



Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

# NAND Gate:

- NAND (i.e. NOT-AND) gates will only produce a logic 0 output when all inputs are simultaneously at logic 1.
- Other input combination will produce a logic 1 output.
- A NAND gate, is an AND gate with its output inverted. The circle shown at the output denotes this inversion.
- The Boolean expression for the output:  $Y = \overline{A \cdot B}$

Logic Diagram



Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

# NOR Gate

- NOR (i.e. NOT-OR) gates will only produce a logic 1 output when all inputs are simultaneously at logic 0.
- Other input combination will produce a logic 0 output.
- A NOR gate, is an OR gate with its output inverted. A circle is used to indicate inversion.
- The Boolean expression for the output.  $Y = \overline{A + B}$

Logic Diagram



Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

# EX-OR Gate

- A two input Exclusive-OR gates will produce a logic 1 output, whenever either one of the inputs is at logic 1 and the other is at logic 0.
- Exclusive-OR gates produce a logic 0 output whenever both inputs have the same logical state (i.e. when both are at logic 0 or both are at logic 1).
- The Boolean expression for the output,  $Y$ , of an exclusive-OR gate with inputs  $A$  and  $B$  is: 
$$Y = A \cdot \overline{B} + B \cdot \overline{A}$$

Logic Diagram



Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# EX-NOR Gate

- A two input Exclusive-NOR gates will produce a logic 1 output, whenever both of its inputs are same otherwise it produces logic 0 output.
- The Boolean expression for the output, Q, of an exclusive-NOR gate with inputs A and B is:  $Q = (A \cdot B) + (\bar{A} \cdot \bar{B})$

Logic Diagram      Truth Table



A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

# Adder

- An adder is a device that will add together two bits and give the result as the output.
- There are two kinds of **adders** - **half adders** and **full adders**.
  - A half adder just adds two bits together and gives a two-bit output.
  - A full adder adds two inputs and a carried input from another adder, and also gives a two-bit output.

# Half adder

The circuit adds two binary variables, yields a carry but does not accept carry from another circuit (adder).

The truth table of the half adder with its circuit is shown below.


Truth table:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

S = Sum; C = Carry

$$S = \bar{A}B + A\bar{B} = A \oplus B$$
$$C = AB$$

Logic Diagram

 

# Full adder


- Full Adder is the **adder which adds three inputs and produces two outputs.**
- The first two inputs are A and B and the third input is an input carry,  $C_i$ .
- The output carry is given as  $C_o$  and the normal output as S which is SUM.

Truth Table of Full adder

Row No.	A	B	$C_i$	S	$C_o$
1	0	0	0	0	0
2	0	0	1	1	0
3	0	1	0	1	0
4	0	1	1	0	1
5	1	0	0	1	0
6	1	0	1	0	1
7	1	1	0	0	1
8	1	1	1	1	1
 
# Full adder ...


- It is observed from the truth table that  $C_0=1$  for rows which have two 1's otherwise it is 0.
- Its Boolean Function is  $C_0=AB+BC_i+C_iA$
- It can be implemented by three AND and one OR gates.  $S=1$  for rows with one 1 and three 1's., i.e odd number of 1's. its implemented by a three input XOR.



# Multiplexer

Multiplexer is to select one signal from a group of  $2^n$  inputs, and map on to a single output line.

 - Example: 2:1, 4:1, 8:1
- Block diagram of an 8:1 Multiplexer is shown below.
- Lines  $D_0, D_1, \dots, D_7$  are the data input lines and  $F$  is the output line, Lines  $A, B$  and  $C$  are called select lines.




# Multiplexer Implementation


Select Lines			O/P
A	B	C	F
0	0	0	$D_0 \rightarrow \overline{A} \overline{B} \overline{C} D_0$
0	0	1	$D_1 \rightarrow \overline{A} \overline{B} C D_1$
0	1	0	$D_2 \rightarrow \overline{A} B \overline{C} D_2$
0	1	1	$D_3 \rightarrow \overline{A} B C D_3$
1	0	0	$D_4 \rightarrow A \overline{B} \overline{C} D_4$
1	0	1	$D_5 \rightarrow A \overline{B} C D_5$
1	1	0	$D_6 \rightarrow A B \overline{C} D_6$
1	1	1	$D_7 \rightarrow A B C D_7$

Select Lines			O/P
A	B	C	F
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$


□ A=0 B=0 C=0

 


□ A=0 B=0 C=1

 

□ A=1 B=0 C=1

 

# Multiplexer logic diagram

 


# Multiplexer Application

- To choose one of the several Inputs
- $2^n : 1$  multiplexer can be used to Implement Boolean function with  $n$  variables by associating each input line with a row of truth table.

 
# Decoder

- It decodes an  $n$ -bit binary number, producing a signal on one of  $2^n$  output lines.
- If input  $A=1$ ,  $B=0$ ,  $C=1$  , the output  $D_5$  is 1 and all other outputs are 0.



# Truth table of 3-to-8 decoder

# Decoder logic diagram

 


# Decoder application

- A decoder with an Enable line can be used as a **De-Multiplexer**, which directs a single data line to one of the  $2^n$  output lines
- Decodes memory address for read or write operation of RAM

 
# COMBINATIONAL LOGIC CIRCUITS

- A combinational logic circuit is defined as a circuit in which the outputs at any instant are dependent only upon the inputs present at that instant.
- Examples – Adders, subtractors, decoders, multiplexers.


 
# SEQUENTIAL LOGIC CIRCUITS



- A sequential circuit is defined as a circuit in which the outputs at any instant are dependent not only upon the present inputs, but also upon the past history or sequence of inputs.
- In order to preserve past history of inputs, sequential circuits are said to have *memory*.



Examples include counters,  
registers etc.
  
# BISTABLES

- All memory elements consist of a basic bistable element.
- The basic bistable element has two stable conditions or states.



# BISTABLES


- As a result of having two stable conditions, the basic bistable element is used to store binary symbols.
- In the case of positive logic, when the output line  $Q$  is 1, the element is said to be storing 1.
- When the output line  $Q$  is 0, the element is said to be storing 0.
- The two outputs are complementary.

When  $Q=0$ ,  $\bar{Q} = 1$

When  $Q=1$ ,  $\bar{Q}=0$





# R-S BISTABLES

- 

 


- The simplest form of bistable is the R-S bistable.
- This device has
  - two inputs SET and RESET
  - complementary outputs Q and  $\bar{Q}$ .
- A logic 1 applied to the SET input will cause the Q output to become (or remain at) logic 1
- A logic 1 applied to the RESET input will cause the Q output to become (or remain at) logic 0.
- The bistable will remain in its present state until the application of another input.

# OPERATION OF AN R-S BISTABLE

    


# OPERATION OF AN R-S BISTABLE

 


- The above analysis yields contradictory results
- Hence,  $R=1, S=1$  is an invalid and forbidden state
- R-S bistable cannot be used when both the inputs are at logic 1

# TRUTH TABLE OF R-S BISTABLES

 

INPUTS		OUTPUTS		COMMENTS
S	R	$Q_{N+1}$	$\bar{Q}_{N+1}$	
0	0	Q	$\bar{Q}$	Memory
0	1	0	1	Reset
1	0	1	0	Set
1	1	?	?	Forbidden

 
# $\bar{S}$ - $\bar{R}$ BISTABLE USING NAND GATES



INPUTS		OUTPUTS		COMMENTS
$\bar{S}$	$\bar{R}$	$Q_{N+1}$	$\bar{Q}_{N+1}$	
0	0	?	?	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	$Q$	$\bar{Q}$	Memory

 
# D-TYPE BISTABLES

- The D-type bistable has two inputs: D (standing for ‘data’ or ‘delay’) and CLOCK (CLK).
- D-type bistable is a modified Set-Reset bistable with the addition of an inverter to prevent the S and R inputs from being at the same logic level.



 
# WORKING OF A D-TYPE BISTABLE

- The D-type bistable consists of
  - Input D that determines its next state and control.
  - Input clock that determines when the D input is effective.




# WORKING OF A D-BISTABLE

When clock=0

 

When clock=1, D=0

 


→

INPUTS		OUTPUTS		COMMENTS
S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	Memory
0	1	0	1	Reset
1	0	1	0	Set
1	1	?	?	Forbidden

# WORKING OF A D-TYPE BISTABLE

When  $\text{clock}=1$ ,  $\text{D}=1$

 


→

INPUTS		OUTPUTS		COMMENTS
S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	Memory
0	1	0	1	Reset
1	0	1	0	Set
1	1	?	?	Forbidden

# TRUTH TABLE OF D-TYPE BISTABLE


INPUTS		OUTPUTS		COMMENTS
CLOCK	D	Q	$\overline{Q}$	
0	X			Memory
1	0	0	1	Reset
1	1	1	0	Set

# TIMING DIAGRAM FOR A D-TYPE BISTABLE

 

 
# J-K BISTABLES

- J-K bistables have
  - two clocked inputs (J and K),
  - two direct inputs (PRESET and CLEAR),
  - a CLOCK input,
  - outputs (Q and  $\bar{Q}$ ).
- A 0 on the PRESET input will set the Q output to 1 whereas a 0 on the CLEAR input will set the Q output to 0



 
# INPUT AND OUTPUT STATES (PRESET AND CLEAR INPUTS)




INPUTS		OUTPUT	COMMENTS
CLEAR	PRESET		
0	0	?	Indeterminate
0	1	0	Q is reset
1	0	1	Q is set
1	1	Clocked operation	Enables clocked operation
 
# INPUT AND OUTPUT STATES (CLOCKED OPERATION)




INPUTS		OUTPUT	COMMENTS
J	K		
0	0	Q	No change in state of the Q output
0	1	0	Q is reset
1	0	1	Q is set
1	1		Q output changes to the opposite state

# CLOCKED OPERATION OF A J-K BISTABLE

 

INPUTS		OUTPUT	COMMENTS
J	K		
0	0	Q	No change in state of the Q output
0	1	0	Q is reset
1	0	1	Q is set
1	1		Q output changes to the opposite state

# CLOCKED OPERATION OF J-K BISTABLE

 


INPUTS		OUTPUT	COMMENTS
J	K		
0	0	Q	No change in state of the Q output
0	1	0	Q is reset
1	0	1	Q is set
1	1		Q output changes to the opposite state

# J-K Bistables can be configured in various ways

- Binary Dividers
- Binary Counters
- Shift Registers
 
# Data Representation and Microcontroller System



# Data Representation


- **Binary(Base 2)**

- Large binary numbers are inconvenient to handle
- Hence convert to hexadecimal

- **Hexadecimal(Base 16)**

- Easy to comprehend
- Offers advantage over decimal (base 10)
- Conversion from binary to hexadecimal and vice versa is easy
- A single hexadecimal character(range is 0 to F) represents 4 binary digits

# Nibble, byte, word, double word

 

**Nibble**-A group of 4 bits or single hex character

**Byte**- A group of 8 bits  
Represented by 2 hex characters

**WORD**-A group of 16 bits

Represented by four hexadecimal characters

**Double word** –A group of 32 bits

Represented using 8 hex characters

groups of  
four bits  
(nibble)-


- Each  
hexadecim  
al number  
is

=100 in  
decimal  
\$7FH =

- add H to  
Ex. A3 in  
Hex = 1010  
0011 in  
binary
- 11101000  
in binary

## Binary, Denary, Hex Table

Binary	Denary	Hexadecimal
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	8
1001	9	9
1010	10	A
1011	11	B
1100	12	C
1101	13	D
1110	14	E
1111	15	F

 

# Data Types

- One byte of data can be stored at each address of the memory space in a microprocessor
- For a 16 bit address bus, total memory locations =65,536
- Within a byte, bits are numbered 0 (Least Significant Bit) to 7(Most Significant Bit)
- For 16 bit words, 15 is the MSB bit
- Negative(signed) numbers are represented using 2's complement notation.
- Here MSB indicates the sign of the number(1=negative, 0= positive)
- Only bits 0 to 6 represent the magnitude of the number
- Ex: signed 8 bit number 10000001 = -1(denary)

# Range of Integer Data values

Data type	Bits	Range of values
Unsigned byte	8	0 to 255
Signed byte	8	-128 to +127
Unsigned word	16	0 to 65,535
Signed word	16	-32,768 to +32,767

# Data Storage

- Semiconductor ROM
  - Provides storage for the program code
  - Stores any permanent data
  - These are non-volatile
  - They remain intact when power supply is off
- Semiconductor RAM
  - Provides storage for transient data, variables used by the program
  - Part of RAM temporarily stores data while doing normal tasks
- CMOS RAM
  - Data stored in RAM is lost when power switched off
  - In CMOS RAM, data is kept alive using a small battery
  - It retains important data- time and date


# Data Storage

- The data stored in the memory device is represented in kilobytes(KB)
- 1 Kilobyte = 1024 bytes . It is nearest power of 2. ( $2^{10} = 1024$ )
- Semiconductor ROM capacity = address range \* number of bits stored at each address
- Ex: 2k x 8 bits(2KiloBytes) , 4k x 8 bits (4 Kilobytes)

# Microcontroller system



# Microcontroller system

 

# Typical Microcontroller system

- The sensed quantities(temperature, position) are converted to electrical signals using sensors
- Sensor outputs are either digital or analogue in nature
- These signals passed to microcontroller. Microcontroller also accepts user options
- Software instructions control the operation of the microprocessor and output signals sent to controlled devices
- Controlled device converts electrical energy from one form into another form
- In real world, systems are self regulating called closed loop system  
Ex. Heating control system

# Typical Microcontroller system

- Micro controllers have a CPU which performs arithmetic, logical and timing operations
- Some input sources are switches, sensors, keypads
- Some output devices are LED indicators, LED 7 segment displays, motors and actuators, relays, transistor drivers and other solid-state switching devices

# Input devices

- Input device is keyboard, mouse scanner and modem
- Switches or contacts which make and break
- Sensors which provide logic level outputs
- To connect an input device to a microcontroller, the device must provide a logic compatible signal.
- In microcontroller inputs can only accept digital input signals  
0v= logic 0 and 5v = logic 1 signal
- Some devices sense analogue quantities
- Some microcontrollers provide ADC and provide digital data.
- Resolution of the ADC depends on the number of bits used (8, 10 or 12 bits)

# Output devices


- They are used to communicate information to the outside world
- Common output devices are flat screen display, printers and modems
- Microcontroller uses output devices such as LEDs, piezoelectric sounders, relays and motors
- DAC are required at the output of the microcontroller
- The resolution of the DAC also depends on the number of bits

# Interface Circuit


- When the output and input signals are not logically compatible interface circuits are needed
- Also, when a load requires more current than is available from standard logic device or output port
- They provide the additional current drive

Ex: Interface circuits allow a microcontroller to interface to an AC mains connected load. To control a central heating system
 
# Ex: An analog input signal connected to a microcontroller via ADC



 
# Ex: An analog output signal produced by connecting DAC to microcontroller



# Shift Register

- Registers are the devices used to store multiple bits of information
- Flip-flops are used to store 1-bit of information, for n-bit of information to be stored in the registers, registers use n-number of flip-flops.
- Using the shift registers along with storing the information, stored information can be read parallel or series.
- Shift registers are used to write/read the information either in series(1-bit at a time) or in parallel (all bits of data at a time).
 
## Block diagram of shift register (SISO):



- JK flip-flop with active low Preset and Clear is used to construct the 4-bit shift register.
- Negative edge of the clock is used to trigger the operation of the flip-flops
- 4-bit data of 1010 is sent to the shift register serially (1-bit per clock) through serial in. Data 1010 is fed in with LSB first
- Each bit is shifted to the through the 4 flip-flops and output through serial out after the occurrence of 4 negative edges of the clock.

# Operation of Shift Register:

Clock pulse	Serial in	$Q_3$	$Q_2$	$Q_1$	$Q_0$ (serial out)	
0	0	0	0	0	0	
1	1	1	0	0	0	
2	0	0	1	0	0	
3	1	1	0	1	0	Data entered
4	0	0	1	0	1	
5	0	0	0	1	0	
6	0	0	0	0	1	
7	0	0	0	0	0	1 Register cleared


# Register types

- Serial In Serial Out(SISO)
- Serial In Parallel Out (SIPO)
- Parallel In Serial Out(PISO)
- Parallel In Parallel Out(PIPO)
 
# Register types


- Parallel out – output connections taken from Q3 to Q0
- Parallel in – After clearing the FFs, “Parallel in” is set ‘1’. Data fed simultaneously on D3-D0

Any  $D_i$  input causes  
 $D_i = 0, P_r = 1$  and  $Q_i = 0$   
 $D_i = 1, P_r = 0$  and  $Q_i = 1$



 
# Shifting of Data to Left

- Previously, the data was shifted from left by one bit at clock pulse by feeding output at FF0 to input FF1, and FF1 to FF2, FF2 to FF3.
- In the below fig, On the occurrence of a pulse, the data word will shift one bit to left.



# Bidirectional Shift Registers

 

# Counters

- A counter is a circuit that counts the number of occurrence of an input.
- Each count, a binary number, is called a state of the counter.
- A counter counting in terms of **n-bits** has  **$2^n$**  different states.
- The number of different states of a counter is known as the modulus of the counter. Thus an n-bit counter is a **modulo- $2^n$**  counter.
- Counter circuits are primarily constituted of **flip-flops**, along with **combinational elements** are used for the generation of counter signals.

# Counters

Counter can be divided into two major categories:


1. **Asynchronous counter (Ripple counter)**: all the flip-flops are not clocked simultaneously.
2. **Synchronous counter**: all the flip-flops are clocked simultaneously.

# Asynchronous Counters

The below figure shows a 3-bit (modulo 8) asynchronous counter.

**Operation:** All the flip flops are initially cleared. The clock pulses are then applied.

 - With each negative edge of the clock pulse (1 to 0), Q0 toggles.
- For each negative edge (1 to 0) of Q0, Q1 toggles.
- Similarly for 1 to 0 transition of Q1 , Q2 toggles.




# Operation of Asynchronous Counter

Input (Clock)	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0
 
# Observation

- The 3-bit counter counts the 8-clock pulses, negative edge occurs at  $Q_0$  4 times,  $Q_1$  2 times and  $Q_3$  1 time.
- The frequency of the clock pulse reduces by a factor of 2 at each stage.



# Counters

- **Down counter:**  $\bar{Q}$ s are connected to the next flip-flop. As  $\bar{Q}$  toggles from 1 to 0, the corresponding Q toggles 1 to 0, which is count down.
- **Up-down counter:** For up/down count, CK is connected to Q and  $\bar{Q}$  through AND-OR logic.