

**B.M.S. College of Engineering, Bengaluru-560019**

Autonomous Institute Affiliated to VTU

**September 2024 Supplementary Examinations****Programme: B.E.****Semester: I / II****Branch: Common to all Branches****Duration: 3 hrs.****Course Code: 22EC1ESBEC / 22EC2ESBEC****Max Marks: 100****Course: Basic Electronics**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
 2. Missing data, if any, may be suitably assumed.


<b>UNIT – I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>
1	a)	Explain the V-I characteristics of PN junction diode with Shockley's equation.	-	-	<b>6</b>
	b)	Derive the expression for Ripple factor and efficiency of Half-wave rectifier.	<i>CO1</i>	<i>PO1</i>	<b>8</b>
	c)	The diode current is 0.6mA when the applied voltage is 500mV. Determine the $\eta$ , assume $V_T=25mV$ .	<i>CO1</i>	<i>PO1</i>	<b>6</b>
<b>OR</b>					
2	a)	Explain the forward and reverse biased condition of PN junction Diode.	-	-	<b>4</b>
	b)	Arrive at the expression for Ripple factor and efficiency of Bridge rectifier.	<i>CO1</i>	<i>PO1</i>	<b>10</b>
	c)	For a Zener regulator $R=2.2K\ \Omega$ , $R_L=1K\ \Omega$ , calculate the range of input voltage for which output will remain constant. $V_Z=6.1V$ , $I_{Zmin}=2.5mA$ , $I_{Zmax}=25mA$ , $R_z=0\ \Omega$ . 6 Marks	<i>CO1</i>	<i>PO1</i>	<b>6</b>
<b>UNIT – II</b>					
3	a)	Deduce the relationship between various Transistor current and also $\alpha$ and $\beta$ of a transistor. In a common emitter transistor circuit, if $\beta = 100$ and $I_B = 50\mu A$ , compute the values of $\alpha$ , $I_E$ and $I_C$ .	<i>CO1</i>	<i>PO1</i>	<b>10</b>
	b)	With a neat diagram, explain the input and output characteristics of a transistor in common emitter configuration.	-	-	<b>10</b>
<b>UNIT - III</b>					
4	a)	Derive the expression of the output of an Op-Amp Integrator with a neat circuit diagram.	<i>CO1</i>	<i>PO1</i>	<b>5</b>
	b)	Draw the output waveform of an Op-Amp <ul style="list-style-type: none"> <li>i. If square wave is given at the differentiator input.</li> <li>ii. If triangular wave is given at the differentiator input</li> </ul>	<i>CO1</i>	<i>PO1</i>	<b>5</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 Revealing of identification, appeal to evaluator will be treated as malpractice.

	c)	<p>i .The transistor RC phase shift oscillator has three RC sections with <math>C = 0.01\mu F</math> and <math>R = 6.3 K\Omega</math>. If <math>R_L = 4.7k\Omega</math>. Determine the frequency of oscillation.</p> <p>ii. What is the frequency of Hartley oscillator if the total inductance of <math>L_1</math> and <math>L_2</math> is <math>50mH</math> and the capacitance of the resonant circuit is <math>200pF</math>?</p>	CO 1	PO1	5 +5
--	----	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------	-----	------

### UNIT - IV

5	a)	With the state table, explain the working of SR Flip-flop realized using NAND gates.	-	-	5
	b)	<p>Perform the following conversion</p> <p>(i) <math>(25.6)_{10} = ( )_2 = ( )_H</math></p> <p>(ii) <math>(7BEF)_H = ( )_{10} = ( )_2 = ( )_8</math></p> <p>(iii) <math>(57279)_{10} = ( )_{16}</math></p>	CO 1	PO1	10
	c)	Design Full Adder circuit using 2 Half adders.	CO 3	PO3	5
<b>OR</b>					
6	a)	With the state table, explain the working of JK Flip-flop realized using NAND gates.	-	-	5
	b)	<p>Perform the following</p> <p>i. <math>(532.65)_{10} = ( )_{16}</math></p> <p>ii. <math>(250.67)_{16} = ( )_2 = ( )_{10}</math></p> <p>iii. <math>(952.01)_{10} = ( )_{16} = ( )_8</math></p>	CO1	PO1	10
	c)	Analyze the logic circuit shown in figure below. Determine the Boolean function for $y$ and state its truth table.	CO2	PO2	5

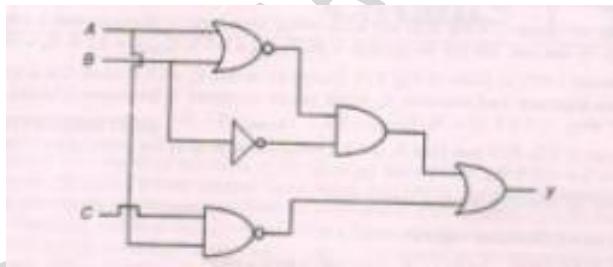

### UNIT – V

7	a)	Explain the different types of modulation techniques with relevant Waveforms. Mention the modulation index of AM and FM wave.	-	-	4
	b)	A 100MHz carrier wave is frequency modulated by a 10KHz sinusoidal modulating signal. If the maximum frequency deviation is 50KHz, Compute the modulation index and also find Carrier Swing.	CO1	PO1	4
	c)	Write a short note on (i) Cellular communication system (ii) computer communication network. (iii) Compare 1G, 2G, 3G and 4G technologies of cellular communication.	-	-	12

\*\*\*\*\*