

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

December 2023 Supplementary Examinations

Programme: B.E.

Branch: Electronics and Communication Engineering

Course Code: 22EC3PCAEC

Course: Analog Electronic Circuits

Semester: III

Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1 a) Identify the type of clipper, analyse the given circuit and represent the waveforms. **05**

 


Fig-1

b) Design a suitable circuit represented by the box shown below which has the input and output waveforms as indicated for a frequency of 1KHz. **05**

 
 
 


Fig-2

c) Explain frequency response of BJT RC coupled amplifier. Derive expression for higher cut off frequency considering the effect of device capacitors, miller capacitance and parasitic/stray wiring capacitors. **10**

UNIT - II

2 a) Identify the feedback mechanism in Fig3. Deduce an expression for gain, input impedance and output impedance for the same. **08**

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

 


Fig-3

b) Determine the transformer turns ratio required to match a 16Ω speaker load so that the effective load resistance seen at the primary is $10\text{ k}\Omega$. **04**

c) Deduce an expression for efficiency of a Class B power amplifier. What are the drawbacks of the same? **08**

UNIT - III

3 a) Briefly describe the working of an enhancement type MOSFET under following conditions: **10**

- With application of Small V_{DS}
- Operation of the device as V_{DS} is increased

b) Design the circuit shown in the fig 4 such that the transistor operates at $I_D=0.4\text{mA}$ and $V_D=0.5\text{V}$. The NMOS transistor has $V_t=0.7\text{V}$, $k_n=100\mu\text{A/V}^2$, $L=1\mu\text{m}$ and $W=32\mu\text{m}$. Assume $\lambda=0$ **10**

 


Fig-4

OR

4 a) With the help of neat cross sectional view describe the structure of a CMOS. **05**

b) Illustrate the significance of biasing a MOSFET using drain to gate feedback resistor. **05**

c) Consider an n-channel MOSFET with $tox = 20\text{ nm}$, $\mu_n = 650\text{ cm}^2/\text{V} \cdot \text{s}$, $V_t = 0.8\text{ V}$, and $W/L = 10$. Find the drain current in the following cases:

- $V_{GS} = 5\text{ V}$ and $V_{DS} = 1\text{ V}$.
- $V_{GS} = 2\text{ V}$ and $V_{DS} = 1.2\text{ V}$.
- $V_{GS} = 5\text{ V}$ and $V_{DS} = 0.2\text{ V}$.
- $V_{GS} = V_{DS} = 5\text{ V}$.

10

UNIT - IV

5 a) Deduce an expression for small signal voltage gain of an enhancement MOSFET as an amplifier. **10**
b) With supportive diagrams derive an expression for overall voltage gain of a grounded gate amplifier. **10**

UNIT - V

6 a) Briefly describe the working of the differential pair in Common Mode and Differential Mode. **10**
b) Determine the output V_o for the Adder-Subtractor circuit shown in Fig-5. Represent the equivalent circuits at each stage. **10**

 


Fig 5

OR

7 a) It is required to convert a voltage signal to a proportional output current for a certain application. Suggest and describe the different types of converters with necessary equations and circuits. **10**
b) Suggest a suitable circuit to generate a symmetric square wave generator. Deduce an expression for the total time period for the same. **10**
