

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## October 2024 Supplementary Examinations

**Programme: B.E.**

**Branch: Electronics and Communication Engineering**

**Course Code: 23EC3PCAEC**


**Course: Analog Electronic Circuits**

**Semester: III**

**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.
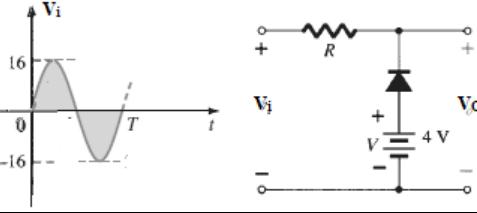
<b>UNIT - I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>
1	a)	Analyse voltage divider circuit using exact method.	<i>CO 3</i>	<i>PO2</i>	<b>5</b>
	b)	What is clamper? Explain the operation of positive clamper with equations and draw the input output waveforms.	<i>CO 1</i>	-	<b>6</b>
	c)	Determine the dc bias voltage $V_{CE}$ and the current $I_C$ for the voltage divider configuration given $R_1 = 39 \text{ k}\Omega$ , $R_2 = 3.9 \text{ k}\Omega$ , $R_C = 10 \text{ k}\Omega$ , $R_E = 1.5 \text{ k}\Omega$ , $V_{CC} = 22\text{V}$ and $\beta = 100$ . Draw the DC loadline.	<i>CO 2</i>	<i>PO 1</i>	<b>9</b>
<b>OR</b>					
2	a)	Derive the expression for $Z_i$ , $Z_o$ , $A_v$ , using $r_e$ model in a common Emitter voltage divider bias configuration.	<i>CO 2</i>	<i>PO 1</i>	<b>9</b>
	b)	Analyse the working of the clipping circuit shown. Draw the output waveform and transfer characteristics. Assume the diode as ideal.	<i>CO 3</i>	<i>PO 2</i>	<b>6</b>
	c)	 Explain the significance of coupling and the bypass capacitors in a CE amplifier.	<i>CO 1</i>	-	<b>5</b>
<b>UNIT - II</b>					
3	a)	Explain the different types of feedback used in amplifiers.	<i>CO 1</i>	-	<b>8</b>
	b)	For an amplifier, the midband gain is 100 and lower cut-off frequency is 1kHz. Calculate the gain of the amplifier at frequency of 20 Hz.	<i>CO 2</i>	<i>PO 1</i>	<b>4</b>
	c)	Obtain the expression for gain, input resistance and output resistance for a voltage series feedback amplifier.	<i>CO 2</i>	<i>PO 1</i>	<b>8</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

<b>UNIT - III</b>						
4	a)	Explain the classification of power amplifiers	<i>CO 1</i>	-	<b>8</b>	
	b)	With a neat circuit diagram, explain the operation of complementary symmetry Class B push-pull amplifier and show that its maximum conversion efficiency is 78.5%.	<i>CO 2</i>	<i>PO 1</i>	<b>8</b>	
	c)	What is distortion in power amplifiers? Define harmonic distortion.	<i>CO 1</i>	-	<b>4</b>	
<b>UNIT - IV</b>						
5	a)	State the disadvantage of fixed $V_{GS}$ biasing technique and explain how stability of operating point is achieved in drain to gate feedback resistor biasing technique in a MOSFET amplifier.	<i>CO 1</i>		<b>8</b>	
	b)	Determine the values of $R_S$ and $R_D$ for the circuit shown so that the transistor operates at $V_{DD} = -V_{SS} = 2.5V$ , $I_D = 0.3$ mA and $V_D = +0.4$ V. The NMOS transistor has $V_t = 1$ V, $\mu_n C_{ox} = 60$ $\mu\text{A/V}^2$ and $W/L = 40$ . Neglect the channel-length modulation effect (i.e., assume that $\lambda = 0$ ).	<i>CO 2</i>	<i>PO 1</i>	<b>6</b>	
	c)	Compare the n-channel and p-channel enhancement type MOSFET characteristics	<i>CO 2</i>	<i>PO 1</i>	<b>6</b>	
<b>UNIT - V</b>						
6	a)	Draw the conceptual MOSFET amplifier circuit and derive the expression for drain current $i_D$	<i>CO 2</i>	<i>PO 1</i>	<b>8</b>	
	b)	Explain the basic MOSFET amplifier configurations.	<i>CO 1</i>	-	<b>6</b>	
	c)	A MOSFET is to operate at $I_D = 0.1$ mA and is to have $g_m = 1$ mA/V. If $k_n' = 50$ mA/V $^2$ . Find the required (W/L) ratio and the overdrive voltage.	<i>CO 2</i>	<i>PO 1</i>	<b>6</b>	
<b>OR</b>						
7	a)	Analyze the circuit of common drain amplifier and derive the expressions for no-load voltage gain, overall voltage gain, input resistance and output resistance.	<i>CO 3</i>	<i>PO 2</i>	<b>8</b>	
	b)	For the circuit shown in figure, derive the expression for $R_{in}$ , $R_o$ , $A_v$ and $A_{vo}$ using T- Model	<i>CO 2</i>	<i>PO 1</i>	<b>6</b>	
	c)	Explain the operation of Wilson MOS Mirror	<i>CO 2</i>	-	<b>6</b>	

\*\*\*\*\*