

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## June 2025 Semester End Main Examinations

**Programme: B.E.**

**Branch: Electronics and Communication Engineering**

**Course Code: 22EC3PCAEC**

**Course: Analog Electronic Circuits**

**Semester: III**


**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

UNIT - I			CO	PO	Marks
1	a)	Determine the output waveform for the sinusoidal input of the figure1.	CO2	PO1	06
	b)	Determine input impedance, output impedance and voltage gain from ac equivalent circuit of a voltage divider biasing of BJT.	CO2	PO1	06
	c)	Analyze voltage divider bias circuit using exact analysis.	CO1	-	08
<b>OR</b>					
2	a)	For the following transfer characteristics in figure 2 identify and analyze the circuit, also obtain the output wave form if the input wave form is $10\sin\omega t$ .(assume Si diode)	CO3	PO2	8
	b)	For CE amplifier with voltage divider bias, calculate $r_e$ , $Z_i$ , $Z_o$ , $A_v$ , $A_i$ if $R_1=47K\Omega$ , $R_2=8.2K\Omega$ , $R_C=6.2K\Omega$ , $R_E = 1.5K\Omega$ , $\beta=90$ .	CO3	PO2	12
<b>UNIT - II</b>					
3	a)	Write the block diagram of the following indicating $A$ , $A_f$ and $\beta$ .	CO1	-	10

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

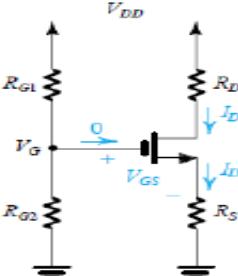		i) Voltage series feedback amplifier (ii) Voltage shunt feedback amplifier (iii) Current series feedback amplifier and (iv) Current shunt feedback amplifier.			
	b)	Describe the working principle of a class A transformer coupled power amplifier circuit. Show that maximum power conversion efficiency is 50% for class A power amplifier.	CO2	PO1	10
	<b>OR</b>				
4	a)	With a neat diagram and waveforms, explain the working of complementary symmetry class B power amplifier. Also derive an expression for conversion efficiency.	CO1	-	12
	b)	A voltage series feedback amplifier has $R_B=50\text{ k}\Omega$ , $R_C=2.7\text{ k}\Omega$ , $R_E=600\Omega$ , $V_{CC}=15\text{ V}$ , $h_{FE}=200$ , $h_{IE}=1000\text{ }\Omega$ . Calculate (1) $A_V$ & $A_{VF}$ (2) $R_i$ & $R_{if}$ (3) $R_o$ & $R_{of}$ .	CO2	PO1	8
	<b>UNIT - III</b>				
5	a)	Analyse biasing by fixing $V_{GS}$ in a MOSFET with $i_D$ - $V_{GS}$ characteristics.	CO3	PO2	08
	b)	Design the circuit in Fig 3 to establish a DC drain current $I_D=0.5\text{ mA}$ . The MOSFET is specified to have $V_t=1\text{ V}$ and $k_nW/L=1\text{ mA/V}^2$ . For simplicity neglect the channel-length modulation effect. Use a power supply $V_{DD}=15\text{ V}$ . Calculate the percentage change in the value of $I_D$ obtained when the MOSFET is replaced with another unit having the same $k_nW/L$ but $V_t=1.5\text{ V}$	CO4	PO3	08
	 <p>Fig 3</p>				
	c)	Derive the expression for the signal current in the drain terminal for small signal operation with the help of a neat conceptual amplifier circuit.	CO2	PO1	04
	<b>OR</b>				
6	a)	With the neat circuit diagram, Explain the biasing of MOSFET using a Drain to Gate feedback resistor.	CO1	-	08
	b)	Analyze the circuit in Fig 4 and determine its small-signal voltage gain, its input resistance and the largest allowable input signal. The transistor has $V_t=1.5\text{ V}$ , $k_nW/L=0.25\text{ mA/V}^2$ and $V_A=50\text{ V}$ . Assume the coupling capacitors to be sufficiently large so as to act as short circuits at the signal frequencies of interest.	CO3	PO2	08

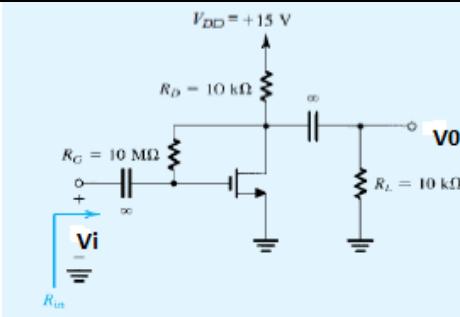


Fig 4

c) Derive the expression for the voltage gain of a MOSFET amplifier. Draw the instantaneous waveforms of  $V_{GS}$  and  $V_{DS}$ .

**UNIT - IV**

7 a) Derive the expression for  $R_{in}$ ,  $A_v$ ,  $A_{v0}$ ,  $G_m$  and  $R_0$  for CS amplifier for small signal analysis.

b) Analyze the three different relationships for determining transconductance  $g_m$ .

**OR**

8 a) Derive the expression for input resistance, output resistance, voltage gain and overall voltage gain of a common gate MOSFET amplifier

b) With suitable diagrams and equations deduce an expression for current gain in a current mirror circuit.

**UNIT - V**

9 a) With a neat circuit diagram, explain Instrumentation amplifier using op-amp.

b) With a neat functional diagram, explain the working of 555 timer as an Astable multivibrator. Derive the expression for time period and duty cycle.

**OR**

10 a) Find the output voltage for the circuit shown in the figure 5

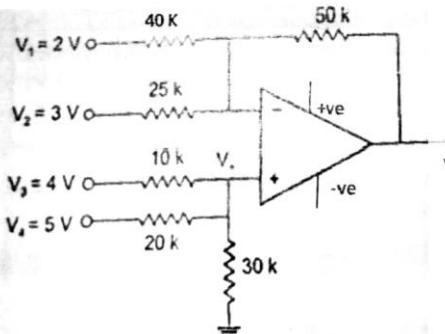


Fig 5

b) With a neat block diagram explain Phase Locked Loop

\*\*\*\*\*