

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

June 2025 Semester End Main Examinations

Programme: B.E.

Semester: IV

Branch: Electronics and Communication Engineering


Duration: 3 hrs.

Course Code: 23EC4PCAIC

Max Marks: 100

Course: Analog Integrated Circuits

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

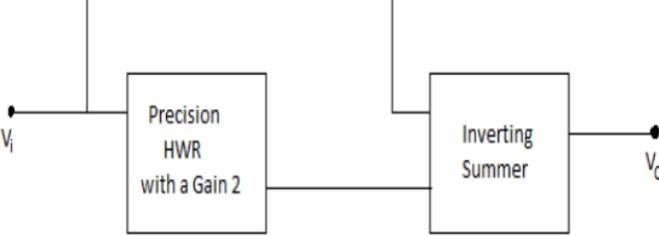UNIT - I			CO	PO	Marks
1	a)	<p>Explain the following parameters that specify the characteristics of typical op-amp 741:</p> <ul style="list-style-type: none"> i) Input bias current ii) Input offset current iii) Input offset voltage 	1		6
	b)	<p>What are the advantages of Instrumentation amplifier over differential amplifier? Draw the circuit diagram and prove that the gain of the instrumentation amplifier is $(1+2R'/R)$ times the differential gain.</p>	2	1	7
	c)	<p>Identify the following block diagram shown in figure 1c, write the circuit for the same and obtain the output equation and waveform.</p> 	3	2	7
figure 1c					
OR					
2	a)	<p>Draw the circuit of a voltage to current converter and explain the working of the circuit if the load is i) floating and ii) grounded</p>	1		6
	b)	<p>Analyze the circuit shown in figure 2b and arrive at the equation for output voltage considering all resistors are same.</p>	3	2	6

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

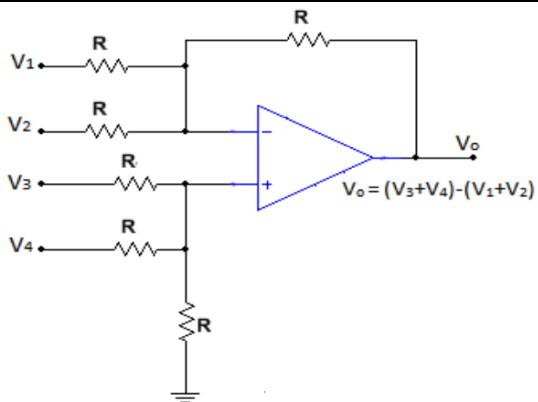


figure 2b

c) Explain the external frequency compensation techniques with relevant equation and circuit diagram.

UNIT - II

3 a) Assume an input of $V_{in}=6\sin\omega t$ and draw the output waveforms and transfer characteristics for the following circuits.
 (a) Inverting comparator with $V_{ref}=+3V$, $V_{ref}=-3V$, $V_{ref}=0V$.
 (b) Non inverting comparator with $V_{ref}=+3V$, $V_{ref}=-3V$, $V_{ref}=0V$

b) With a neat circuit diagram, explain the working of inverting Schmitt trigger along with input-output waveforms, transfer characteristics, when UTP=+2 V, LTP=-2V.

c) Explain simple op-amp as square wave generator with relevant waveforms.

OR

4 a) Construct the circuit that requires gain of 3 and $R_F=2R_1$ to produce sustained oscillations. Also derive the gain equation.

b) i) Illustrate the working of a wave generator circuit shown in figure 4b which produces an output waveform by integrating a square wave.
 ii) Assume that for the circuit $R_1=100K\Omega$, $R_2=10K\Omega$, $R_3=20K\Omega$, $C_1=0.01\mu F$ and $\pm V_{sat}=\pm 14V$ for the op-amps. Determine
 a) Period b) Frequency c) Peak value of triangular wave

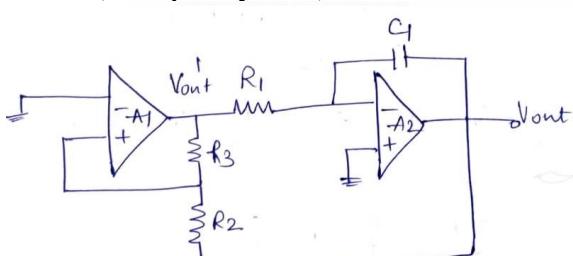
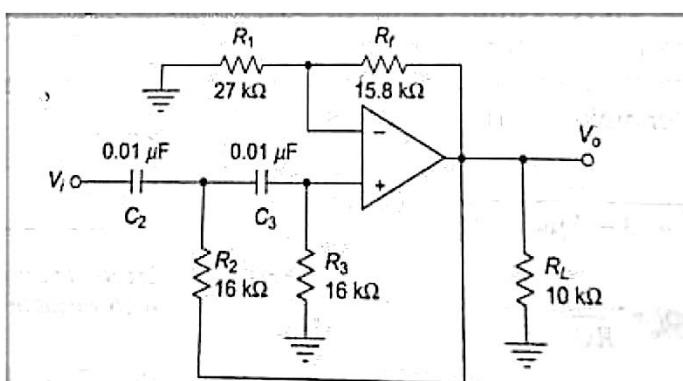
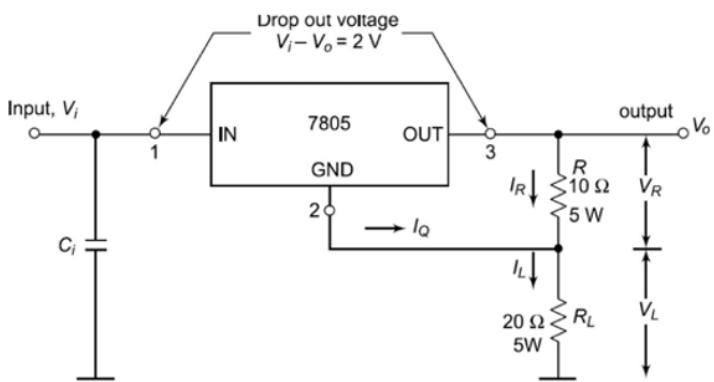


figure 4b

UNIT - III

5 a) Explain a regulated power supply using appropriate circuit.

	b)	With the diagram explain low voltage regulator using 723 IC	1		7
	c)	Design a 2 nd order Butterworth low pass filter having upper cutoff frequency of 2KHz. Assume C=0.1 μ F and $\alpha = 1.414$.	4	3	7
		OR			
6	a)	Explain how fixed regulator can be used as adjustable regulator.	1		6
	b)	Find the lower cut-off frequency f_L for the second order high-pass Butterworth filter shown in figure 6b. Also, find the passband gain of the filter and plot the frequency response of the filter.	2	1	7
					
		Figure 6b			
	c)	Using 7805 voltage regulator, design a current source to deliver 250 mA current to a 10 W, 3W load.	4	3	7
					
		UNIT - IV			
7	a)	With block diagram and an example explain the working of Successive approximation ADC.	1		8
	b)	A dual slope ADC uses a 16-bit counter and a 4 MHz clock rate. The maximum input voltage is +10V. The maximum integrator output voltage should be -8V when the counter has cycled through 2^n counts. The capacitor used in the integrator is 0.1 μ F. Find the value of the resistor R of the integrator.	2	1	6
	c)	What output voltage would be produced by a D/A converter whose output is 0 to 10V and whose input binary number is (i)10 (for a 2-bit D/A converter)	2	1	6

		(ii) 0110 (for a 4-bit DAC) (iii) 10111100 (for an 8-bit DAC)			
OR					
	8	a) With a neat circuit diagram and truth table, explain the working of binary weighted resistor DAC	1		6
		b) An 8 bit ADC accepts an input voltage signal of range 0 to 10 V. a. What is the minimum value of input voltage required to generate a change of 1 LSB? b. What input voltage will generate all 1s at the A/D converter o/p? c. What is the digital output for an applied input voltage of 4.8V?	2	1	7
		c) A counting ADC uses a 7bit DAC. The MSB of the output voltage is +5V. i) If analog input voltage is +6.85 V, what will be the R-2R ladder output voltage when the clock stops? ii) What is the number of clock pulses that occur between the release of reset and stopping of the clock?	2	1	7
UNIT - V					
	9	a) With a neat functional diagram and pin diagram explain the working of 555 monostable multivibrator. Draw the relevant waveforms.	1		10
		b) Design an astable multivibrator using 555 timer IC to have 5kHz as the output frequency and also to have (a) D=60% (b) D=40%. Assume C=0.01 μ F.	4	3	10
OR					
	10	a) Explain with relevant block diagram the operation of IC 566 VCO.	1		10
		b) Identify the circuit in figure 10b and show that with introduction of diode, how same circuit can be used for adjustable duty cycle with appropriate equations.	3	2	10

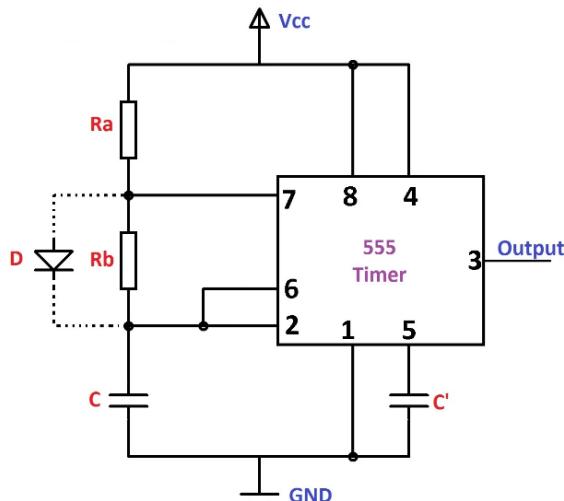


figure 10b
