

U.S.N.								
--------	--	--	--	--	--	--	--	--

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

September / October 2023 Supplementary Examinations

Programme: B.E

Branch: Electronics and Communication Engineering

Course Code: 19EC4PCHDL

Course: HDL Programming

Semester: IV

Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1	a)	Design a 4-to-16 decoder using 2-to-4 decoders with enable using bottom-up design methodology	06
	i.	Draw the logic block diagram.	04
	ii.	Code the same in Verilog HDL.	
	b)	Design a Verilog module for a D flipflop and write a testbench to verify the functionality. Also show the expected waveforms.	10

UNIT - II

2	a)	Use only Verilog logical, ternary and shift operators to perform following operations. Assume A=4'b1110; B=8'b11010010.	02
	i.	A divided by 2 and A multiplied by 2	02
	ii.	Arithmetic right shift on B once and Logical left shift on A twice	02
	iii.	Implement 'Y' as an output that selects 'A' when S=0 and selects 'B' when S=1	02
	b)	Implement an S-R latch in Verilog using dataflow modeling. Also write a testbench to verify the functionality of the same.	06
	c)	Design a Gate-level schematic for a 2-input unsigned multiplier and implement the same in Verilog using Gate-level modeling.	08

UNIT - III

3	a)	Write a task that generates output 'Y' =1 when input 'X' is high for 3 clock cycles. The output 'Y' must be high for one clock cycle.	08
	b)	Design a N-Bit Parallel Adder using generate block, using the 1-bit full adder as a building block.	06
	c)	Write a Verilog code for 3-bit universal shift register.	06

OR

4	a)	The table given below shows the logic to generate 'Y', where A, B, C, D are inputs:	
---	----	---	--

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.


A	B	C	D	Y[2]	Y[1]	Y[0]
X	X	1	X	0	1	0
X	1	0	X	0	0	1
X	0	0	1	0	1	1
1	0	0	0	1	0	0
0	0	0	0	0	0	0

i. Write the behavioural description for the output 'Y' as per the above table using ternary operators only. **05**

ii. Implement the output 'Y' as per the above table using the appropriate case construct. **05**

iii. If the last condition (for inputs: A=0, B=0, C=0, D=0) were not specified in the above table, how would the Verilog code be written using if-else-if statements? **05**

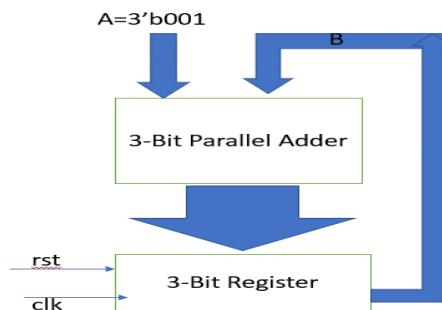b) For the circuit given below, write the Verilog behavioral code. **05**



UNIT - IV

5 a) Draw the equivalent logic circuit for the given code-1 and code-2. **10**

CODE-1	CODE-2
module SYNTH_CODE1(A,B,C,D);	module SYNTH_CODE1(A,B,C,D);
input A,B,C;	input A,B,C;
output reg D;	output reg D;
<u>always@(posedge C or posedge B)</u>	<u>reg Q;</u>
begin	<u>assign D = B ? 1'b0:Q;</u>
if(B) D <= 1'b0;	<u>always@(posedge C)</u>
else D <= A;	<u>Q <= A;</u>
end	<u>endmodule</u>
endmodule	

b) Observe the code below and draw the equivalent logic circuit for the same. **05**

module SYNTH_CODE3(A,B,Y);
input[1:0] A,B;
output[3:0] Y;
assign Y = (A-B)^2;
endmodule

c) For the Verilog code SYNTH_CODE3 shown below, draw the equivalent logic circuit. **05**

module SYNTH_CODE3(A,B,Y);
input[1:0] A,B;
output[3:0] Y;
<u>always@(A)</u>
begin
if(B==2'b11)
Y = A ^ 2;
else
Y = A*2;
end
endmodule

UNIT - V

6	a) Briefly explain the building blocks of an FPGA with the help of a neat diagram.	10
	b) Implement a half adder using 4-input Look-up Tables inside an FPGA.	04
	c) Design a synthesizable Verilog module to generate the sequence 2-3-1-0-4-2.	06

OR

7	a) Design a Verilog Mealy type FSM that detects 010 and 001 (with overlaps) and sets output Z=1.	12
	b) With the help of a neat flowchart, briefly describe the process of implementing a digital system on an FPGA.	08
