

U.S.N.								
--------	--	--	--	--	--	--	--	--

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

September / October 2023 Supplementary Examinations

Programme: B.E.

Branch: Electronics and Communication Engineering

Course Code: 16EC7DCPEL

Course: Power Electronics

Semester: VII

Duration: 3 hrs.

Max Marks: 100

Date: 14.09.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1	a)	Distinguish between (i) Latching current and Holding current, (ii) Device turn off time and Circuit turn off time, (iii) Inverter grade SCR and converter grade SCR.	06
	b)	A thyristor has a forward break over voltage of 175 V when a gate pulse of 3mA is applied. Find the conduction angle, if a sinusoidal voltage of 250 V peak is applied. Draw the waveforms to show delay angle α and conduction angle θ .	06
	c)	List and explain the various types of power electronics circuits?	08

UNIT - II

2	a)	Explain RC triggering circuit with suitable wave forms.	06
	b)	Explain how an SCR can be protected against di/dt and dv/dt .	07
	c)	Identify and analyse a suitable triggering circuit in which the trigger angle can be varied only up to 90° .	07

OR

3	a)	Design a UJT relaxation oscillator for the given specification $\eta=0.51$, $I_p = 10\mu A$, $I_v = 10mA$, $V_v = 3.5 V$, $V_s = 30 V$. The frequency of oscillations $f = 50$ Hz and width of triggering pulse is $t_g = 60\mu sec$. Assume $V_D = 0.5 V$ and $C = 0.5 \mu F$	06
	b)	How a small gate current will turn on the SCR? Analyse using two transistor model.	08
	c)	List and explain the different turn on methods of SCR.	06

UNIT - III

4	a)	List and explain the applications of Controlled rectifiers.	05
	b)	Analyze a suitable control rectifier circuit which exhibits four quadrant operations.	09

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

c) The half wave controlled rectifier has a purely resistive load of R and the delay angle is $\pi/2$, determine **06**

- Rectification efficiency
- Form Factor FF
- Ripple Factor RF

UNIT - IV

5 a) Explain with neat diagram and relevant expressions & waveforms of DC chopper its output is always greater than input and also show that its principle can be applied to transfer energy from one voltage source to another. **10**

b) Identify and analyze the working principle of a regulated DC – DC converter if its output is always less than input voltage. **10**

OR

6 a) Define Chopper? Explain with neat diagram and relevant expressions & waveforms step down chopper? **08**

b) Identify and analyze the working principle of a regulated DC – DC converter if its output is either less than or greater than input voltage and the output voltage polarity is opposite to the input voltage polarity. **12**

UNIT - V

7 a) Explain the principle of operation of single phase half bridge and full bridge inverter with neat diagrams, waveforms and expressions. **14**

b) Explain Variable DC link inverter with neat diagram and waveform. **06**
