

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

January / February 2025 Semester End Main Examinations

Programme: B.E.

Semester: III

Branch: Electronics & Telecommunication Engineering



Duration: 3 hrs.

Course Code: 23ET3PCALC

Max Marks: 100

Course: ANALOG AND LINEAR CIRCUITS

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

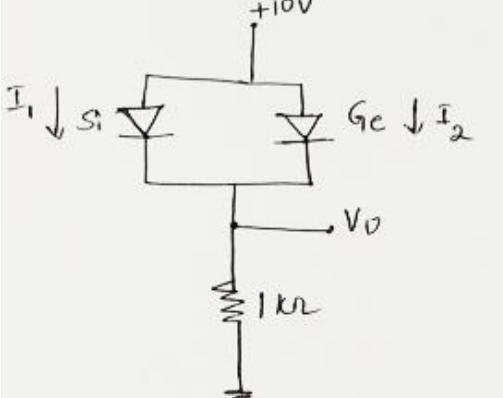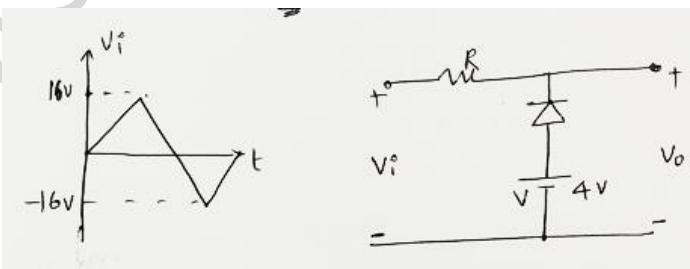UNIT - I			CO	PO	Marks
1	a)	Design a voltage divider bias network with a supply of 24V, a transistor with β of 110 and an operating point of $I_{CQ}=4\text{mA}$ and $V_{CEQ}=8\text{V}$. Choose $V_E=1/8V_{cc}$.	CO2	PO1	10
	b)	Determine V_0, I_1, I_2 for the network shown below in Fig.1b	CO2	PO1	04
		 <p>Fig.1b</p>			
Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.					
	c)	Analyze the circuit shown below in Fig.1c. Determine and sketch V_0 for the circuit shown (assume a silicon diode)	CO2	PO1	06
		 <p>Fig.1c</p>			
OR					
2	a)	Draw a negative (positive peak) clamper circuit and explain its working along with i/p and o/p waveform.	CO2	PO1	07
	b)	For the circuit shown in the Fig.2b below, determine the transfer characteristics and sketch the waveform for V_0 .	CO2	PO1	05

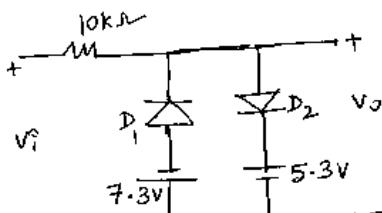
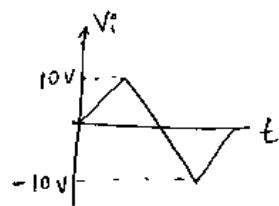


Fig.2b

c) Draw r_e model for a voltage divider bias configuration and derive expressions for input impedance, output impedance and voltage gain.

UNIT - II

3 a) With a neat circuit diagram, Explain the working of transformer coupled class A power amplifier.

b) A class B transformer coupled amplifier is supplied with $V_{CC}=50V$. The signal brings the collector voltage down to $V_{min}=5V$. The total dissipation from both transistors is 40W. Find the total power and conversion efficiency.

c) With a neat circuit diagram and transfer characteristics, derive the expression for power conversion efficiency of class B complementary push pull amplifier.

OR

4 a) Derive the expression for maximum efficiency of a series fed class A amplifier.

b) Identify the amplifier shown in Fig.4b and enumerate its properties.

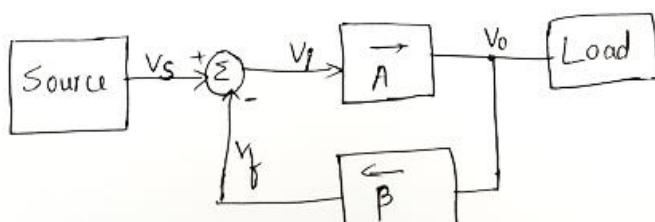



Fig.4b

c) For a harmonic distortion reading of $D_2=0.1$, $D_3=0.02$ and $D_4=0.01$ with $I_1=4A$ and $R_C=8\Omega$, calculate the total harmonic distortion, fundamental power component and total power.

UNIT - III

5 a) Derive an expression for drain current of NMOS transistor that operates in (i) triode region and (ii) saturation region.

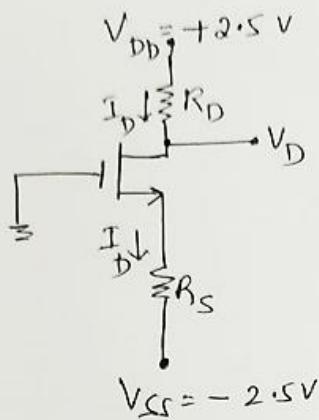b) Design the below given circuit so that the transistor operates at $I_0=0.4mA$ and $V_D=10.5V$. The NMOS transistor has $V_t=0.7V$, $\mu_0C_{0x}=100\mu A/V$, $L=1\mu m$ and $W=32\mu m$. Neglect the channel length modulation effect (assume that $\lambda=0$)



OR

6 a) Derive an expression for transconductance and voltage gain of a common source NMOS amplifier.

CO2 PO1 **12**

b) Consider a common source amplifier circuit with resistor R_S and current source biasing where $g_m=0.5\text{mA/V}$, $V_{DD}=15\text{V}$, $V_{SS}=-15\text{V}$, $R_G=5\text{M}\Omega$, $R_D=10\text{K}\Omega$, $R_t=12\text{K}\Omega$, $R_S=2\text{K}\Omega$ and $R_{sig}=100\Omega$. Find R_{in} , R_{out} , A_v , A_{v0} and G_v . Write its circuit diagram.

CO2 PO1 **08**

UNIT - IV

7 a) For the operational amplifier circuit shown in the Fig.7a, the output saturation voltages are $\pm 15\text{V}$. Find the upper and lower triggering voltages.

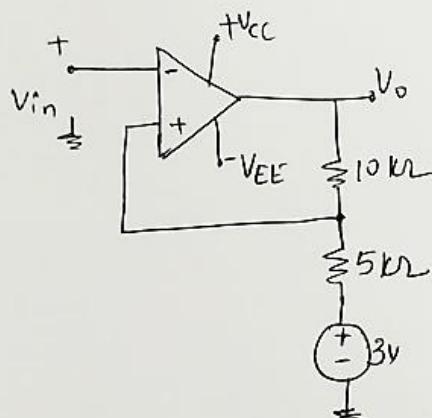


Fig. 7a

b) In the following Fig.7b assume an input of $V_{in}=20\sin\omega t$. Analyse the circuit and draw the i/p and o/p waveform and transfer characteristics. assume $V_{sat}=\pm 14\text{V}$.

CO3 PO2 **07**

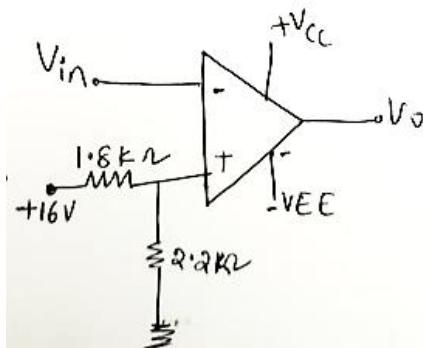
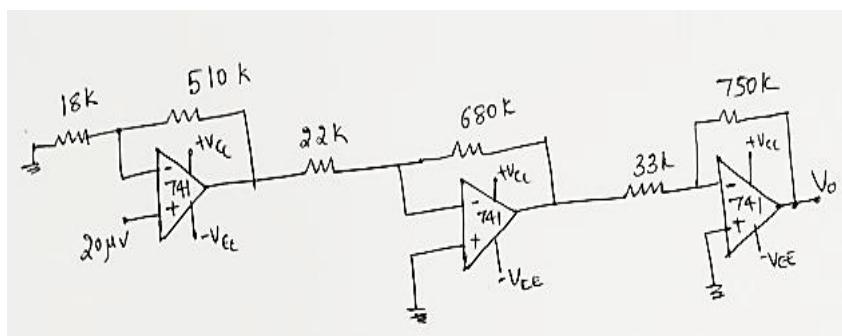
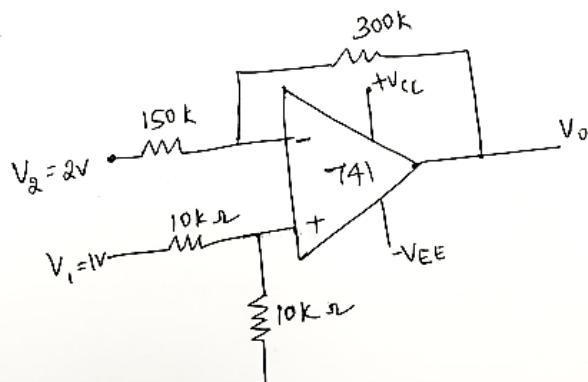


Fig.7b

		c)	Design a non-saturating op-amp positive half wave rectifier circuit. Draw its transfer characteristics. explain its working with the necessary waveforms.	CO2	PO1	05
			OR			
8	a)	With a neat circuit diagram, explain the working of instrumentation amplifier by deriving an expression for its output. What are the characteristics of instrumentation amplifier?	CO1			08
	b)	Calculate the output voltage for the Fig.8b. Find out the overall gain.	CO2	PO1		07
						
		Fig.8b.				
	c)	Determine the output voltage for the given circuit shown in Fig.8c	CO2	PO1		05
						
		Fig.8c				
		UNIT - V				
9	a)	Explain the working of R-2R DAC circuit and mention its advantages.	CO1			10
	b)	Explain the functional block diagram of IC 555 timer.	CO1			10
		OR				
10	a)	Explain the working principle of 3 bit flash type ADC with its advantages and disadvantages.	CO1			10
	b)	Explain the working principle of astable multivibrator using 555 IC and mention its application.	CO1			10