

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## April 2024 Semester End Main Examinations

**Programme: B.E.**

**Semester: III**

**Branch: Electronics and Telecommunication Engineering**


**Duration: 3 hrs.**

**Course Code: 23ET3PCALC**


**Max Marks: 100**

**Course: Analog and Linear Circuits**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.
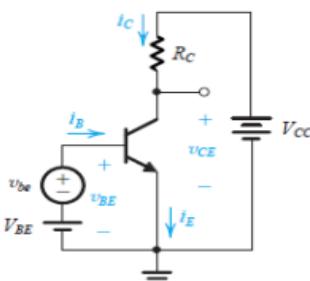
<b>UNIT - I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>
1	a)	Explain the design constraint of classical discrete-circuit biasing arrangement with circuit and relevant equations and also explain how does $R_E$ provide a negative feedback action to stabilize the bias current.	<i>CO1,2</i>	<i>PO1, 2,3</i>	<b>08</b>
	b)	Calculate the voltage gain of the circuit shown in Fig. 1b for $v_{be} = 0.005 \cos \omega t$ V, also find $v_{ce}$ and $i_b$ , if $V_{BE}$ is adjusted to yield a dc collector current of 1 mA, $V_{CC} = 15$ V, $R_C = 5$ k $\Omega$ , and $\beta = 100$ .	<i>CO1,2</i>	<i>PO1,2,3</i>	<b>08</b>
	c)	 <b>Fig. 1b</b>	<i>CO1,2</i>	<i>PO1,2,3</i>	<b>04</b>
<b>UNIT - II</b>					
2	a)	Prove the following properties of Negative feedback: (a) Gain Desensitivity (b) Bandwidth Extension	<i>CO1,2</i>	<i>PO1,2,3</i>	<b>10</b>
	b)	Derive the expression of Gain, Input-Resistance, and Output-resistance for voltage amplifier with the help of a neat circuit diagram and explanation.	<i>CO1,2</i>	<i>PO1,2,3</i>	<b>10</b>
<b>OR</b>					
3	a)	Derive the expression of power-conversion efficiency of Class A amplifier with the help of a neat circuit diagram and explanation.	<i>CO1,2</i>	<i>PO1,2,3</i>	<b>10</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

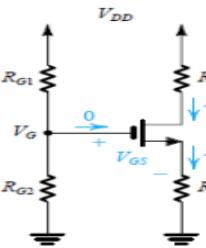	b)	Derive the expression of power-conversion efficiency of Class B amplifier with the help of a neat circuit diagram and explanation.	CO1,2	PO1,2,3	<b>10</b>
		<b>UNIT - III</b>			
4	a)	Explain the effects of Biasing by Fixing $V_{GS}$ in a MOSFET with $i_D-V_{GS}$ characteristic.	CO1,2	PO1,2,3	<b>08</b>
	b)	Design the circuit of Fig. 3b to establish a dc drain current $I_D = 0.5$ mA. The MOSFET is specified to have $V_t = 1$ V and $(kn' W/L) = 1$ mA/V <sup>2</sup> . For simplicity, neglect the channel-length modulation effect (i.e., assume $\lambda = 0$ ). Use a power-supply $V_{DD} = 15$ V. $I_g = 1\mu A$ .	CO1,2	PO1,2,3	<b>08</b>
		 <p>Fig.3b</p>			
	c)	Explain with a neat circuit diagram the Biasing of MOSFET using a Drain-to-Gate Feedback Resistor.	CO1,2	PO1,2,3	<b>04</b>
		<b>UNIT - IV</b>			
5	a)	Explain positive and negative half wave precision rectifier with the help of neat circuit diagrams and relevant waveforms.	CO3,4	PO1,2,3	<b>10</b>
	b)	Explain with a neat circuit diagram Instrumentation Amplifier Using Transducer Bridge.	CO3,4	PO1,2,3	<b>10</b>
		<b>UNIT - V</b>			
6	a)	Explain the DAC using R-2R ladder with the help of a neat circuit diagram.	CO3,4	PO1,2,3	<b>10</b>
	b)	Explain the internal block diagram of 555 timer with a neat diagram.	CO3,4	PO1,2,3	<b>10</b>
		<b>OR</b>			
7	a)	Explain the ADC using the Successive-approximation method with the help of a neat circuit diagram.	CO3,4	PO1,2,3	<b>10</b>
	b)	Explain with a neat circuit diagram the working of a Monostable Multivibrator.	CO3,4	PO1,2,3	<b>10</b>

\*\*\*\*\*