

U.S.N.								
--------	--	--	--	--	--	--	--	--

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## October 2023 Semester End Main Examinations

**Programme: B.E.**

**Semester: IV**

**Branch: Electronics and Telecommunication Engineering**

**Duration: 3 hrs.**

**Course Code: 19ET4PCVLD**

**Max Marks: 100**

**Course: VLSI Design**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

1 a) Along with proper diagrams, explain the fabrication of n - MOS transistor **08**  
 b) Write the stick diagram and mask layout for 2-input CMOS NOR gate **06**  
 c) Discuss Lambda based design rules **06**

### OR

2 a) Discuss the CMOS inverter in detail, along with the respective diagrams and tabulations **08**  
 b) Along with proper diagrams, explain the working of an n-channel Enhancement MOSFET and discuss modes as well as the regions **06**  
 c) Analyze with relevant diagrams the CMOS Twin Tub process **06**

### UNIT - II

3 a) Implement and analyze a 3 I/P Dynamic CMOS NOR logic. Also implement its stick diagram. **08**  
 b) Explain and implement a Bi-CMOS NAND logic structure. **06**  
 c) Analyze the Transmission gate and Tristate Inverter. **06**

### UNIT - III

4 a) Derive the inverter delays for the following using appropriate terminologies:  
 i) CMOS inverter **08**  
 ii) nMOS inverter  
 b) Derive expressions for Rise and Fall time delays. **06**  
 c) Define sheet resistance and area capacitance with appropriate terminologies. **06**

### UNIT - IV

5 a) Implement and analyze the operation of a Carry Skip Adder. **10**  
 b) Implement and analyze the operation of Braun Array multiplier. **10**

### OR

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 Revealing of identification, appeal to evaluator will be treated as malpractice.

6 a) Implement and analyze the operation of a Manchester Carry chain adder. **10**  
b) Implement and analyze the operation of a Wallace tree multiplier. **10**

**UNIT - V**

7 a) Explain the operation of 3T dynamic RAM cell and 1T dynamic memory cell. **10**  
b) Discuss any five practical testability methodologies. **10**

\*\*\*\*\*

B.M.S.C.E. - EVEN SEM 2022-23