

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## December 2023 Supplementary Examinations

**Programme: B.E.**

**Branch: MD/EIE**

**Course Code: 22ES3PCAME**

**Course: Analog Micro Electronics**

**Semester: III**

**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

1 a) Determine  $V_o$  for the network shown in figure 1. A,

**06**

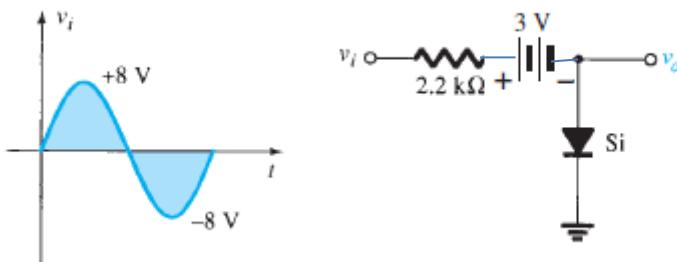


Fig1.a

b) Estimate  $I_C$ ,  $V_E$ ,  $V_B$ ,  $R_1$  for the network shown in figure 1.b,

**06**

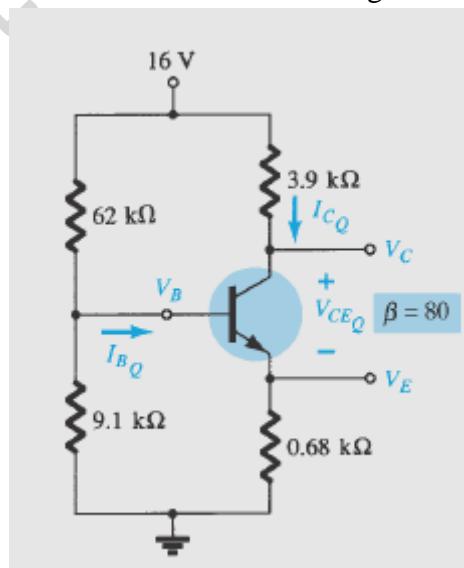


Fig1.b

c) Obtain the AC equivalent model of a CE voltage divider bias network and derive  $Z_i$ ,  $Z_o$ ,  $A_v$ ,  $A_i$  using re model

## OR

2 a) Sketch  $v_o$  for the positive clamping circuit and explain the operation with negative reference voltage 06

b) Determine  $r_e$ ,  $Z_i$ ,  $Z_o$  and  $A_v$  for the network shown in figure 2.b 08

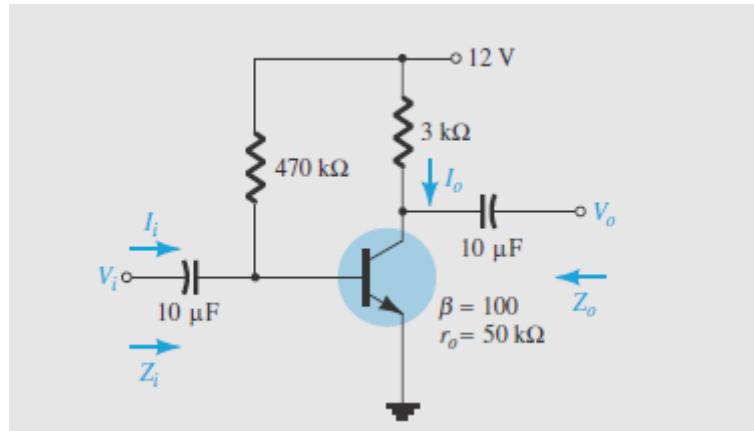


Fig 2.b

c) Derive an equation for  $I_B$  and  $V_{CE}$  of voltage divider biasing, using approximate analysis. 06

## UNIT - II

3 a) Demonstrate the low frequency response of a RC coupled amplifier 08

b) Illustrate the significant of negative feedback on bandwidth of an amplifier. 04

c) Derive an expression for gain, input impedance and output impedance of a voltage shunt feedback amplifier 08

## UNIT - III

4 a) Explain the operation of a series fed class A power amplifier and obtain the efficiency. 08

b) calculate the input power, output power, and power handled by each output transistor of a class B power amplifier and the circuit efficiency for an input of 12 V rms with  $V_{cc} = 25 \text{ V}$ , and a load  $4 \Omega$  06

c) What is harmonic distortion? Explain the causes of distortion. 06

## UNIT - IV

5 a) With a neat diagram and  $i_d-v_{ds}$  characteristics explain the operational of n – channel enhancement MOSFET. When 08

(a)  $V_{GS} \leq V_t$   
 (b)  $V_{GS} > V_t$  &  $V_{DS} < V_{GS} - V_t$   
 (c)  $V_{GS} > V_t$  &  $V_{DS} \geq V_{GS} - V_t$ .

b) Analyze the circuit shown in figure 5.b having  $V_t=1\text{V}$ ,  $K_n'(W/L)=1\text{mA/V}^2$ ,  $\lambda=0$ . determine  $I_D$ ,  $V_s$ ,  $V_{GS}$ ,  $V_D$ . **06**

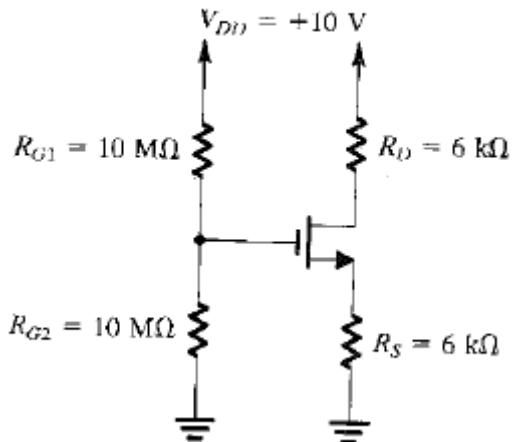


Fig 5.b

c) Using the transfer characteristics of a MOSFET , obtain the analytical expression of drain-to-source resistance in the triode region **06**

#### UNIT - V

6 a) Sketch the T-equivalent model of an n channel enhancement MOSFET. **08**  
 b) Construct the small signal model of a Common Source amplifier and derive an expression for gain, input and output impedance. **08**  
 c) Compare Common Gate and Common Source amplifier **04**

#### OR

7 a) Derive an expression for transconductance of MOSFET. **06**  
 b) With relevant circuits and expressions, explain the MOSFET steering circuits. **06**  
 c) Develop the overall gain, input and output impedance of a source follower using small, signal model of MOSFET **08**

\*\*\*\*\*