

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## April 2024 Semester End Main Examinations

Programme: B.E.

Branch: Cluster (EIE/MD)

Course Code: 22ES3PCAME



Course: Analog Microelectronics

Semester: III


Duration: 3 hrs.

Max Marks: 100

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

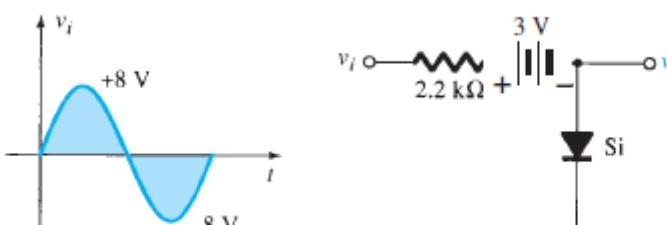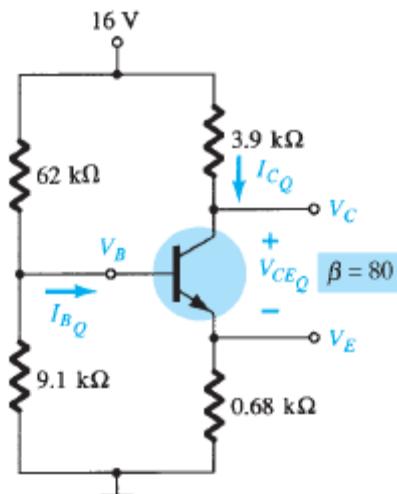UNIT - I			CO	PO	Marks
1	a)	<p>Determine <math>V_o</math> for the network shown in figure 1a</p>  <p>figure 1a</p>	CO1		06
	b)	<p>Estimate <math>I_C</math>, <math>V_E</math>, <math>V_B</math>, <math>R_1</math> for the network shown in figure 1b</p>  <p>figure 1b</p>	CO2	PO1	06
	c)	<p>Obtain the AC equivalent model of a CE voltage divider bias network and derive <math>Z_i</math>, <math>Z_o</math>, <math>A_v</math>, <math>A_I</math> using re model</p>	CO2	PO1	08

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.
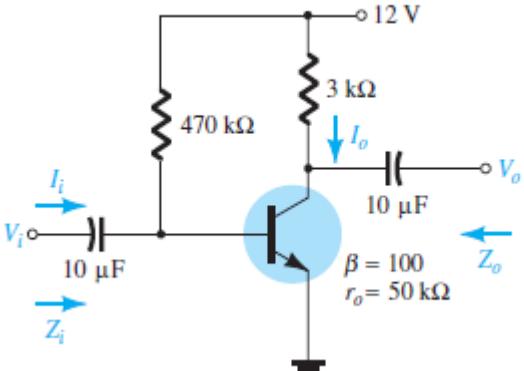
<b>OR</b>					
2	a)	Sketch $v_o$ for the positive clamping circuit and explain the operation with negative reference voltage	CO2	PO1	<b>06</b>
	b)	Determine $r_e$ , $Z_i$ , $Z_o$ and $A_v$ for the network shown in figure	CO2	PO1	<b>06</b>
					
	c)	Derive expression for $I_c$ & $V_{ce}$ for voltage divider bias using exact method of analysis.	CO2	PO1	<b>08</b>
<b>UNIT - II</b>					
3	a)	Demonstrate the low frequency response of a RC coupled amplifier	CO2	PO1	<b>08</b>
	b)	Illustrate the significant of negative feedback on bandwidth	CO2	PO1	<b>04</b>
	c)	Derive an expression for gain and input impedance and output impedance of a voltage shunt feedback amplifier	CO2	PO1	<b>08</b>
<b>UNIT - III</b>					
4	a)	Explain the operation of a series fed class A power amplifier and obtain the efficiency.	CO2	PO1	<b>08</b>
	b)	calculate the input power, output power, and power handled by each output transistor of a class B power amplifier and the circuit efficiency for an input of 12 V rms with $V_{cc}=25$ v, and a load $4\Omega$	CO2	PO1	<b>06</b>
	c)	What is harmonic distortion? Explain the causes of distortion.	CO2	PO1	<b>06</b>
<b>UNIT - IV</b>					
5	a)	Illustrate the operation of a MOSFET as $V_{DS}$ is Increased	CO2	PO1	<b>08</b>
	b)	Analyze the circuit shown in figure 5.b having $V_t=1$ v, $K_n'(W/L)=1$ mA/V <sup>2</sup> , $\lambda = 0$ . determine $I_D$ , $V_s$ , $V_{GS}$ , $V_D$ .	CO2	PO1	<b>06</b>

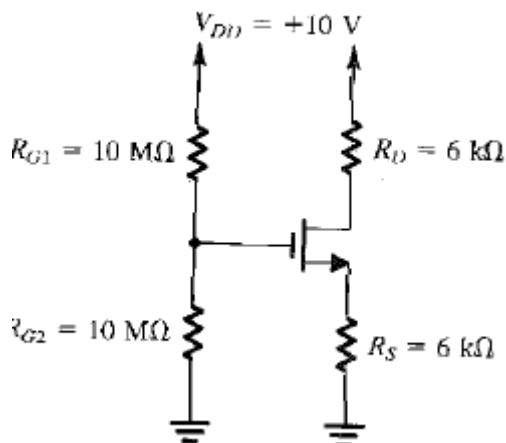


Figure 5b

<b>UNIT - V</b>					
6	a)	Obtain the signal current of MOSFET in the drain terminal	CO2	PO1	<b>08</b>
	b)	Construct the small signal model of a CS amplifier and derive an expression for gain	CO2	PO1	<b>08</b>
	c)	Compare CG and CS amplifier	CO2	PO1	<b>04</b>
<b>OR</b>					
7	a)	Construct the high frequency model of a CS amplifier and derive the expression	CO2	PO1	<b>10</b>
	b)	Develop the overall gain of a source follower using small, signal model	CO2	PO1	<b>10</b>

\*\*\*\*\*