

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

August 2023 Semester End Make-Up Examinations

Programme: B.E.

Branch: MD/EIE

Course Code: 22ES3PCAME

Course: Analog Micro Electronics

Semester: III

Duration: 3 hrs.

Max Marks: 100

Date: 10.08.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
 2. Missing data, if any, may be suitably assumed.

UNIT - I

1 a) Analyze and discuss the working of a negative clamper without reference voltage with necessary diagrams. 06

b) Design a double ended clipping circuit to get the following transfer characteristics as in Fig1(b). Assume silicon diodes and $V_i = 10 \sin \omega t$. Draw input and output waveforms. Explain its working. 06


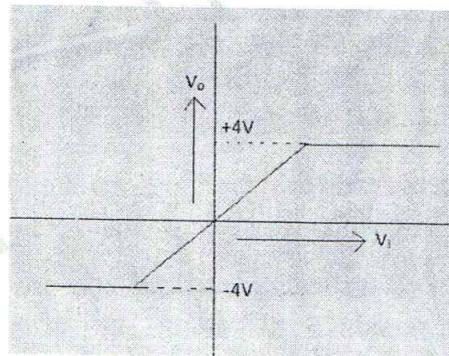


Fig 1(b)

c) For the voltage divider configuration shown below, Use approximate analysis and calculate 08

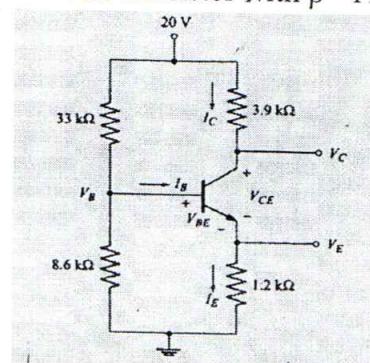a) V_B
 b) I_C and I_B
 c) V_E and V_{CE} . Assume silicon transistor with $\beta = 110$



OR

2 a) For the circuit shown in the Fig 2(a), determine I_D , V_1 , V_2 and V_o

06

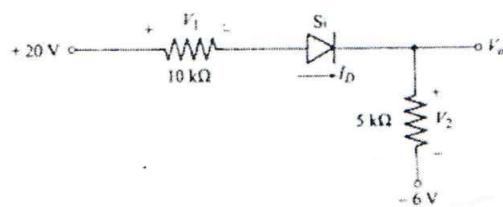


Fig 2(a)

b) Design a suitable circuit for the block shown below which has input and output waveforms as indicated

06

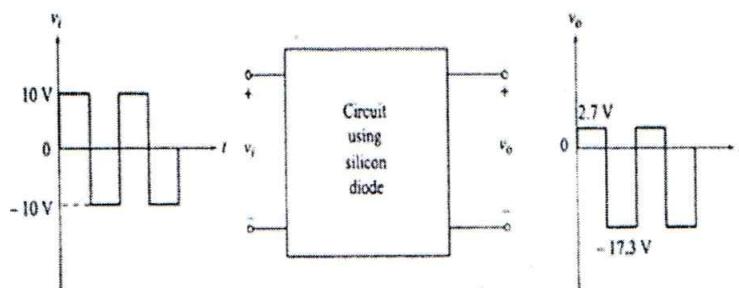


Fig 2(b)

c) Obtain the AC equivalent model of a CE voltage divider network and derive Z_i , Z_o , Av , AI

08

UNIT - II

3 a) Derive expressions for gain, input resistance and output resistance of voltage shunt feedback with block representation approach. 10

b) Discuss the significance of Miller capacitance at high frequencies with suitable expressions. 10

UNIT - III

4 a) What is the drawback of the Class B Power Amplifier? Explain the measures to overcome the same with suitable diagrams. 05

b) Suggest a suitable method to increase the efficiency of series fed Class A Power Amplifier using transformer and deduce an expression to prove the efficiency is higher than Series fed Class A type. 06

c) Determine the voltage gain, input and output impedance with feedback for voltage series feedback having $A=-90$, $R_i=15\text{ k}\Omega$, $R_o=20\text{ k}\Omega$ for feedback of:
 i) $\beta=-0.2$
 ii) $\beta=-0.75$
 Comment on the results 09

UNIT - IV

5 a) Analyze and Comment on the drain currents for a n-channel MOSFET with $t_{ox} = 20$ nm, $\mu_n = 650$ cm 2 /V.s, $V_t = 0.8$ V, and $W/L = 10$. 04

(a) $V_{GS} = 5$ V and $V_{DS} = 1$ V.
 (b) $V_{GS} = 2$ V and $V_{DS} = 1.2$ V.

b) Derive an expression for drain current of NMOS transistor that operates in 09
 i) Triode region ii) Saturation region.

c) Design the circuit shown in the Fig 5(c) so that the transistor operates at $I_D = 0.4$ mA and $V_D = +0.5$ V. The NMOS transistor has $V_t = 0.7$ V, $\mu_n C_{ox} = 100$ μ A/V 2 , $L = 1$ μ m, and $W = 32$ μ m. Neglect the channel length modulation effect. 07

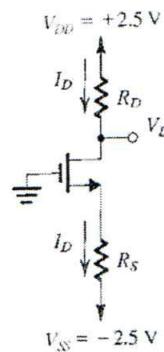


Fig 5(c)

UNIT - V

6 a) Deduce an expression for small signal voltage gain of enhancement MOSFET 10
 amplifier.

b) Develop a T equivalent model of a MOSFET with necessary equations and 10
 diagrams.

OR

7 a) Deduce an expression for overall voltage gain of a source follower amplifier 10
 with the help of equivalent circuits.

b) Analyze and discuss the working of a MOS Current steering circuit with 10
 suitable circuit and equations.
