

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## September / October 2023 Supplementary Examinations

**Programme: B.E.**

**Branch: ES Cluster (EEE/TCE/ECE/EIE/MD)**

**Course Code: 19ES3CCECA**

**Course: ELECTRICAL CIRCUIT ANALYSIS**

**Semester: III**

**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

1 a) By using Source Transformation, calculate single voltage equivalent for the network shown in the Fig.1.a. **10**

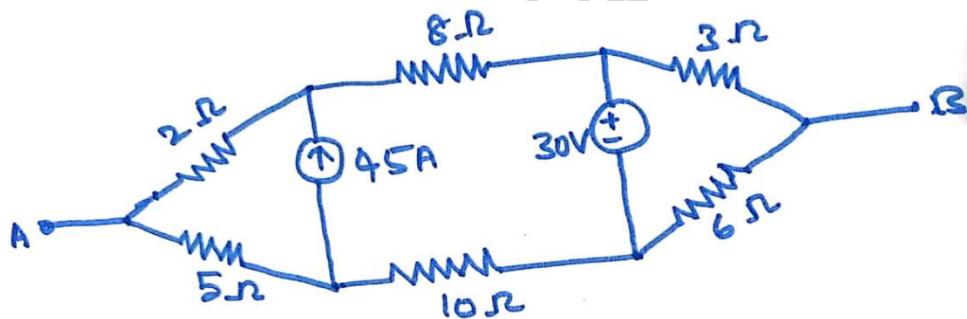


Fig. 1.a.

b) Explain the concept of Super-node analysis with an example. **06**  
c) Explain Independent and dependent sources. **04**

**OR**

2 a) Calculate mesh currents using mesh analysis for the circuit shown in the Fig.2. a. **10**

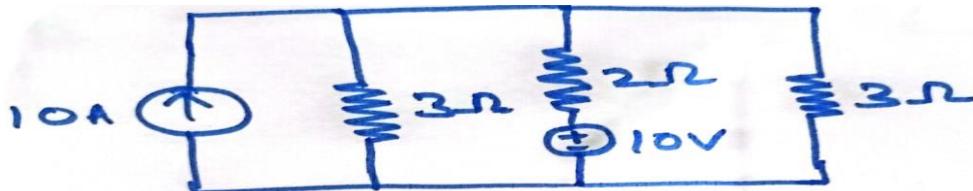


Fig.2.a.

b) Determine the node voltage by nodal analysis for the given network of Fig.2.b. **10**

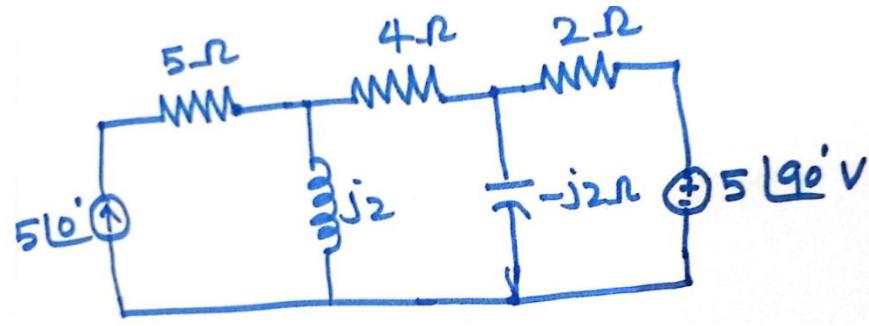


Fig.2.b.

### UNIT - II

3 a) A series RLC circuit consist of  $R=10 \Omega$ ,  $L=0.01 \text{ H}$ , and  $C=0.01 \mu\text{F}$  is connected across a supply of  $10\text{mV}$ . Determine (i) fo (ii) Q-factor (iii) BW (iv)  $f_1$  and  $f_2$  (v)  $I_0$  **10**

b) Explain with examples the principles of Duality by graphical method. **10**

### UNIT - III

4 a) Determine the Thevenin's equivalent circuit across the terminals A-B of the network shown in the Fig.4.a **10**

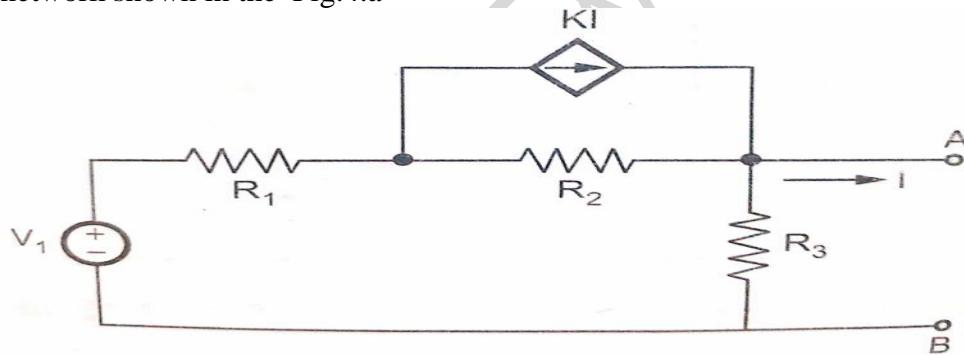


Fig.4.a

b) Determine the current through  $10\Omega$  resistance of the network shown in Fig.4.a using Superposition Theorem. **10**

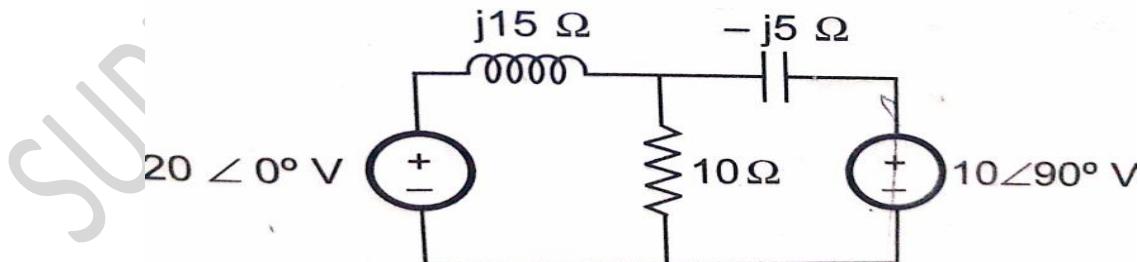


Fig.4.b.

### UNIT - IV

5 a) Calculate the expression for the current in a series RLC circuit fed by a D.C. voltage of  $20\text{V}$  with  $R=4\Omega$ ,  $L=1 \text{ H}$ , and  $C=1/4 \text{ F}$ . Assume initial conditions to be zero. **10**

b) Determine the Laplace transform of the periodic function shown in the Fig. 5.b. 10

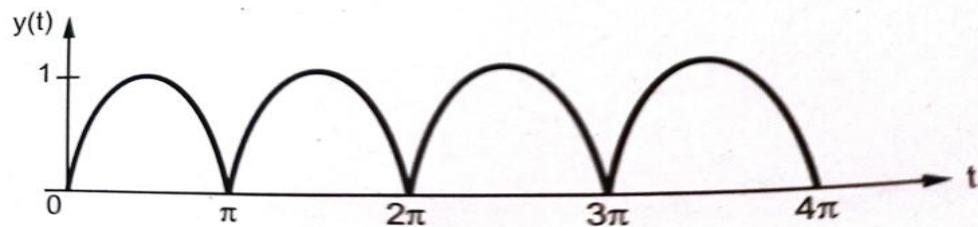


Fig. 5.b.

OR

6 a) State & prove Initial value theorem and Final value theorem. 10

b) The network shown in the Fig.6.b. is under steady state condition with switch K is at position 1. Determine expression for  $i(t)$  if switch K is moved to position 2. Draw variation of  $i(t)$ . 10

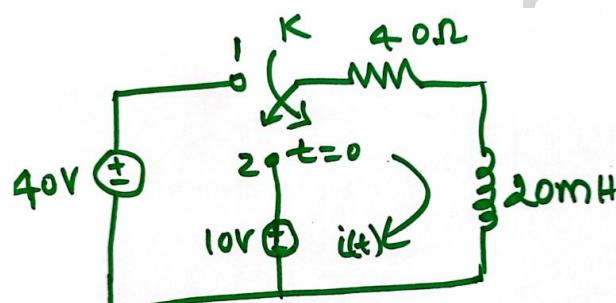


Fig.6.b

### UNIT - V

7 a) Obtain Z-Parameter of the circuit shown in the Fig. Fig.7.a 10

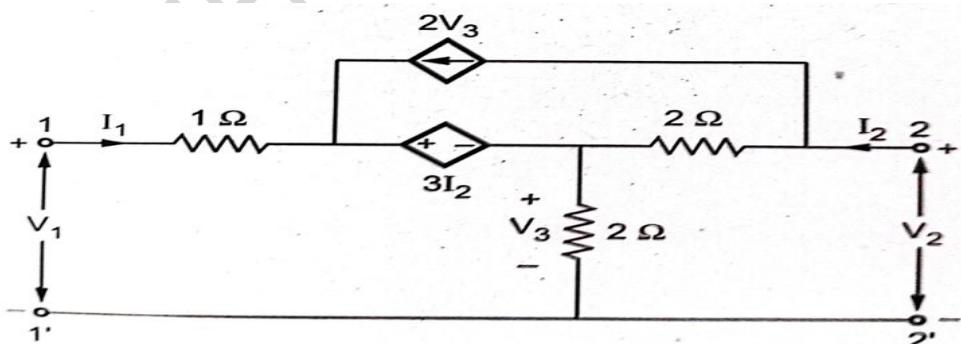


Fig.7.a

b) Determine 'Y' parameter of the network shown in Fig.7.b. 10

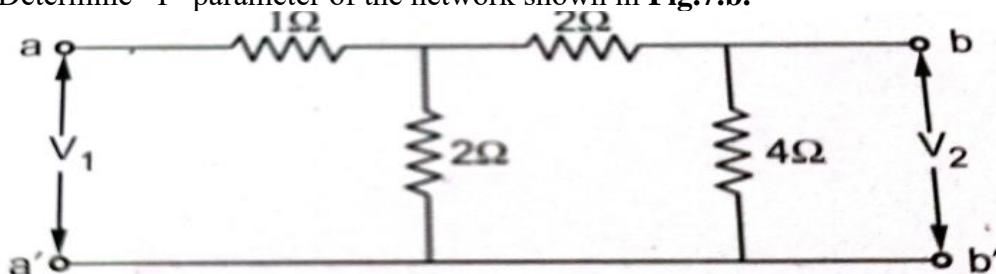


Fig.7.b.

\*\*\*\*\*