

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

May 2023 Semester End Main Examinations

Programme: B.E.

Branch: ES Cluster (EEE/TCE/ECE/EIE/MD)

Course Code: 19ES3CCECA

Course: ELECTRICAL CIRCUIT ANALYSIS

Semester: III

Duration: 3 hrs.

Max Marks: 100

Date: 17.05.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1 a) Apply mesh analysis and find I_1 , I_2 and I_3 for the circuit shown in Fig 1.1

10

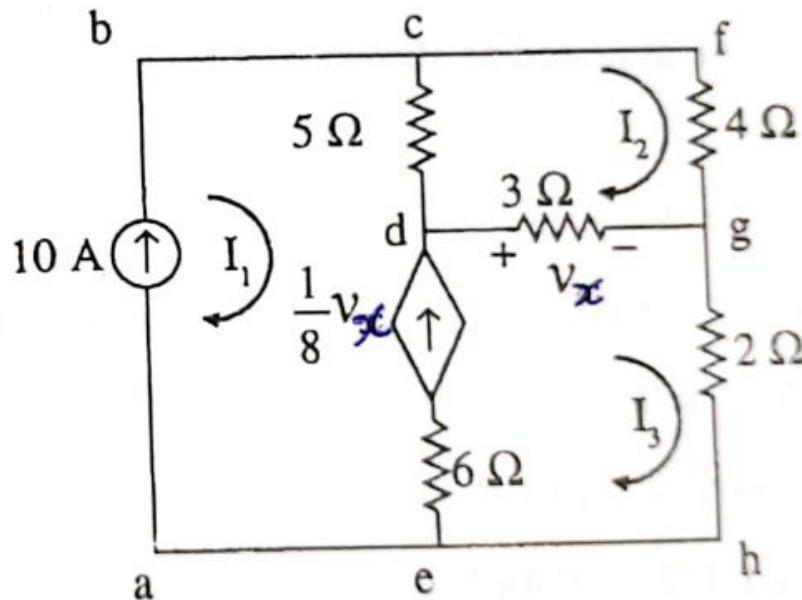


Fig 1.1

b) Use nodal analysis to find current flowing through 4Ω in the circuit shown in Fig 1.2

10

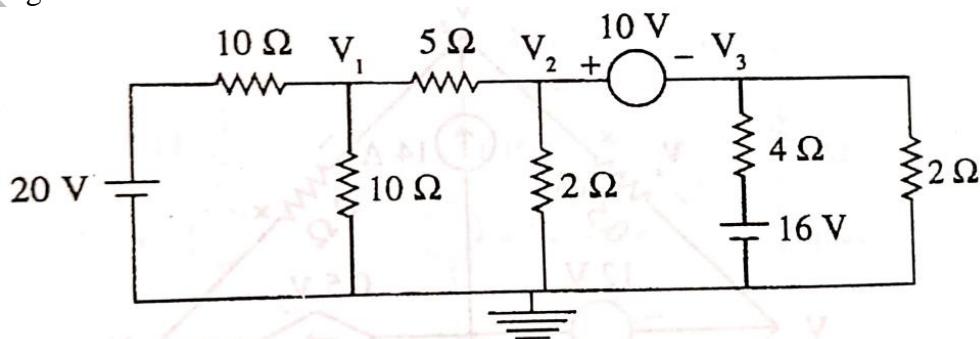


Fig 1.2

OR

2 a) Find all branch currents using nodal analysis for the circuit shown in Fig 2.1

10

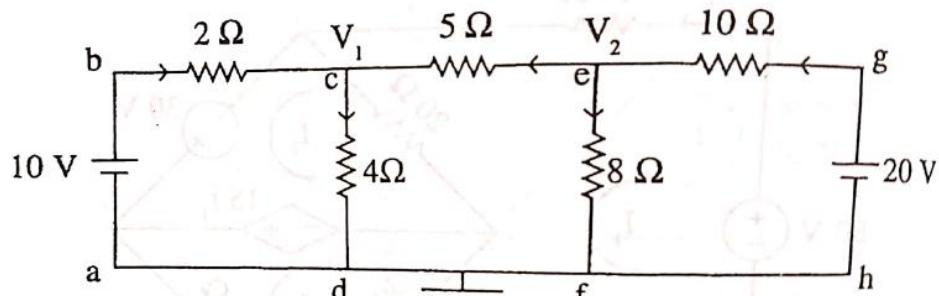


Fig 2.1

b) With relevant example explain source transformation and source shifting

10


UNIT - II

3 a) Derive the expression for the cutoff frequency, bandwidth and quality factor for a series resonant circuit

10

b) For the network shown in fig 3.1 draw the oriented graph. Select a tree and write the tie set and cutset matrices. Also write the incidence matrix.

10

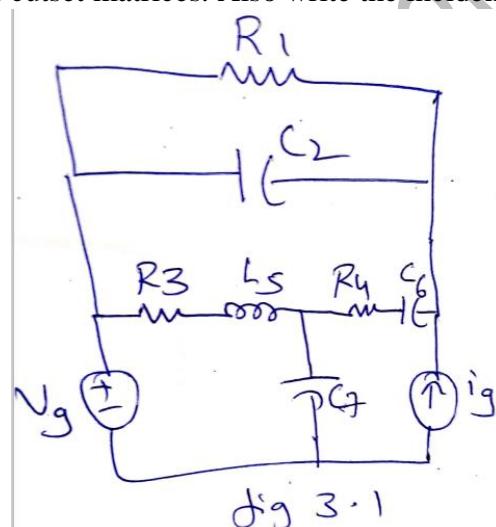

UNIT - III

4 a) State maximum power transfer theorem and derive an expression for maximum power

07

b) For the circuit shown in Fig 4.1 find the power dissipated in a 5 Ω resistor connected between A and B using Norton theorem

08

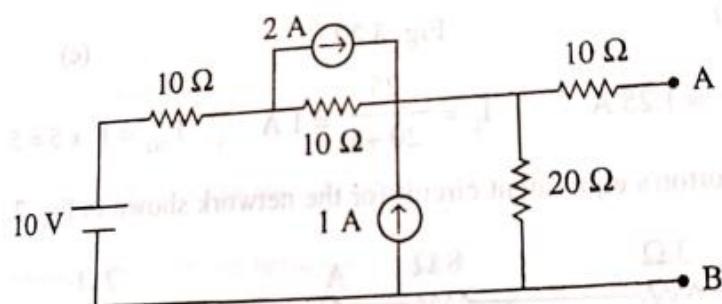


Fig 4.1

c) Using Millman's theorem find the current through the load resistance $R_L = 10 \Omega$ for the circuit shown in Fig 4.2 05


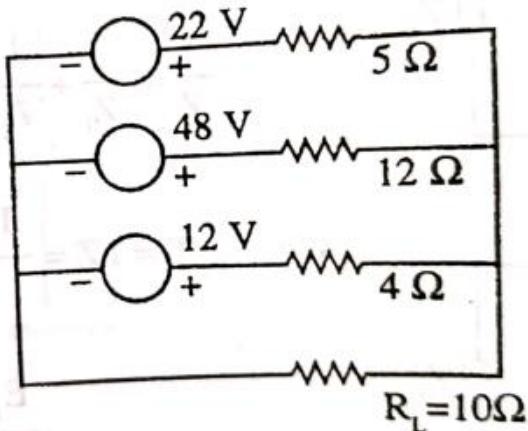



Fig 4.2

UNIT - IV

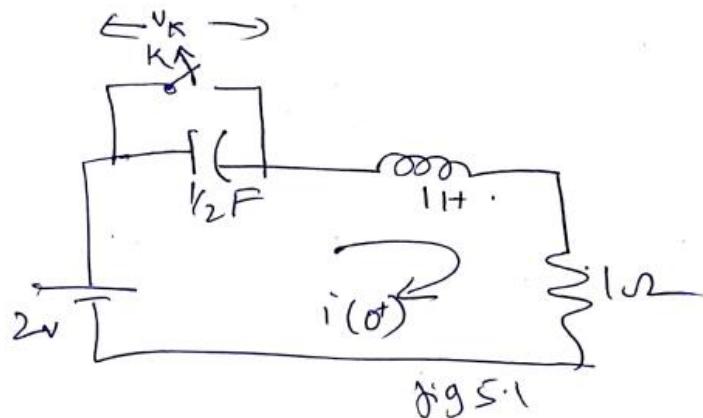5 a) State and prove final value theorem 06
 b) A steady state is reached when switch is closed. At $t=0$ switch is open. Find $i(0+)$, $di(0+)/dt$, $d^2i(0+)/dt^2$ for the circuit shown in fig 5.1 08



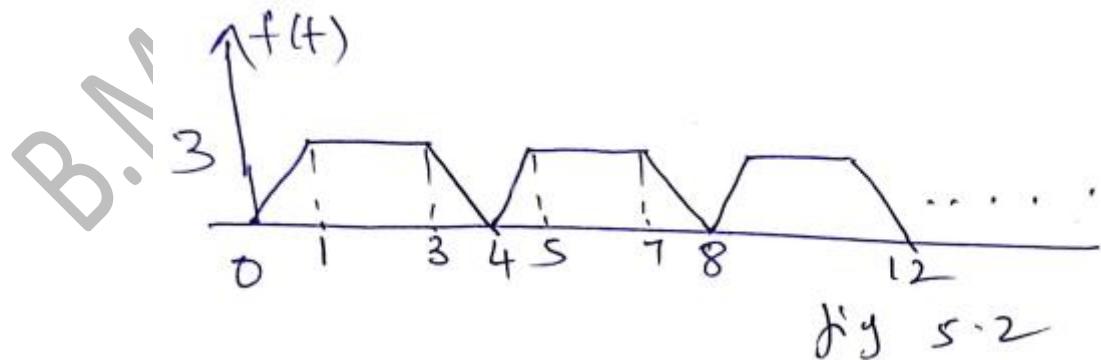c) Find the Laplace transform of the waveform shown in fig 5.2 06



OR

6 a) Find the Laplace transform of the waveform given in Fig 6.1

06

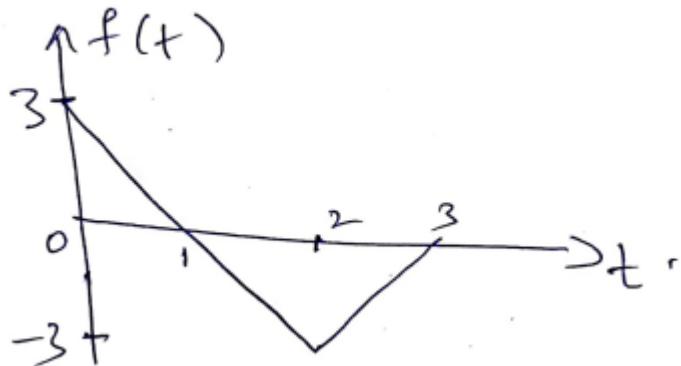


Fig 6.1

b) State and prove initial value theorem
 c) For the network shown in Fig 6.2 $R=1k\Omega$, $L=1H$, $C=0.1\mu F$ switch k is closed and steady state has been reached. At $t=0$, switch is opened. Find $i(0+)$, $di(0+)/dt$, $d^2i(0+)/dt^2$

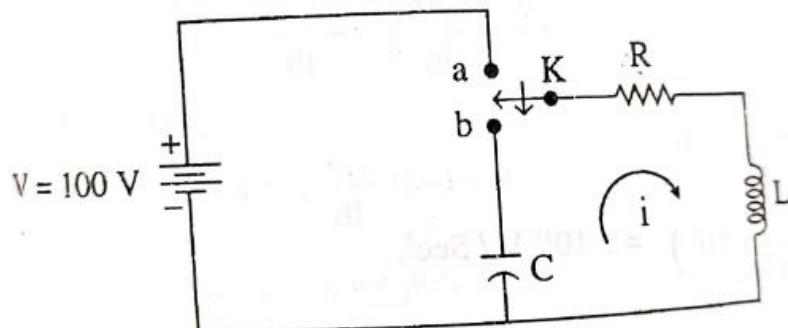


Fig 6.2

UNIT - V

7 a) Define Z parameters
 b) Express H-parameters in terms of T parameter by relevant conversions.
 c) Find Y parameters for the circuit shown in fig 7.1.

04

08

08

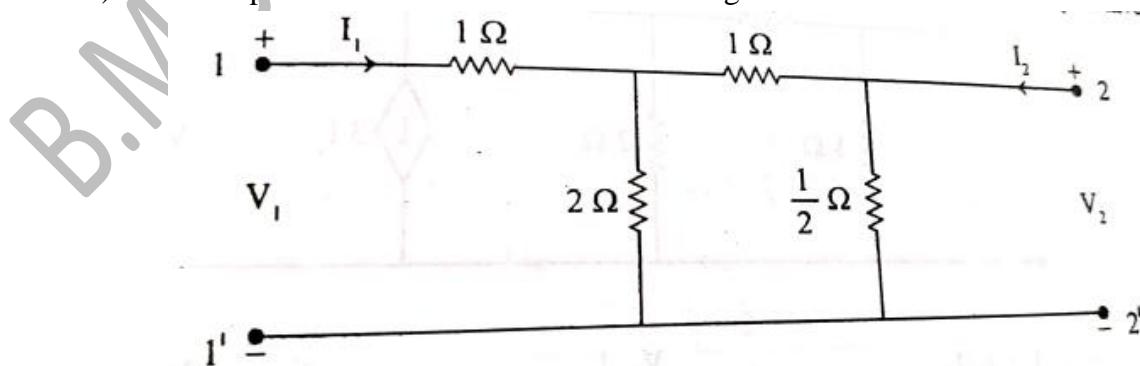


Fig 7.1
