

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## April 2024 Semester End Main Examinations

**Programme: B.E.**

**Branch: ES Cluster (EEE/ET/ECE/EIE/MD)**

**Course Code: 22ES3PCECA**



**Course: Electrical Circuit Analysis**

**Semester: III**


**Duration: 3 hrs.**


**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.
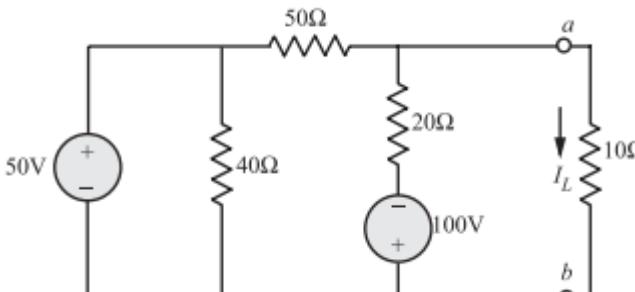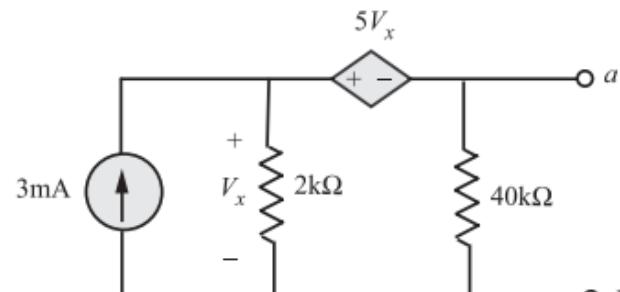
<b>UNIT - I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>
1	a)		CO1	PO1	<b>07</b>
		<p>Fig 1.1 For the circuit shown in Fig 1.1 find <math>I_L</math> using nodal analysis</p>			
	b)		CO1	PO1	<b>07</b>
		<p>Fig 1.2 Determine the voltage across a and b using mesh analysis for the circuit shown in Fig 1.2</p>			
	c)	Explain the concept of source shifting using an example	CO1	PO1	<b>06</b>
		<b>OR</b>			
2	a)	Derive the expression for star resistances in terms of delta resistances	CO1	PO1	<b>07</b>

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

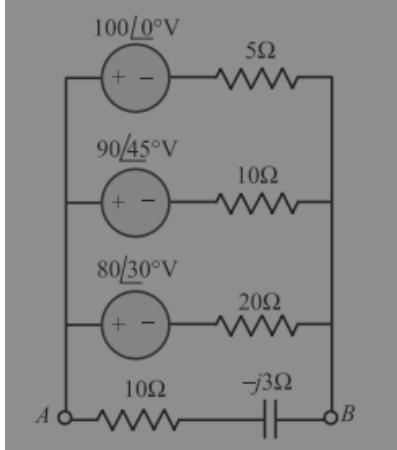	b)	 <p>Fig 2.2 Using source transformation find current through AB.</p>	CO1	PO1	07
	c)	Explain the concept of super mesh with an example	CO1	PO1	06
<b>UNIT - II</b>					
3	a)	Derive the expression for bandwidth for both series and parallel resonant circuit.	CO1	PO1	10
	b)	In a series circuit $R = 6\Omega$ , $\omega_0 = 4.1 \times 10^6$ rad/sec, band width = $10^5$ rad/sec. Compute L, C, half power frequencies and Q.	CO1	PO1	10
<b>UNIT - III</b>					
4	a)	<p>fig 3.1 For the circuit shown in fig 3.1 find the current flowing through <math>80\Omega</math> resistor using thevenin's theorem and verify the same using norton's theorem</p>	CO2	PO2	10
	b)	State and prove maximum power transfer theorem for AC circuits	CO2	PO2	10
<b>UNIT - IV</b>					
5	a)	In the given network, K is closed at $t=0$ , with zero current in the inductor. Find the values of $i$ , $di/dt$ , $d^2i/dt^2$ at $t=0+$	CO2	PO2	07

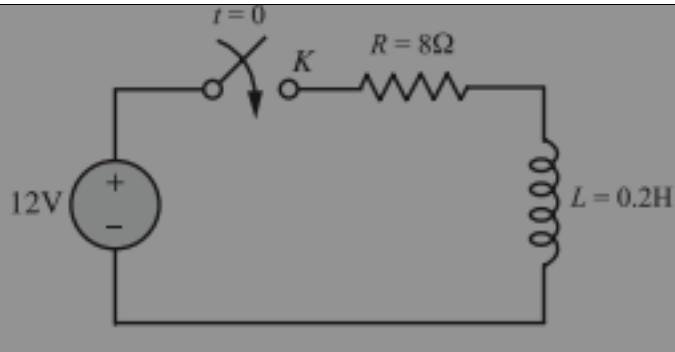

b) State and prove initial value theorem

**06**

c) Find the Laplace transform of a periodic square wave shown in fig 5.2

CO2

PO2

**07**


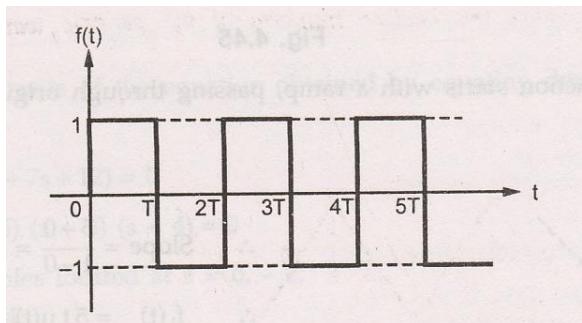


Fig 5.2

**OR**

6

a)

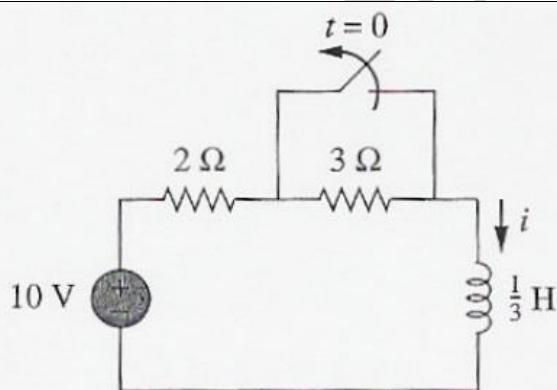

Assume the circuit shown in fig 6.1 has been closed for a long time. Find  $i$  at  $t=0^+$  and  $i$  at  $t=\infty$

CO2

PO2

**06**

b)

Discuss the initial and final conditions in passive network elements

-

-

**06**

c)

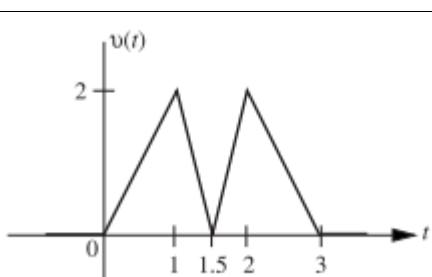


Fig 6.2

Find the laplace transform of  $v(t)$  as shown in Fig 6.2

CO2

PO2

**08**

**UNIT - V**


7 a) Define T parameter

- - **04**

b) Derive Z parameters in terms of H parameters.

CO1 PO1 **08**

c)

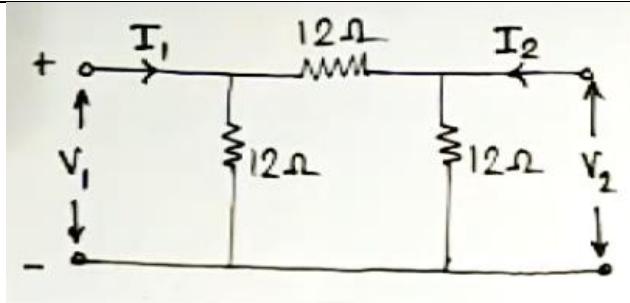CO2 PO2 **08**

Find h parameters for the circuit shown in fig 7.1

\*\*\*\*\*