

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## December 2023 Supplementary Examinations

**Programme: B.E.**

**Semester: III**

**Branch: ETE, EIE**

**Duration: 3 hrs.**

**Course Code: 22ES3PCECA**

**Max Marks: 100**


**Course: Electric Circuit Analysis**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I


1 a) Find the current flowing through  $5\Omega$  resistor using mesh analysis

**06**

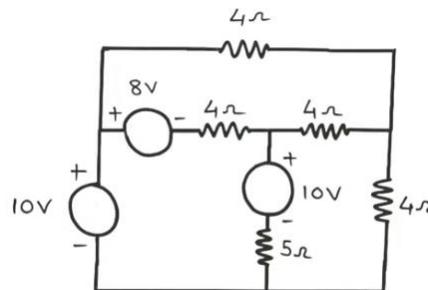


b) Determine the total resistance between terminal 'A-B' using Star- Delta conversion (All the resistors' values are  $9\Omega$ )

**07**

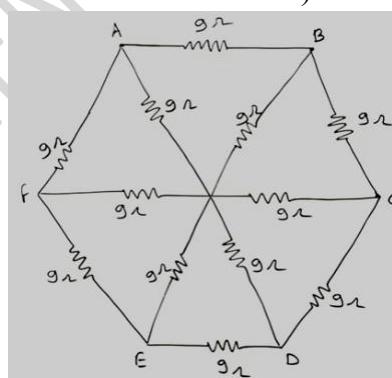

c) For the circuit, find the node voltages  $V_1$  &  $V_2$  using nodal analysis.


**07**

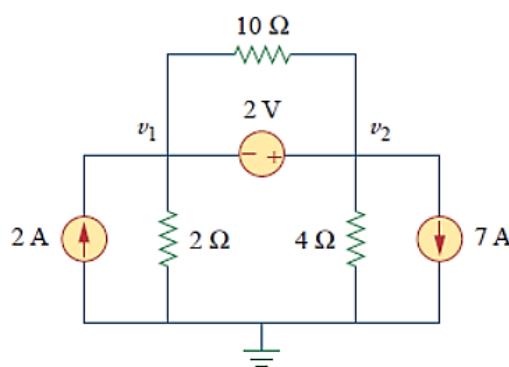


**OR**

2 a) Determine the 'v<sub>x</sub>' using source transformation method.

07

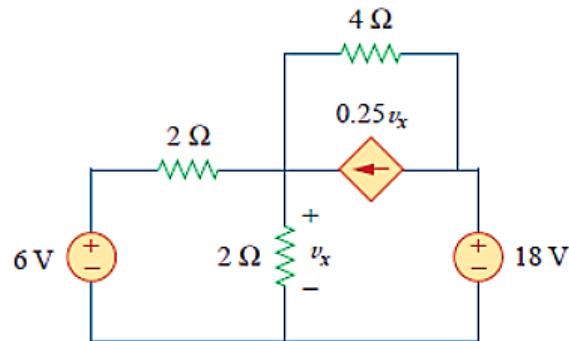


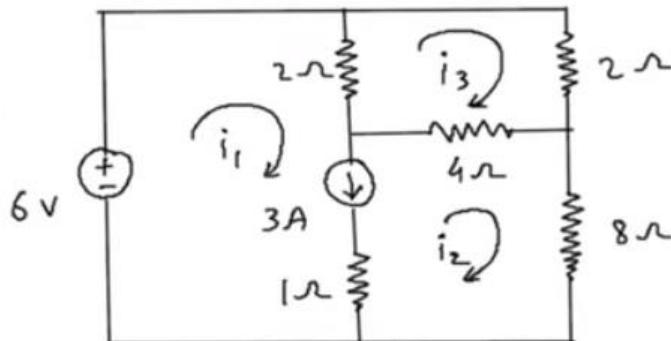b) Find all the loop currents using super mesh analysis



c) Find KCL for the circuit shown below

06

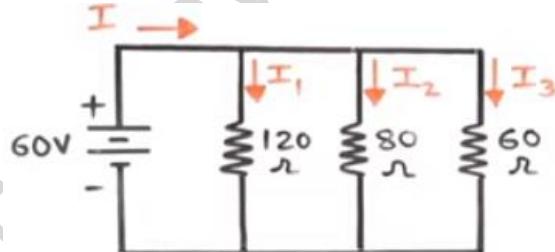


**UNIT - II**

3 a) Given below is Reduced Incidence matrix, draw the oriented graph from the incidence matrix

$$[A_r] = \begin{bmatrix} 1 & 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 & 0 \\ -1 & 0 & -1 & -1 & 0 \end{bmatrix}$$

b) For the network shown below, draw the graph, select a tree, write the tie set schedule and obtain the KVL equations.

08

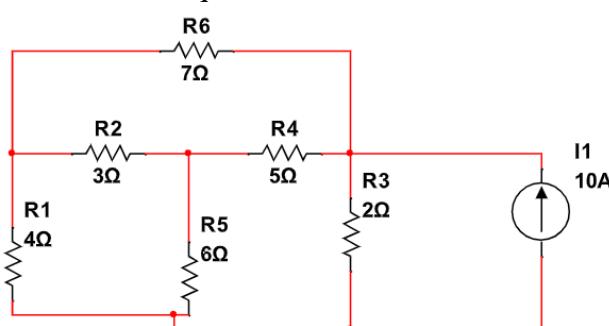


c) Three Impedance  $Z_1$ ,  $Z_2$  &  $Z_3$  are connected in series across, 250v, 50Hz supply. If  $Z_1=20 \Omega$ ,  $Z_2=8+j10 \Omega$ ,  $Z_3=15-j5 \Omega$ . Determine 08


1. Current through the circuit.
2. Power factor of the circuit.
3. Voltage across each impedance.
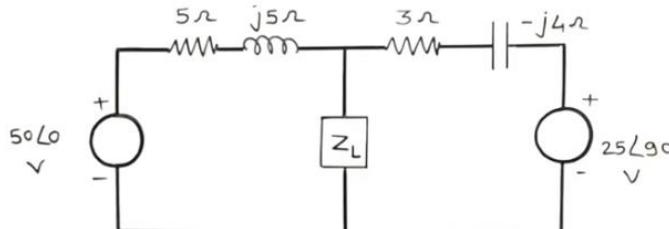
### UNIT - III


4 a) In the circuit shown below find the load impedance  $Z_L$  that will draw maximum power. Also find the value of that maximum power. 07



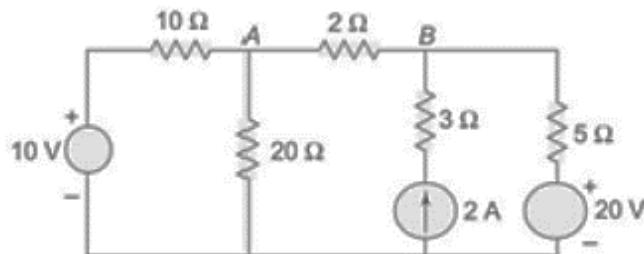b) Find the voltage across the 2ohm resistor in circuit shown below by using the superposition theorem. 06



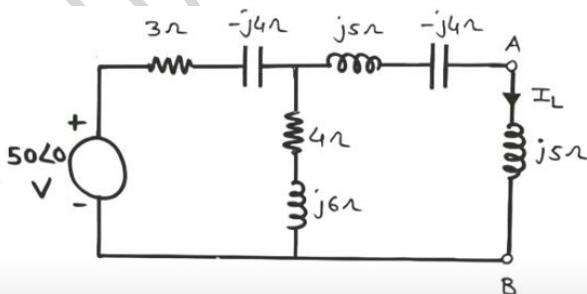
c) Obtain the Thevenin's equivalent circuit between the terminals A & B for the circuit shown below and also find the load current passing through 'j5Ω'. 07



### UNIT - IV

5 a) State and prove Initial and Final value theorem. 05

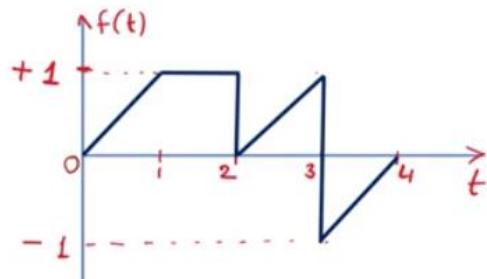
b) Find the Laplace Transform for the given waveforms. 08




c) Solve for  $f(0)$  and  $f(\infty)$ , If  $F(s)= 4e^{-2s} (s+50) / s$  07

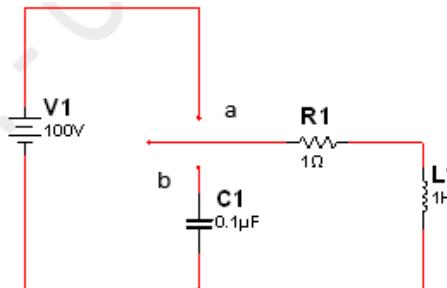**OR**

6 a) The switch S is moved from 'a' to 'b' at  $t = 0$ . Find the values of  $i$ ,  $di/dt$ ,  $d^2i/dt^2$  at  $t = 0^+$  if  $R = 1\Omega$ ,  $L = 1H$ ,  $C = 0.1\mu F$  and  $V = 100V$ . Assume steady state is achieved when S is at 'a'. 07



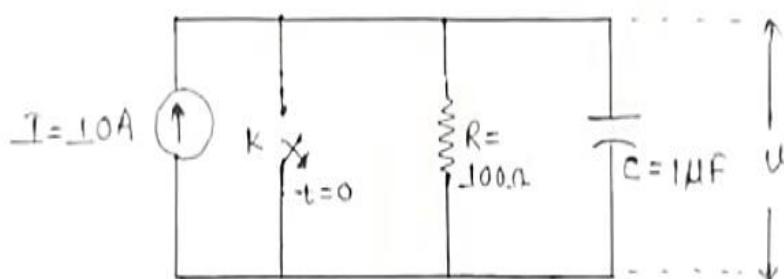b) In the given network the switch 'k' is closed at  $t=0$  with capacitor uncharged. Find  $v$ ,  $dv/dt$ ,  $d^2v/dt^2$  at  $t = 0^+$ . 07




c) Find the Laplace transform of the following functions 06


- $X(t) = 5u\left(\frac{t}{3}\right)$
- $X(t) = 2tu(t) - 4\frac{d\delta(t)}{dx}$

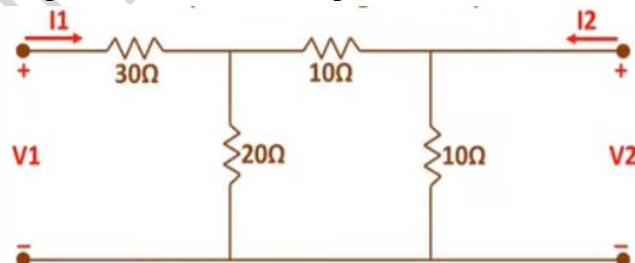**UNIT - V**

7 a) Find the 'ABCD' parameter for the two-port network shown 08



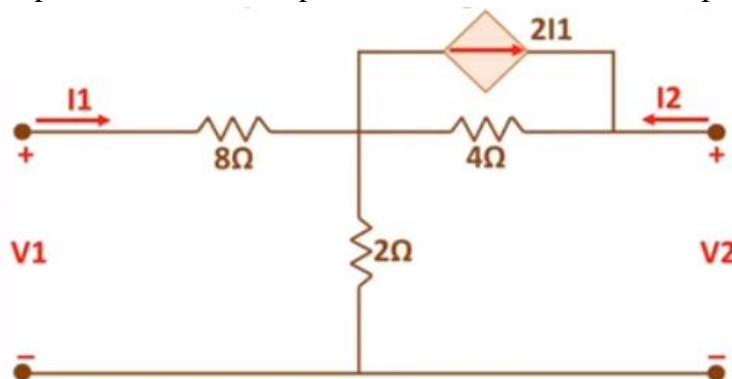b) Determine Z parameters of a two-port network and hence find Y-parameter. 12



\*\*\*\*\*