

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

May 2023 Semester End Main Examinations

Programme: B.E.

Semester: III

Branch: ETE, EIE

Duration: 3 hrs.

Course Code: 22ES3PCECA

Max Marks: 100

Course: Electric Circuit Analysis


Date: 17.05.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.


UNIT - I

1 a) Using loop analysis find V_o in the network shown in fig 1.1

10

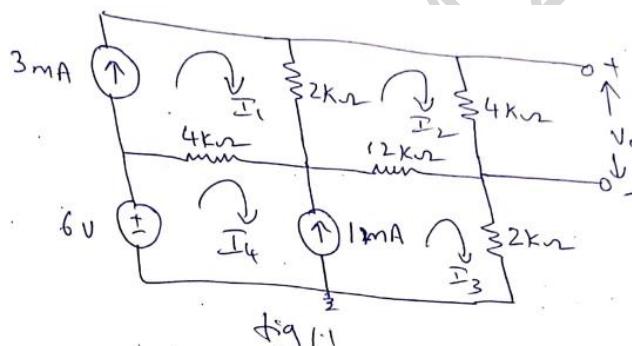

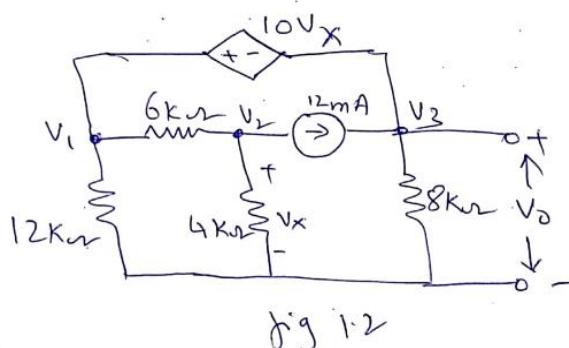
b) Apply nodal analysis to find power dissipated across $8k\Omega$ resistor as shown in Fig 1.2 10



OR

2 a) Find V_o in the network using source transformation for the circuit shown in fig 2.1 06

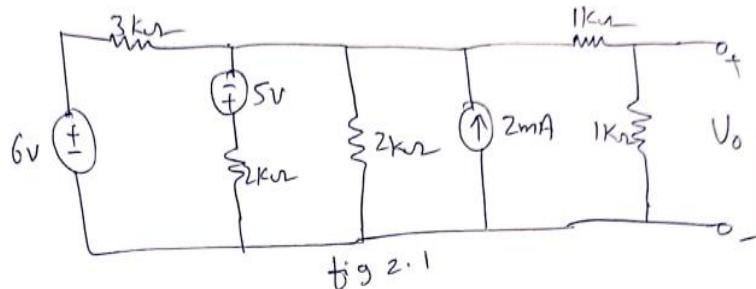Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.



b) Express star network in terms of delta network and find their equivalent resistances **06**

c) For the circuit shown in fig 2.2, find the voltage across 2mA source **08**


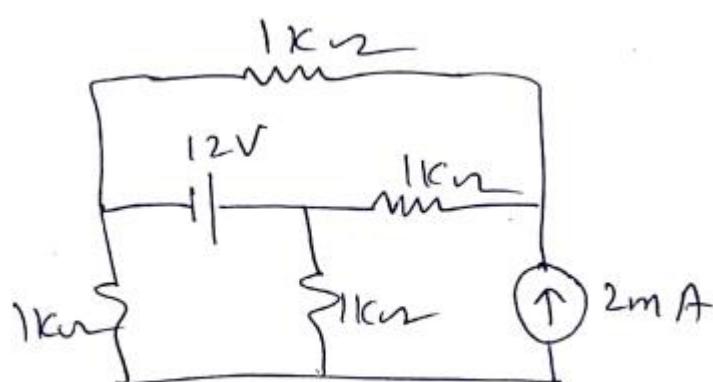


fig 2.2

UNIT - II

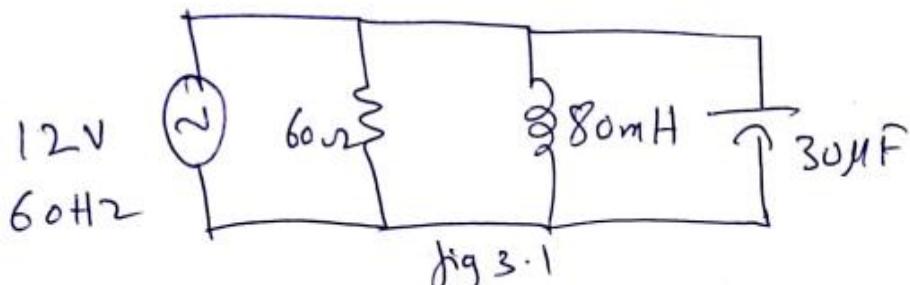3 a) For the parallel resonant circuit shown in fig 3.1, find Z and total current I **06**




b) Derive the expression for quality factor in a series resonant circuit **04**

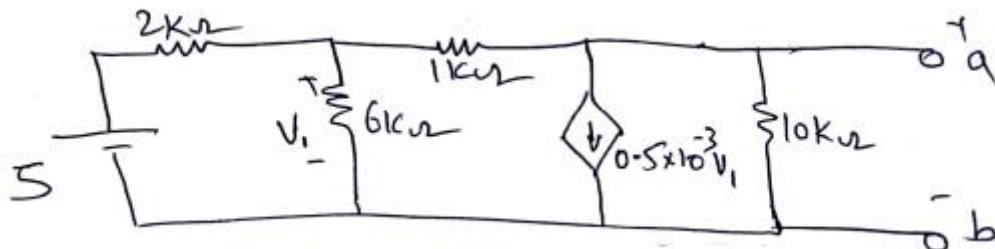c) Select a 3 mesh electrical circuit and indicate graph, branch, node, oriented graph, tree, cotree. Write the incidence matrix, tieset schedule and cutset schedule for the same. **10**

UNIT - III

4 a) Find the Norton's equivalent circuit between a and b **10**



b) Apply superposition theorem to find I_o in the network shown in fig 4.2

10

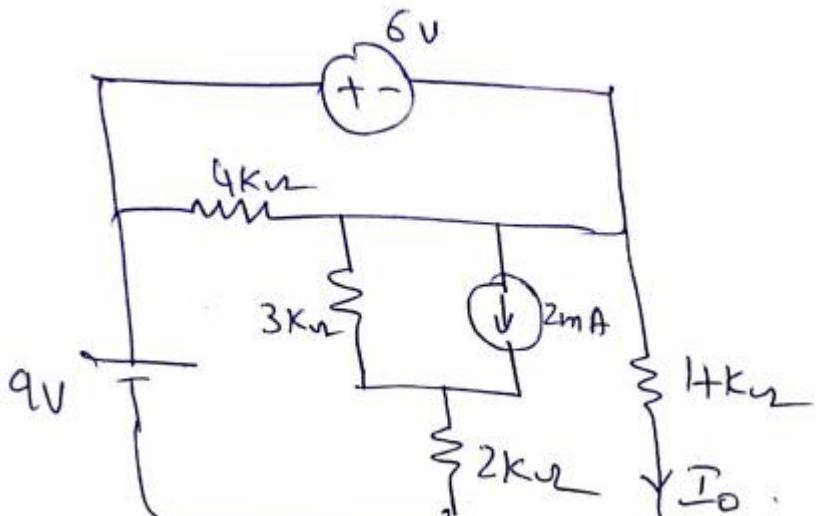


Fig 4.2

UNIT - IV

5 a) For the network shown in fig 5.1, switch k is closed and steady state has been reached. At $t=0$ switch is opened. Find $i(0^+)$, $di(0^+)/dt$, $d^2i(0^+)/dt^2$ at $t=0^+$

07

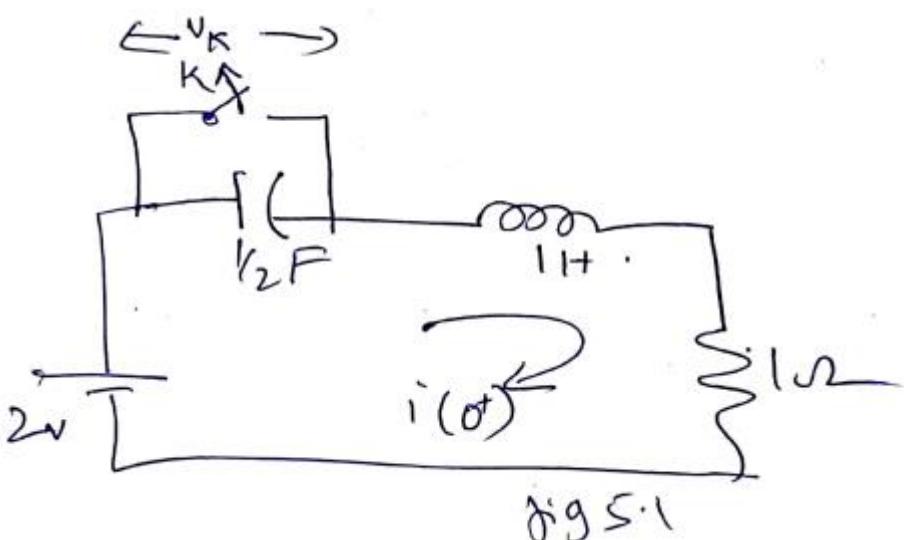


Fig 5.1

b) State and prove initial value theorem

05

c) Find the Laplace transform of the periodic waveform shown in fig 5.2

08


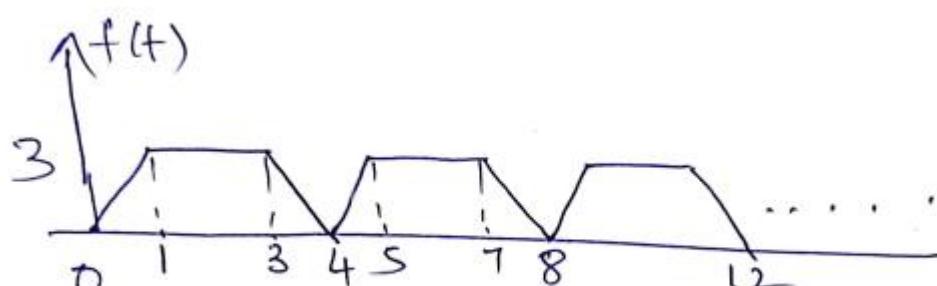


Fig 5.2

OR

6 a) Find the Laplace transform of $f(t)$.

08

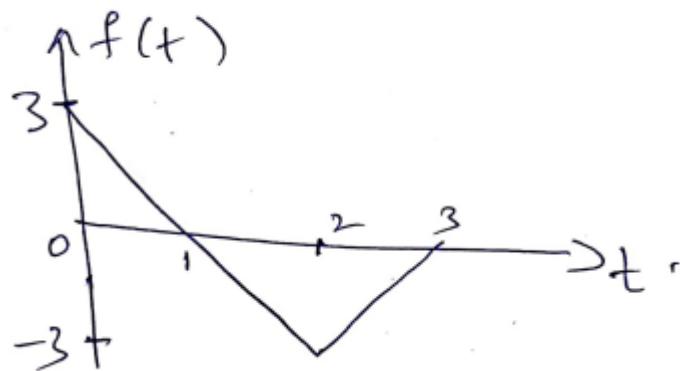

b) Find the Laplace transform of a delayed ramp function

04

c) In the given network fig 6.2, k is closed at $t=0$. Find i , di/dt , d^2i/dt^2

08

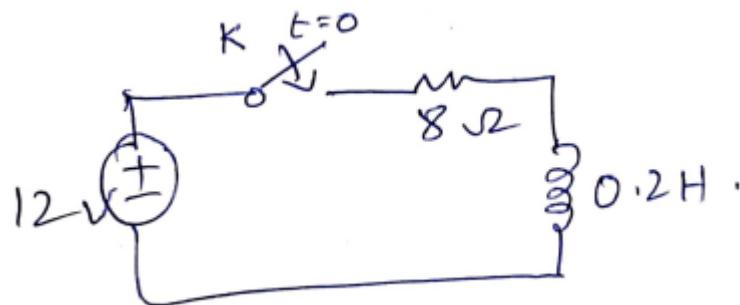


Fig 6.2

UNIT - V

7 a) Define ABCD parameter with relevant mathematical expressions

04

b) Find $[Z]$ and $[T]$ parameters for the circuit shown

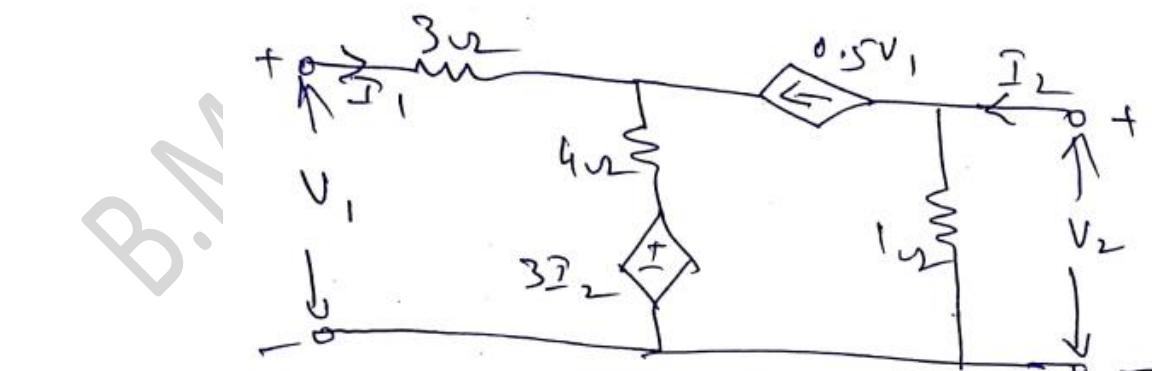


Fig 7.1

c) Derive the relationship between h parameter and Y parameters

06
