

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

May 2023 Semester End Main Examinations

Programme: B.E.

Branch: ES Cluster (EEE/TCE/ECE/EIE/ML)

Course Code: 15ES3GCLCA

Course: Linear Circuit Analysis

Semester: III

Duration: 3 hrs.

Max Marks: 100


Date: 19.05.2023

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I

1 a) For the circuit shown below, determine all the branch currents.

08

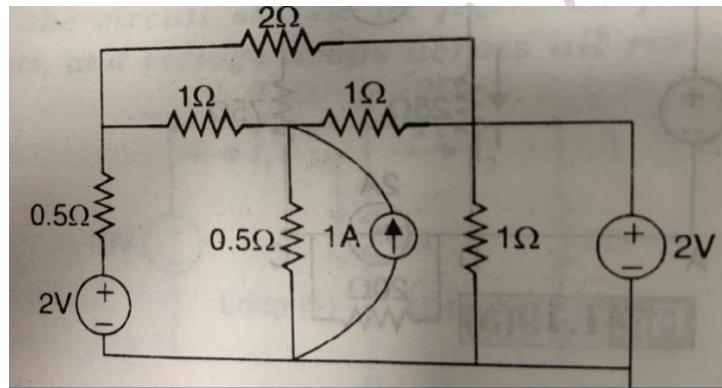


b) Three resistors $R_1=5\Omega$, $R_2=10\Omega$ & $R_3=15\Omega$, are connected in series, and a 10-volt Voltage source is connected across them. Find the voltage drop across R_2 , using voltage division rule.

c) Find the current flowing through 20Ω and 40Ω resistance using KCL

04


08

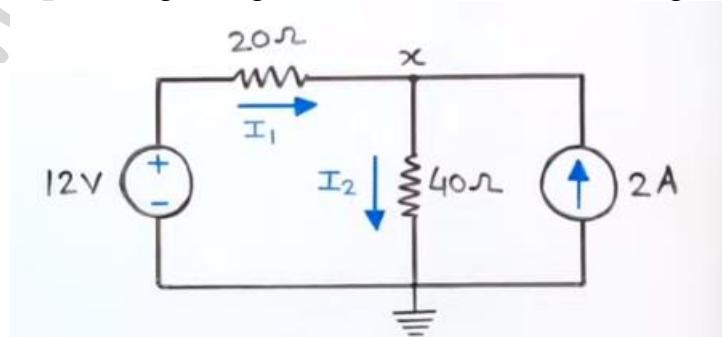


OR

2 a) Find the voltage drop across 10Ω resistance for the circuit shown below using star-delta transformation

12

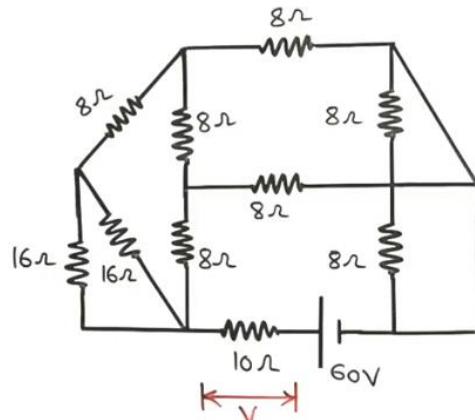

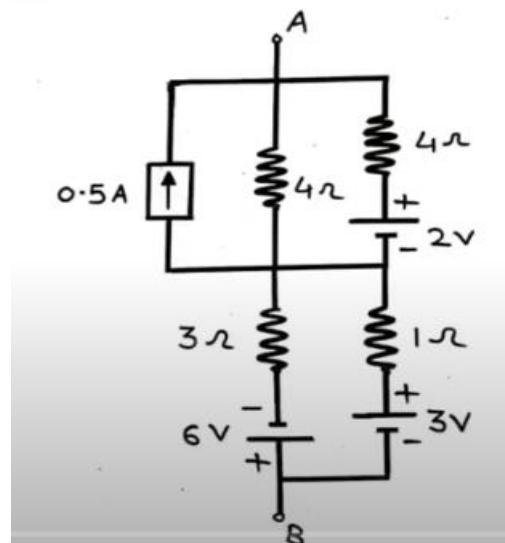
b) Reduce the network shown in fig. into a single current source in parallel with one of the elements. 08



UNIT - II

3 a) A series connected RLC circuit has $R = 15\text{ohm}$, $L = 40\text{mH}$ and $C = 40\mu\text{F}$. Determine the resonant frequency, and under resonant condition, calculate the current, power, the voltage drops across various elements, if the applied voltage is 75 volts. 10

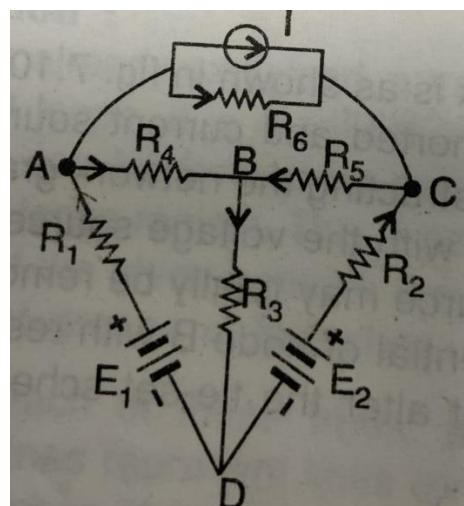
b) For the network shown below, draw the graph, select a tree and write the tie-set schedule. 10



UNIT - III


4 a) Evaluate the current through 10-ohm resistor by Norton Theorem.

10

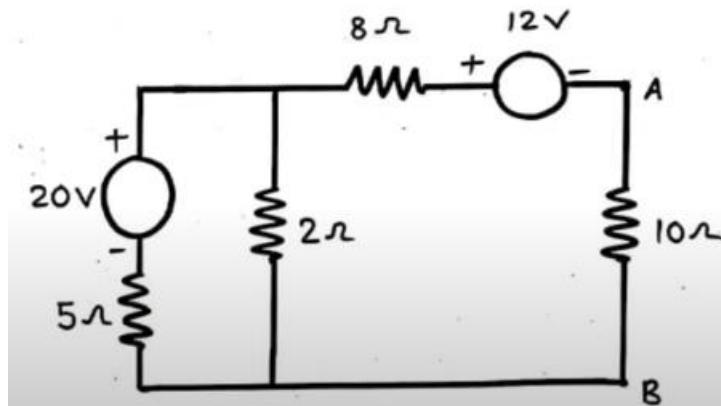

b) For the circuit shown below find the load resistance R_L to have maximum power dissipated. Also find that maximum power.


10

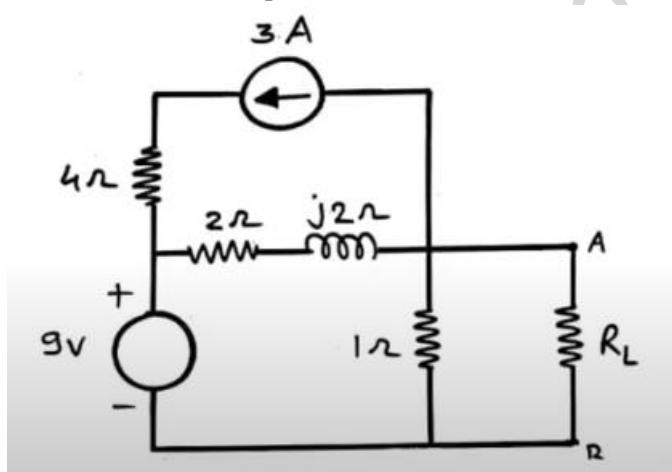

UNIT - IV


5 a) The network achieves a steady state with the switch closed. At $t = 0$, switch is opened. Find $i(t)$ for $t > 0$.

10

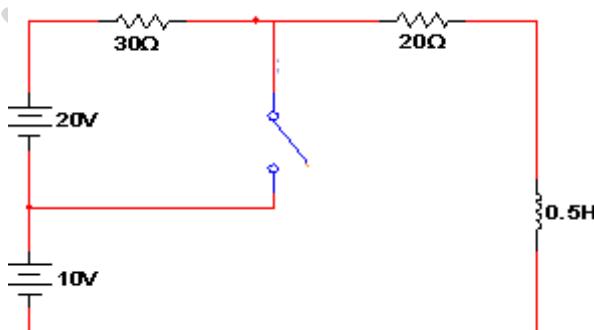


b) In the network steady state is reached with the switch K open. At $t = 0$, switch is closed. Determine the values of $V_a(0^-)$ and $V_a(0^+)$

10

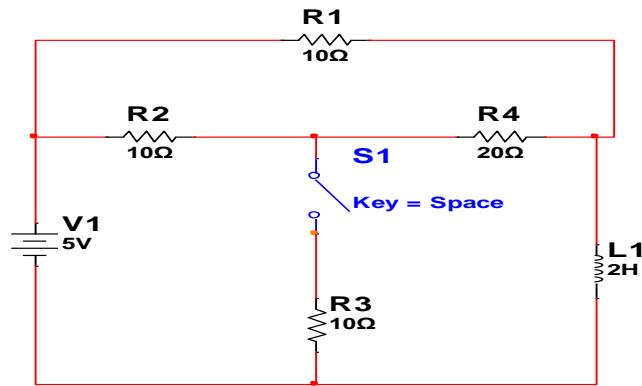


OR

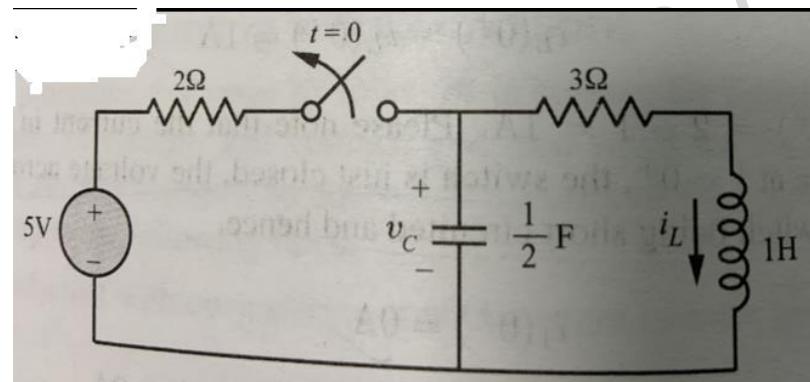
6 a) In the circuit given, find $i_L(0+)$ and $v_C(0+)$. The circuit is in steady state with the switch in closed condition. 07



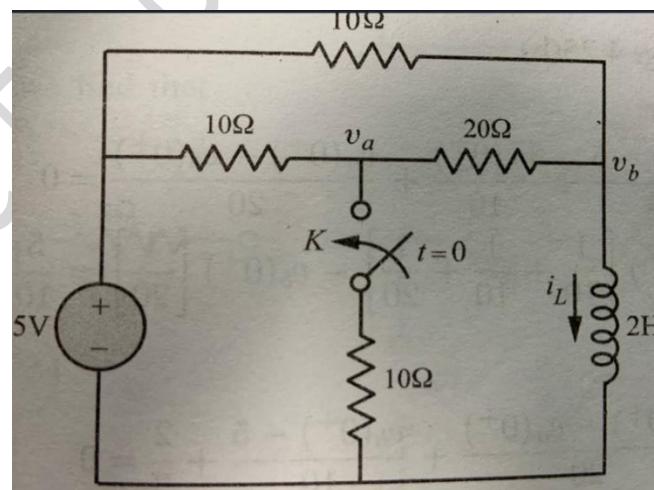b) In the circuit below, a steady state is reached with switch K open. At $t=0$, the switch is closed. For the element values given, determine the values of $v_a(0-)$ and $v_a(0+)$ 08




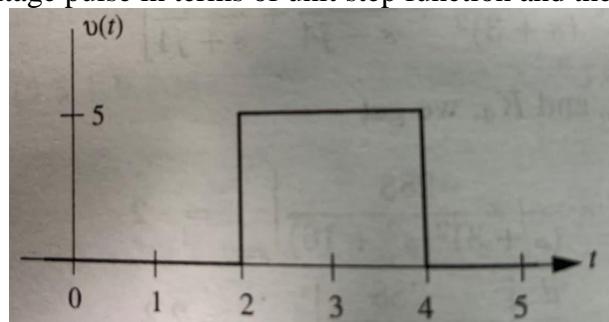c) Express the voltage pulse in terms of unit step function and then find $V(s)$. 05



UNIT - V

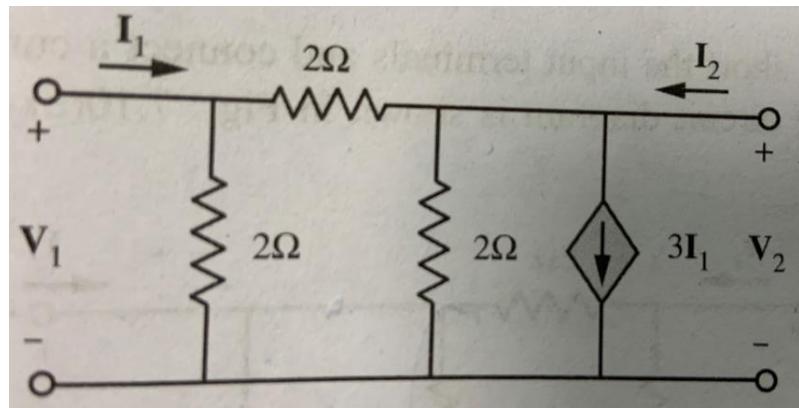7 a) For the network shown in the figure below containing a current- controlled current source. For this network, find the 'z' and 'y' parameters 10



b) Determine the 'Y' parameters for a two-port network if the z parameters are $z = \begin{bmatrix} 10 & 5 \\ 5 & 9 \end{bmatrix}$ 05

c) Following are the hybrid parameter for a network: 05

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 5 & 2 \\ 3 & 6 \end{bmatrix}$$

Determine the 'y' parameters for the network.
